

Pisni izpit 4. 6. 2019

Ime in priimek: _____

Vpisna številka: _____


Naloga 1Določite enosmerno delovno točko tranzistorja (I_D, U_{DS}).

$$U_{DD} = 9V, R_{src} = 100\Omega, R_L = 10k\Omega$$

$$K = 4mA/V^2, U_T = 0.8V, \lambda = 10^{-4}/V$$

$$R_1 = 50k\Omega, R_2 = 15k\Omega, R_D = 5k\Omega, R_S = 1k\Omega$$


$$C_1 = 47\mu F, C_2 = 10\mu F, C_S = 10\mu F$$

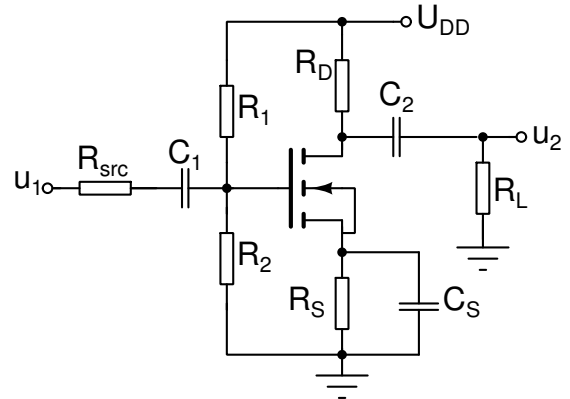**Naloga 2**Delovni tok tranzistorja je $I_D = 1.39mA$. Določite tokovno ojačenje $A_i = \frac{i_2}{i_1}$ pri srednjih frekvencah.

$$U_{DD} = 5V, R_{src} = 50\Omega, R_L = 1k\Omega$$

$$K = 5mA/V^2, U_T = 1.2V, \lambda = 10^{-4}/V$$

$$R_1 = 10k\Omega, R_2 = 20k\Omega, R_S = 1k\Omega$$

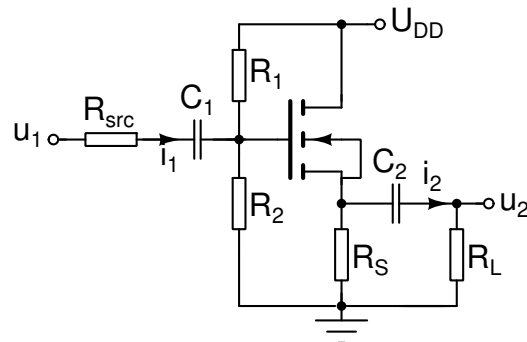
**Naloga 3**Določite zgornjo frekvenčno mejo za napetostno ojačenje $A_u = \frac{u_2}{u_1}$. Admitančni parametri tranzistorja za orientacijo s skupnim emitorjem so:

$$Y_E = \begin{bmatrix} 71.9\mu S & 0 \\ 18.0mS & 4.5\mu S \end{bmatrix}$$

$$U_{CC} = 9V, R_{src} = 100\Omega, R_L = 5k\Omega$$


$$R_1 = 20k\Omega, R_2 = 3k\Omega, R_E = 1k\Omega, R_C = 8k\Omega$$

$$C_1 = C_2 = C_E = 10\mu F, C_{be} = 25pF, C_{bc} = 2pF$$

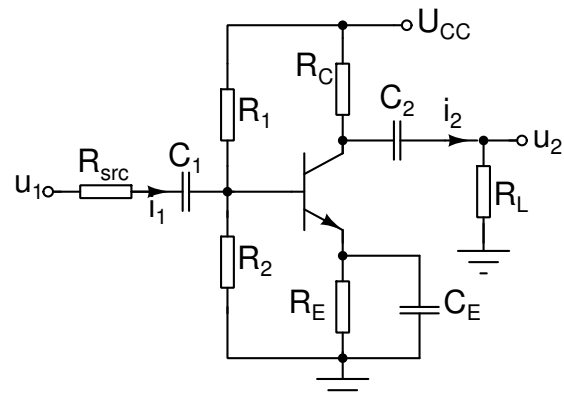**Naloga 4**Določite R_E, R_C , da bo v delovni točki $I_C = 1mA, U_{CE} = 6V$.

$$U_{CC} = -U_{EE} = 9V, R_B = 50k\Omega$$
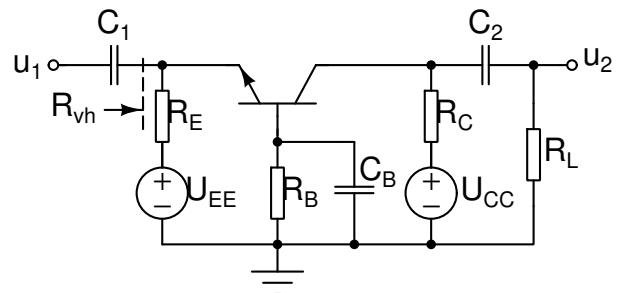
$$\beta_F = 250, V_{AF} = 100V, R_L = 10k\Omega$$



Admitančni parametri:

$$\begin{aligned}i_1 &= y_{11}u_1 + y_{12}u_2 \\i_2 &= y_{21}u_1 + y_{22}u_2 \\y_{11} &= \frac{1}{h_{11}}, \quad y_{12} = -\frac{h_{12}}{h_{11}} \\y_{21} &= \frac{h_{21}}{h_{11}}, \quad y_{22} = \frac{D_h}{h_{11}}\end{aligned}$$

$$A_u = -\frac{y_{21}}{y_{22} + Y_L}, \quad A_i = \frac{y_{21}}{y_{11} + Z_L D_y}, \quad Y_{in} = y_{11} - \frac{y_{12}y_{21}}{y_{22} + Y_L}, \quad Y_{out} = y_{22} - \frac{y_{12}y_{21}}{y_{11} + Y_{src}}$$

Hibridni parametri:

$$\begin{aligned}u_1 &= h_{11}i_1 + h_{12}u_2 \\i_2 &= h_{21}i_1 + h_{22}u_2 \\h_{11} &= \frac{1}{y_{11}}, \quad h_{12} = -\frac{y_{12}}{y_{11}} \\h_{21} &= \frac{y_{21}}{y_{11}}, \quad h_{22} = \frac{D_y}{y_{11}}\end{aligned}$$

NMOS (skupni izvor):

za $u_{GS} > U_T, u_{DS} > u_{GS} - U_T$:

$$\begin{aligned}i_D &= \frac{1}{2}K(u_{GS} - U_T)^2(1 + \lambda u_{DS}) \\g_{21} &= \frac{2I_D}{U_{GS} - U_T}, \quad g_{22} = \frac{\lambda I_D}{1 + \lambda U_{DS}}\end{aligned}$$

PMOS (skupni izvor):

za $-u_{GS} > U_T, -u_{DS} > -u_{GS} - U_T$:

$$\begin{aligned}-i_D &= \frac{1}{2}K(u_{GS} + U_T)^2(1 - \lambda u_{DS}) \\g_{21} &= \frac{2I_D}{U_{GS} + U_T}, \quad g_{22} = \frac{\lambda I_D}{1 - \lambda U_{DS}}\end{aligned}$$

NPN (skupni emitor):

v aktivnem področju:

$$\begin{aligned}g_{11} &= \frac{I_B}{V_T}, \quad g_{21} = \frac{I_C}{V_T}, \\g_{22} &= \frac{I_C}{U_{CE} + V_{AF}} \\ \frac{g_{21}}{g_{11}} &= \beta = \beta_F(1 + \frac{U_{CE}}{V_{AF}})\end{aligned}$$

PNP (skupni emitor):

v aktivnem področju:

$$\begin{aligned}g_{11} &= -\frac{I_B}{V_T}, \quad g_{21} = -\frac{I_C}{V_T}, \\g_{22} &= \frac{-I_C}{-U_{CE} + V_{AF}} \\ \frac{g_{21}}{g_{11}} &= \beta = \beta_F(1 + \frac{-U_{CE}}{V_{AF}})\end{aligned}$$

RC člen - mejna frekvenca: $f_{-3dB} = \frac{1}{2\pi\tau} = \frac{1}{2\pi R_{eq}C}$ Miller-jev pojav (preslikava impedance med vhom in izhodom tranzistorja z napetostnim ojačenjem A_0 na vhod tranzistorja):

$$Z_{M,vhod} = \frac{Z_{vhod-izhod}}{1-A_0} \Rightarrow \text{za skupni emitor: } C_M = (1 - A_0)C_{bc}$$

Kvadratna enačba:

$$\begin{aligned}ax^2 + bx + c &= 0 \\D &= b^2 - 4ac \\x_{i,2} &= \frac{-b \pm \sqrt{D}}{2a}\end{aligned}$$