



b)  $I_C = 1\text{mA}$

$R_S[\text{k}\Omega]$	0	10	100	330	560	1000
$Z_{izh}[\Omega]$						

