



Laboratorij za načrtovanje integriranih vezij



FE

UNIVERZA V LJUBLJANI  
Fakulteta za elektrotehniko


## Linearna elektronska vezja

### Bipolarni tranzistor: Ojačevalnik


#### In this chapter, we will:

- ▶ Investigate a single-transistor circuit that can amplify a small, time-varying input signal
  - ▶ Develop small-signal models that are used in the analysis of linear amplifiers
- ▶ Discuss and compare the three basic transistor amplifier configurations.
  - ▶ Analyze the common-emitter amplifier.
  - ▶ Analyze the emitter-follower amplifier.
  - ▶ Analyze the common-base amplifier.
- ▶ Analyze multitransistor or multistage amplifiers.

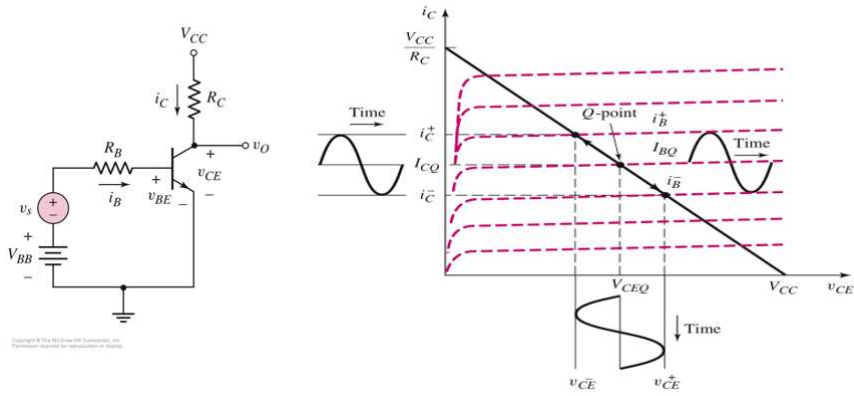
### Common Emitter with Time-Varying Input




### $I_B$ Versus $V_{BE}$ Characteristic

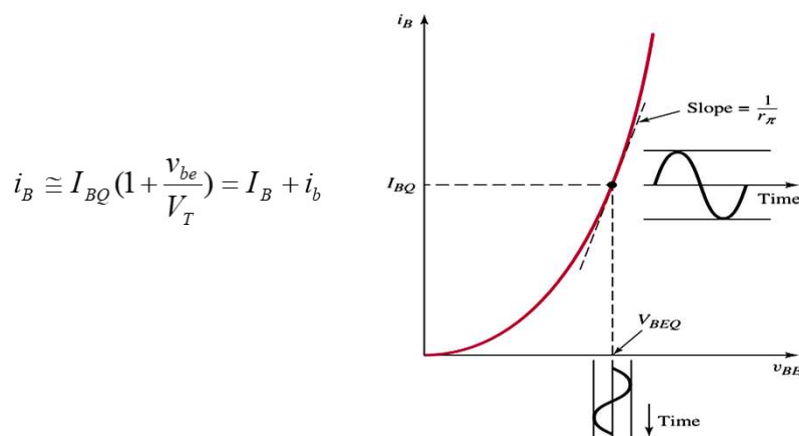
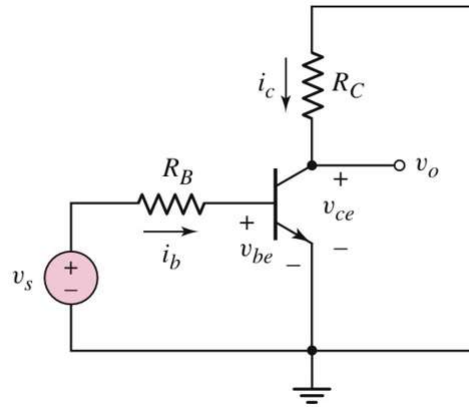
### ac Equivalent Circuit for Common Emitter


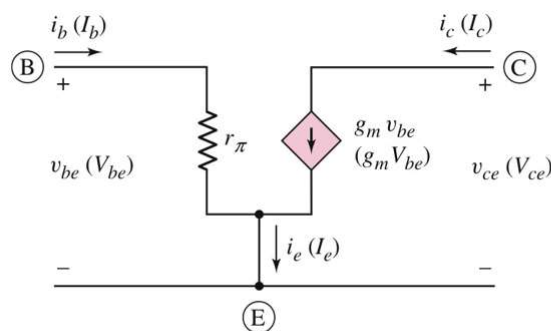
### Small-Signal Hybrid $\pi$ Model for npn BJT



$$g_m = \frac{I_{CQ}}{V_T}$$


$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m r_\pi = \beta$$


Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.


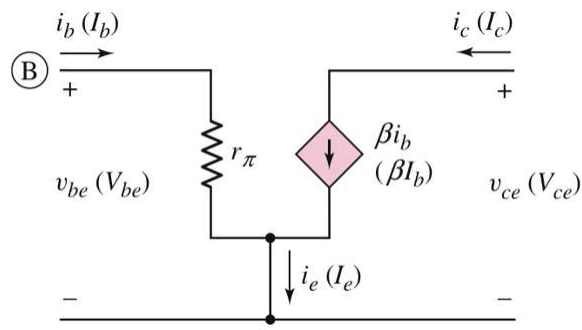
### S-S EC Using Common-Emitter Current Gain


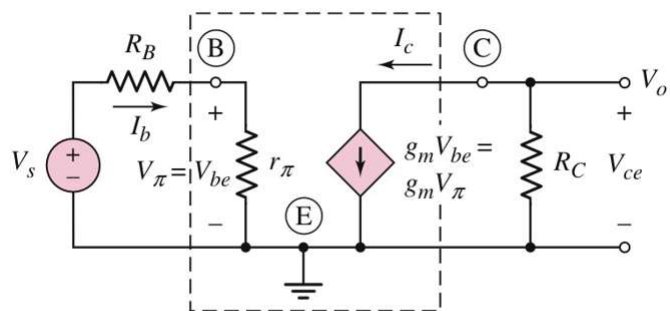
### S-S EC for npn Common Emitter circuit




Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

$$A_v = -(g_m R_C) \left( \frac{r_\pi}{r_\pi + R_B} \right)$$

### Problem Solving Techniques


1. Analyze circuit with only the dc sources to find quiescent solution.
  - Transistor must be biased in active region for linear amplifier.
2. Replace elements with small-signal model.
3. Analyze small-signal equivalent circuit, setting dc sources to zero, to produce the circuit to the time-varying input signals only.
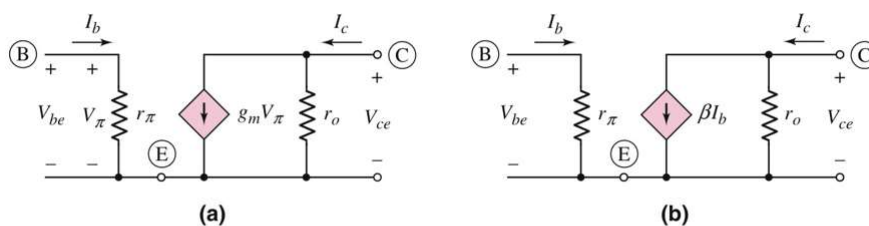
### Hybrid $\pi$ Model for npn with Early Effect




$$r_o = \frac{V_A}{I_{CQ}}$$

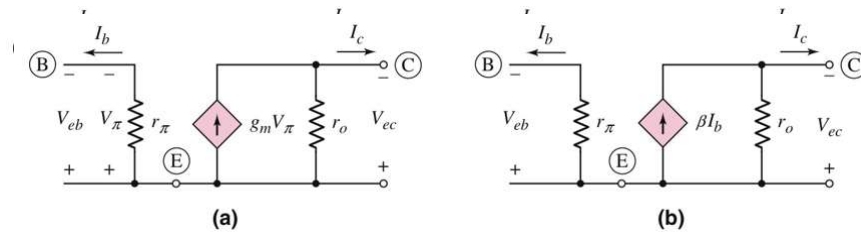
### Hybrid $\pi$ Model for pnp with Early Effect



### Expanded Hybrid $\pi$ Model for npn

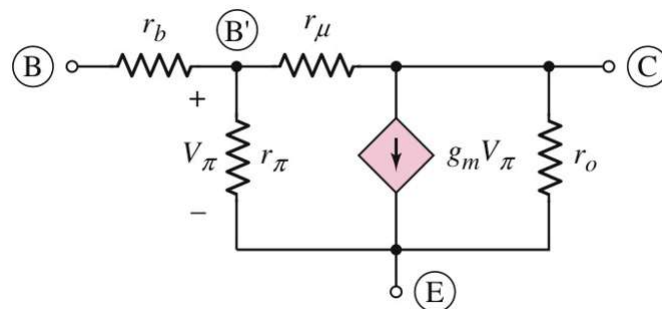

### h-Parameter Model for npn

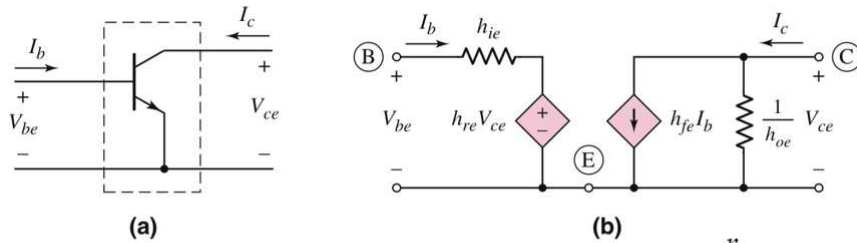


$$h_{ie} = r_b + r_\pi \parallel r_\mu$$

$$h_{fe} = \beta$$


$$h_{re} \cong \frac{r_\pi}{r_\mu}$$

$$h_{oe} = \frac{1 + \beta}{r_\mu} + \frac{1}{r_o}$$

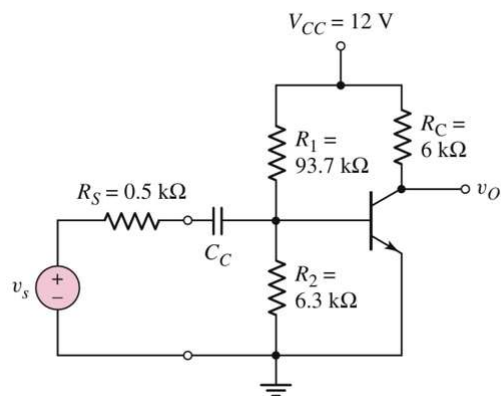
### C-E with Voltage-Divider Bias and a Coupling Capacitor


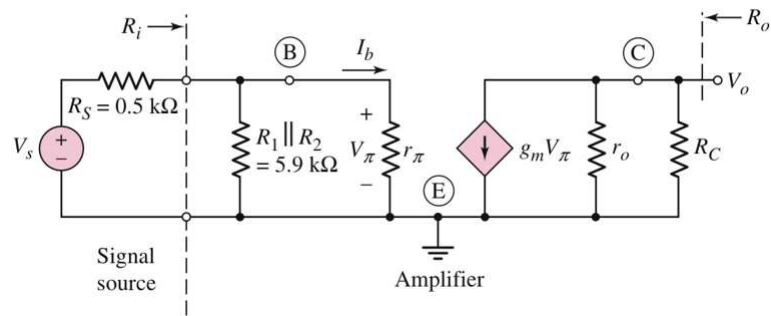
### S-S EC – Coupling Capacitor Assumed a Short



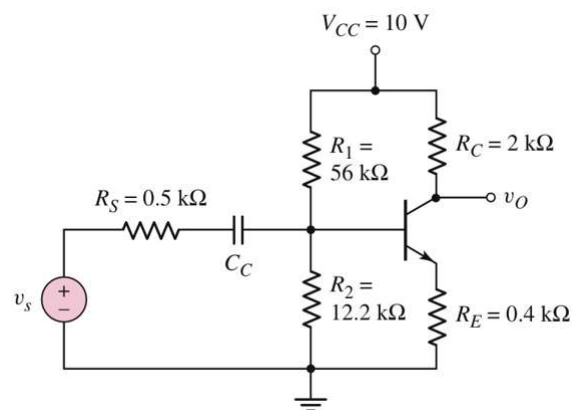
### npn Common Emitter with Emitter Resistor





### S-S EC – Common Emitter with $R_E$

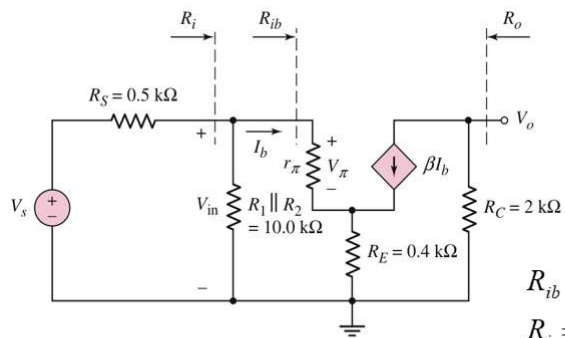


$$R_{ib} = r_{\pi} + (1 + \beta)R_E$$

$$R_i = R_1 \parallel R_2 \parallel R_{ib}$$


$$A_v = \frac{-\beta R_C}{r_{\pi} + (1 + \beta)R_E} \left( \frac{R_i}{R_i + R_S} \right)$$

Copyright © The McGraw-Hill Companies, Inc.  
Permission is granted for reproduction or display.


### $R_E$ and Emitter Bypass Capacitor

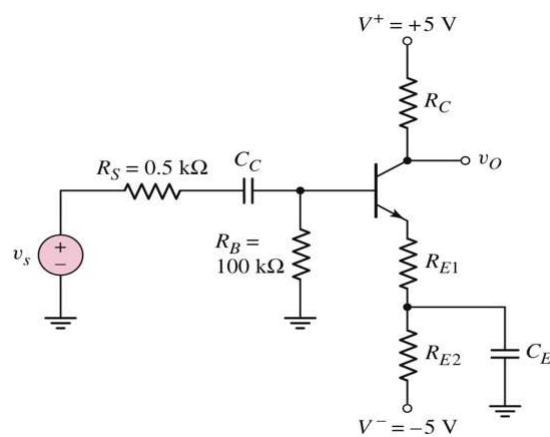

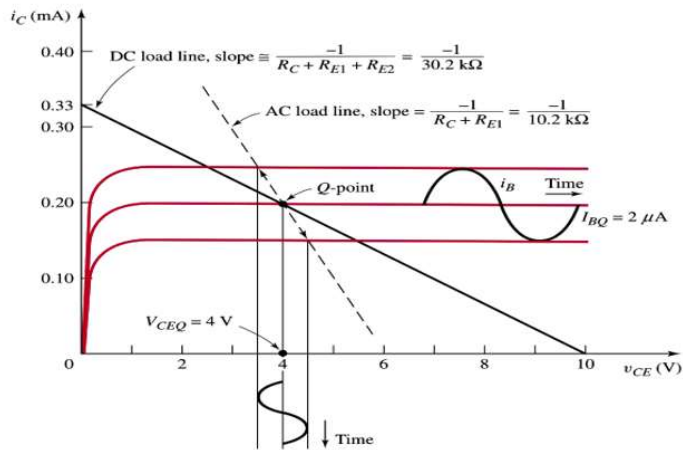
dc AND ac Load Lines:  
 $R_E$  and Emitter Bypass Capacitor



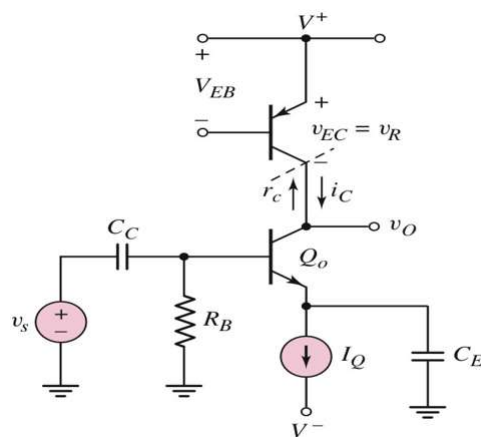Current Source Biasing and Nonlinear Load



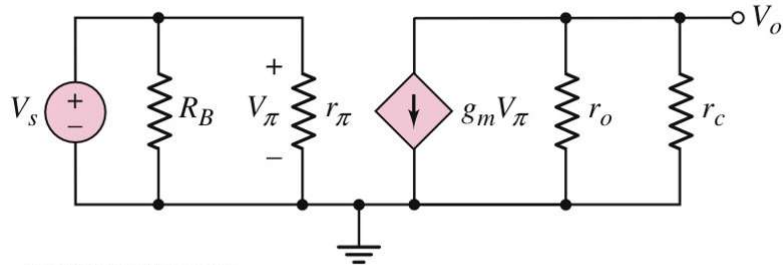
### S-S EC with Current Biasing and Nonlinear Load




Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

$$A_v = -g_m (r_o \parallel r_c)$$
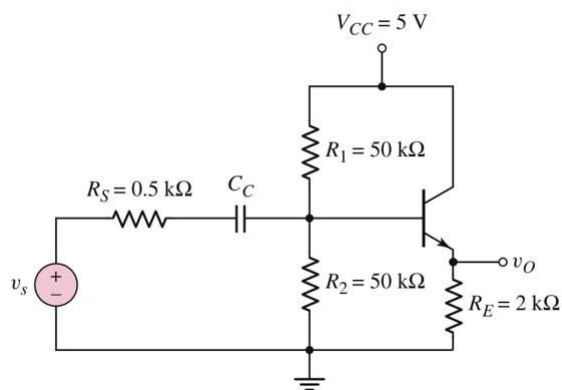
### Common-Collector or Emitter-Follower Amplifier



### S-S EC: Emitter Follower

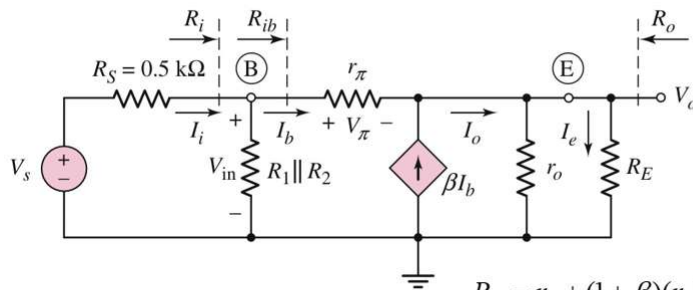


Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

$$R_{ib} = r_{\pi} + (1 + \beta)(r_o \parallel R_E)$$

$$R_i = R_1 \parallel R_2 \parallel R_{ib}$$

$$A_v = \frac{(1 + \beta)(r_o \parallel R_E)}{r_{\pi} + (1 + \beta)(r_o \parallel R_E)} \left( \frac{R_i}{R_i + R_S} \right)$$


### Output Resistance: Emitter Follower

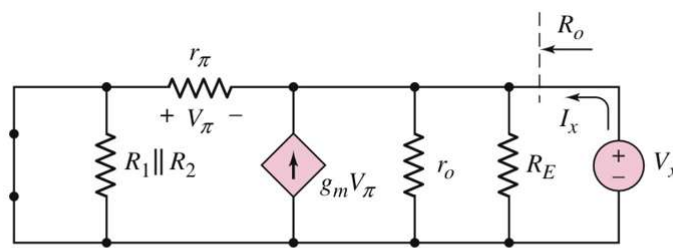


Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

$$R_o = \frac{r_{\pi}}{1 + \beta} \parallel R_E \parallel r_o$$

### Common-Base Amplifier

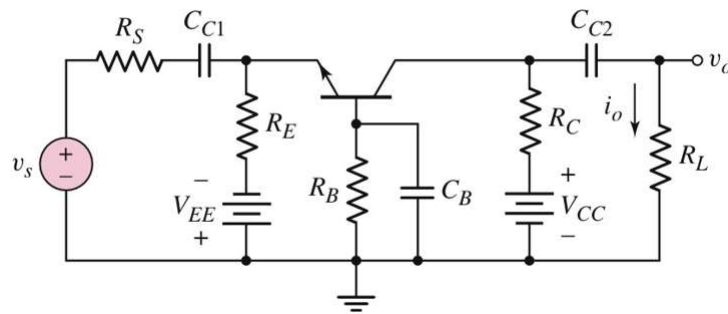

### S-S EC: Common Base

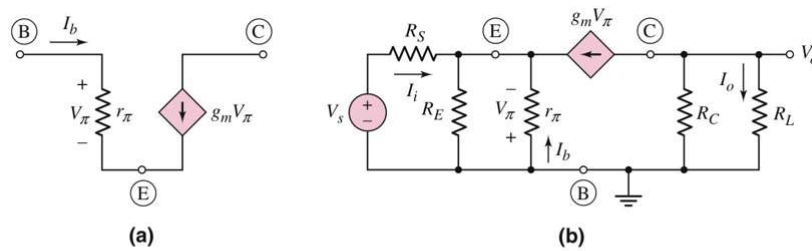


Copyright © The McGraw-Hill Companies, Inc. Permission is required for reproduction or display.

$$A_v = g_m (R_C \parallel R_L)$$

$$A_i = g_m \left( \frac{R_C}{R_C + R_L} \right) \left[ \frac{r_\pi}{1 + \beta} \parallel R_E \right]$$


### Input Resistance: Common Base

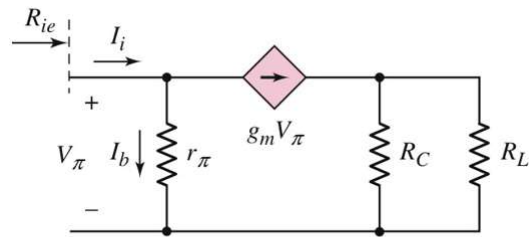

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

$$R_{ie} = r_{\pi}/(1+\beta)$$


### Output Resistance: Common Base

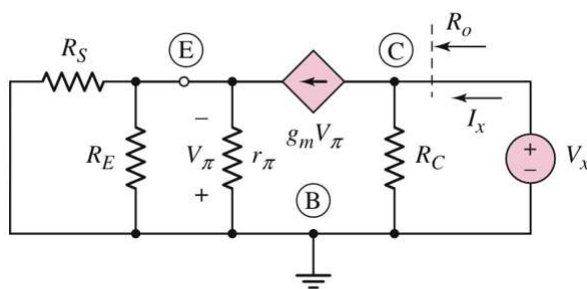


Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

$$R_o = R_C$$


### Common Emitter Cascade Amplifier

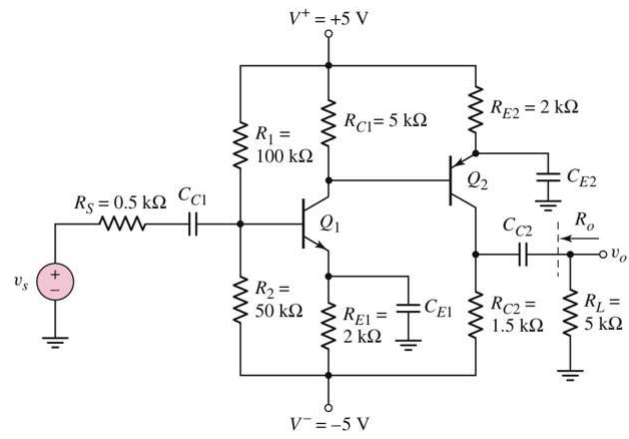

### S-S EC: Cascade Amplifier

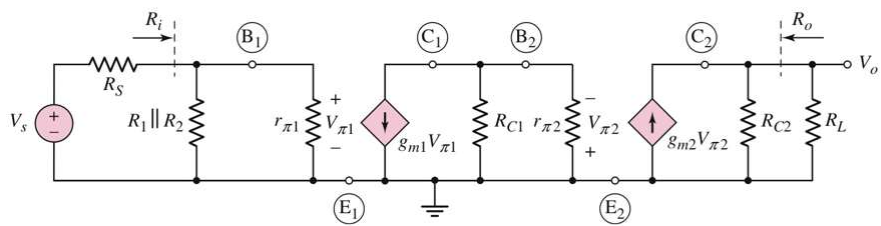


### Darlington Pair

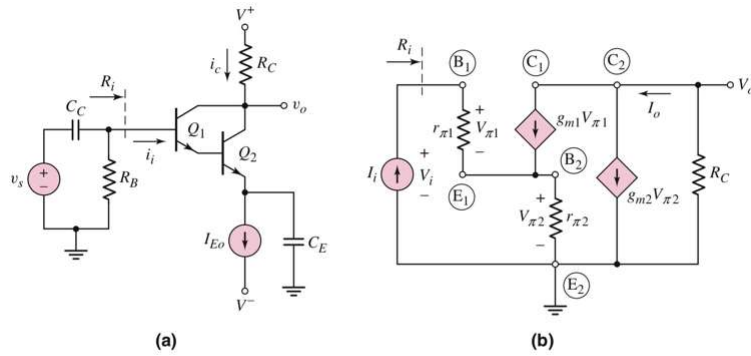


$$A_i \cong \beta_1 \beta_2$$

### Cascode Amplifier

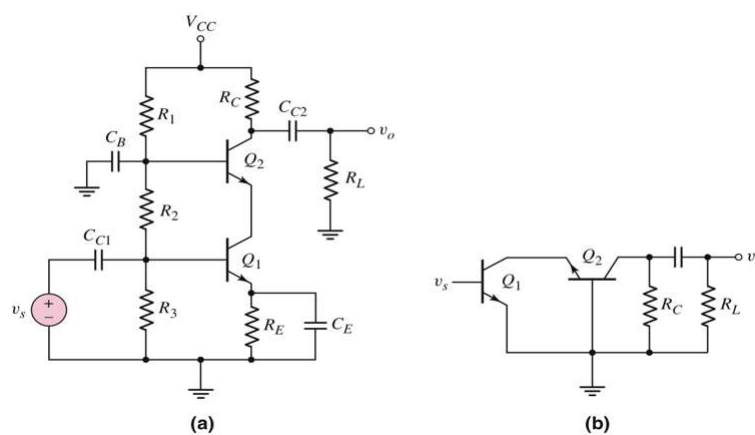



### S-S EC: Cascode Amplifier

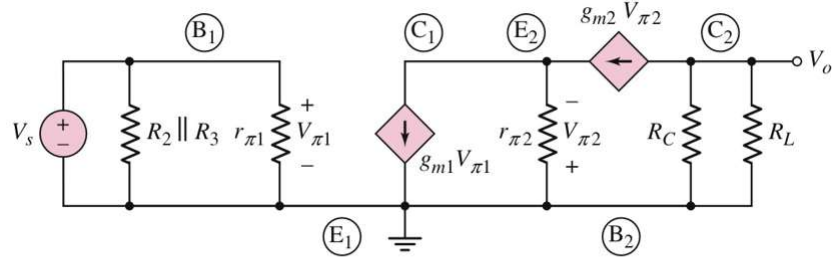

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

$$A_v \cong -g_{m1} (R_C \parallel R_L)$$