

# Microelectronics Circuit Analysis and Design

Donald A. Neamen

## Chapter 11

### *Differential and Multistage Amplifiers*

---

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-1

In this chapter, we will:

- ❑ Describe the characteristics and terminology of the ideal differential amplifier.
- ❑ Describe the characteristics of and analyze:
  - the basic bipolar differential amplifier.
  - the basic FET differential amplifier.
  - BJT and FET differential amplifiers with active loads.
  - various BiCMOS circuits.
- ❑ Analyze multistage amplifiers.
- ❑ Analyze the frequency response of the differential amplifier.


---

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-2

## BJT Differential-Pair Amplifier

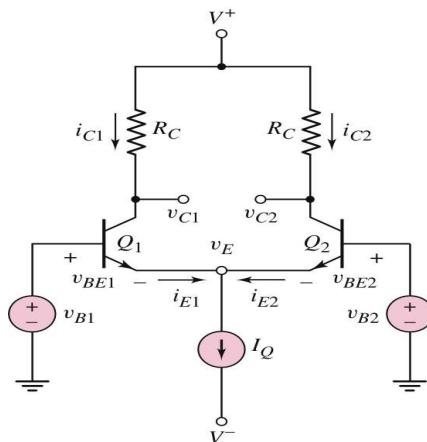

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.


Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-3
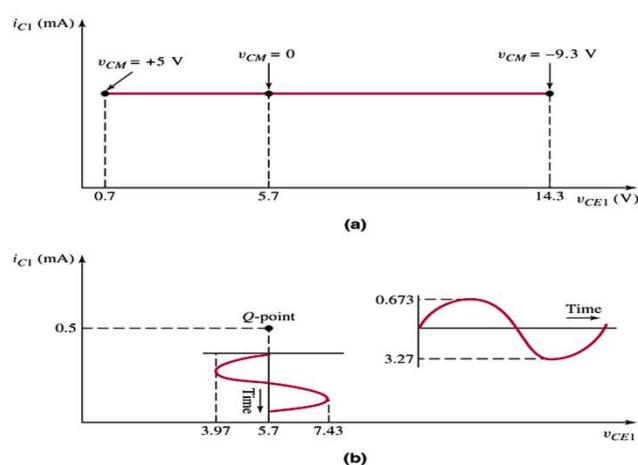
## Variation of Q-Point for Diff-Amp

Common-mode  
input voltage  
varied between  
+5V to -9.3V




Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-4
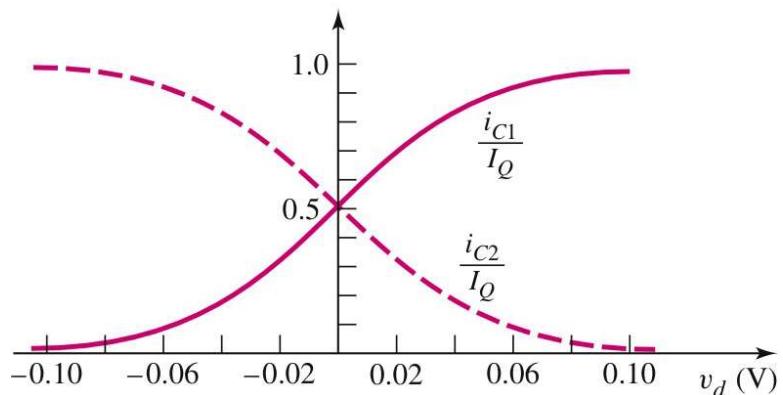
## DC Transfer Characteristics: Bipolar Differential Amplifier




Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-5
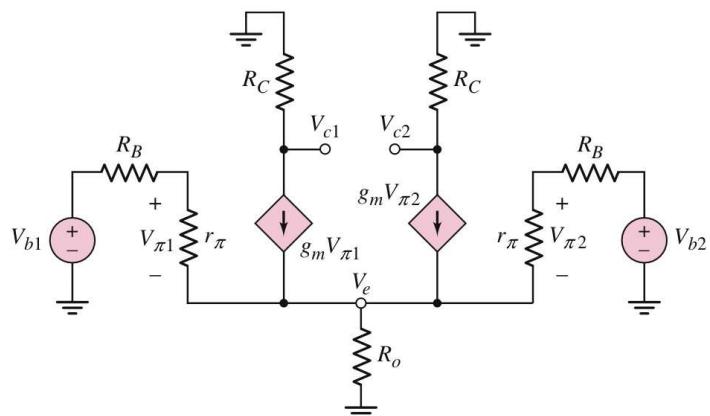
## Small-Signal Equivalent Circuit: Bipolar Differential Amplifier



Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display


Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-6

## ■ Equivalent AC Circuit: Bipolar Differential Amplifier

## Differential-mode input

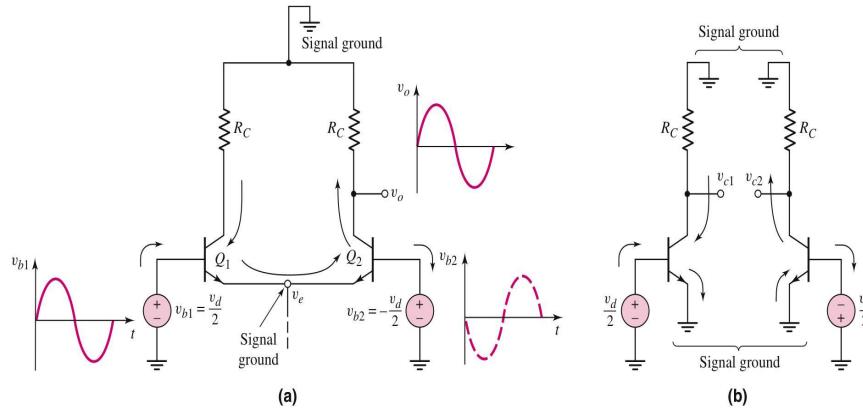


## Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-7

## ■ Equivalent AC Circuit: Bipolar Differential Amplifier

### Common-mode input

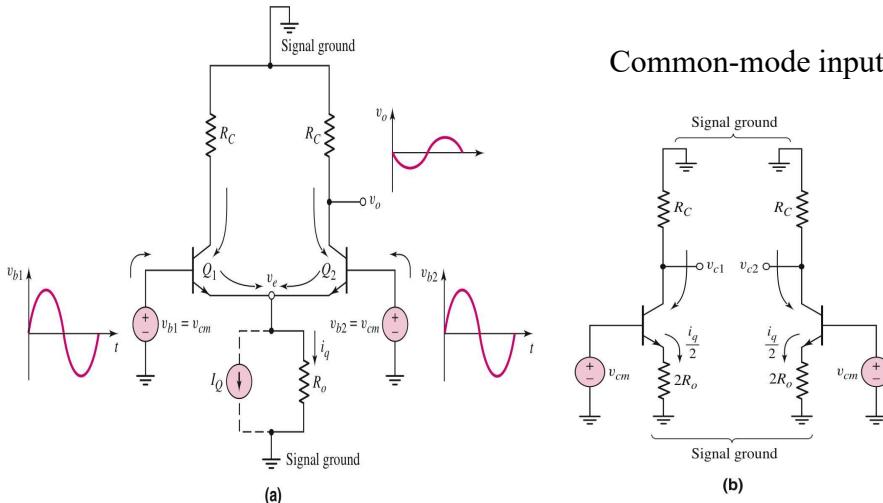

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-8

## Problem-Solving Technique: Diff-Amps with Resistive Loads


1. Apply pure differential-mode input voltage and use differential-mode half-circuit to determine differential-mode gain.
2. Apply pure common-mode input voltage and use common-mode half-circuit to determine common-mode gain.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-9

## MOSFET Differential Pair

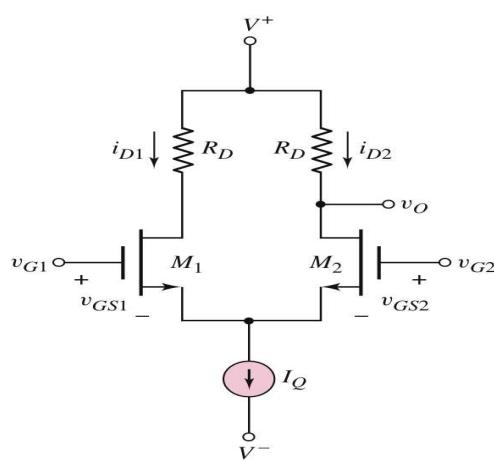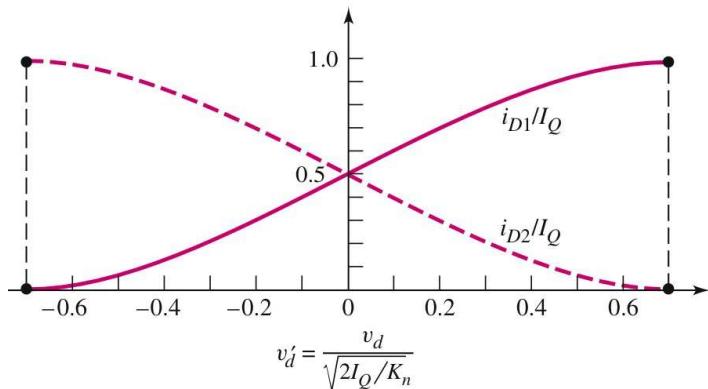

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-10

## DC Transfer Characteristics: MOSFET Differential Amplifier




Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-11
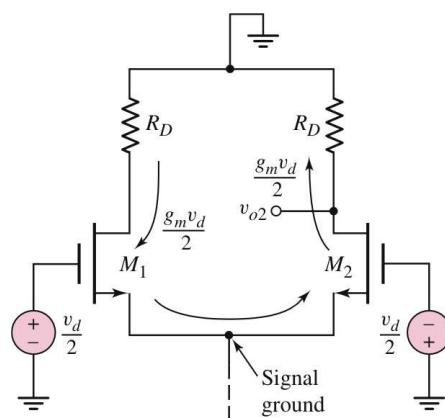
## Small-Signal Equivalent Circuit: MOSFET Differential Amplifier




Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-12
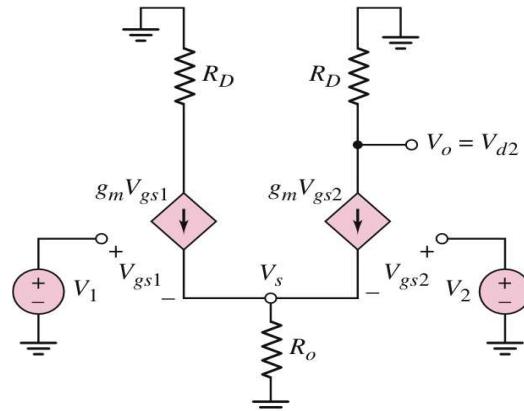
## Small-Signal Equivalent Circuit: MOSFET Differential Amplifier




Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-13
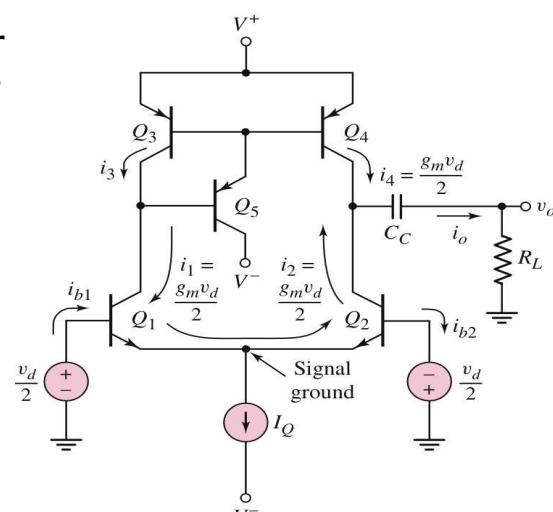
## BJT Diff-Amplifier with 3-Transistor Active Load




Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-14

## Small-Signal Equivalent Circuit: BJT Diff-Amplifier with Active Load

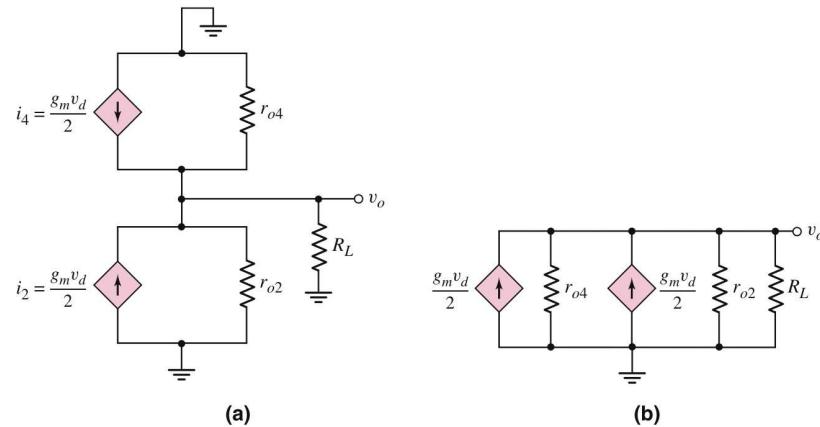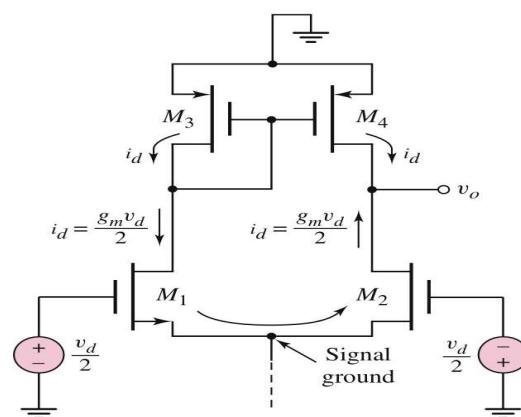

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-15

## AC Equivalent Circuit: MOSFET Diff-Amp with Active Load

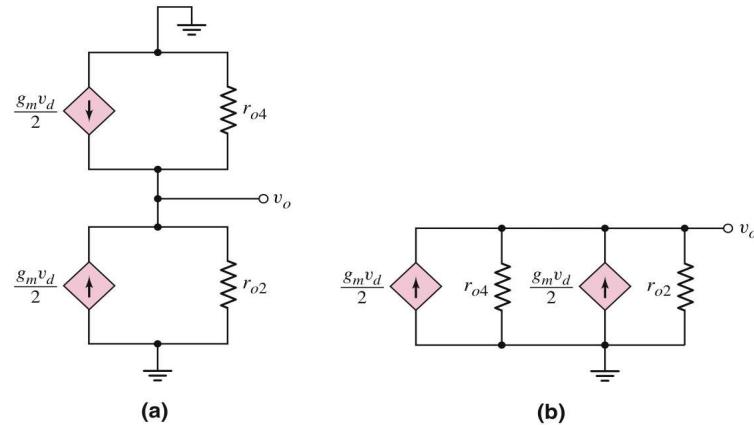

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-16

## Small-Signal Equivalent Circuit: MOSFET Diff-Amplifier with Active Load

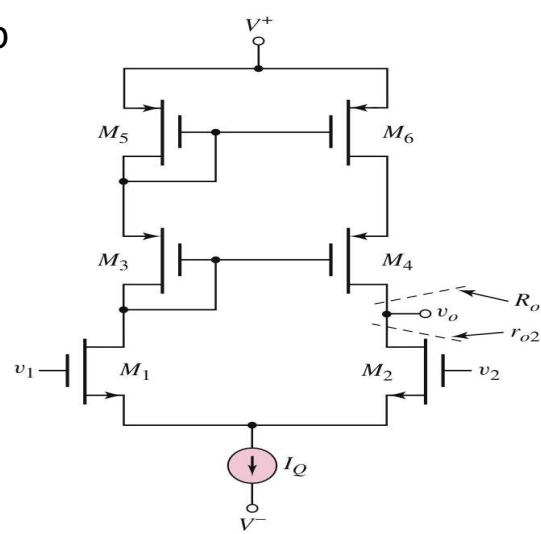

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-17

## MOSFET Diff-Amp with Cascode Active Load


Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.


Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-18


## Darlington Pair

Bipolar configuration

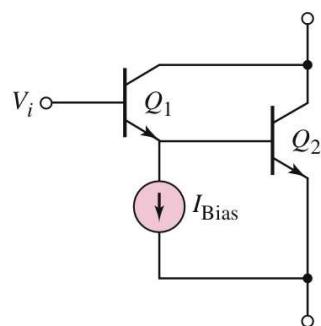

(a)

BiMOS configuration

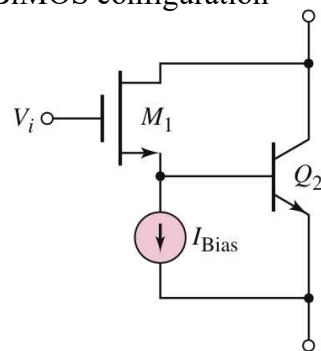

(b)

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.


Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-19


## Cascode Configuration

Bipolar configuration

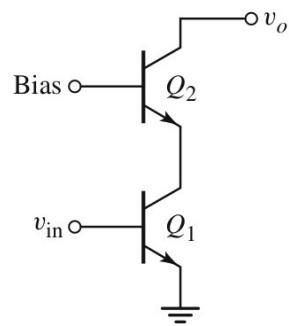

(a)

BiMOS configuration

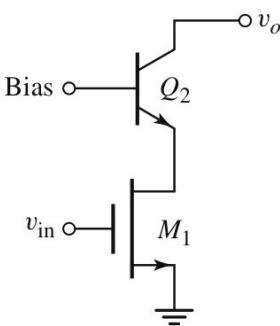

(b)

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.


Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-20

## Cascode Constant-Current Source


Bipolar configuration

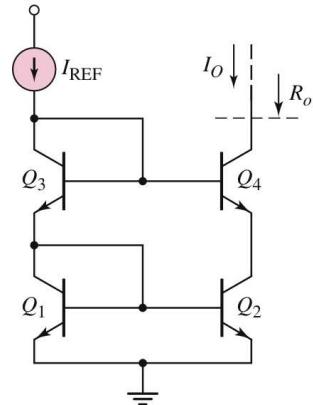

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

BiMOS double cascode configuration

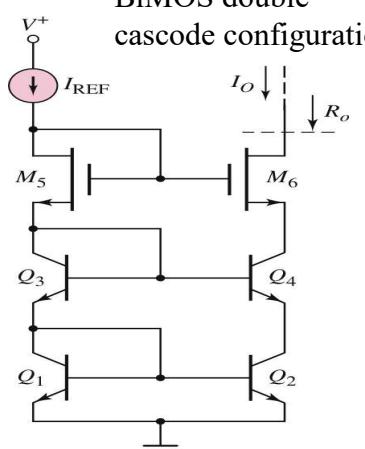


Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Microelectronics, 4e  
McGraw-Hill

Chapter 11-21
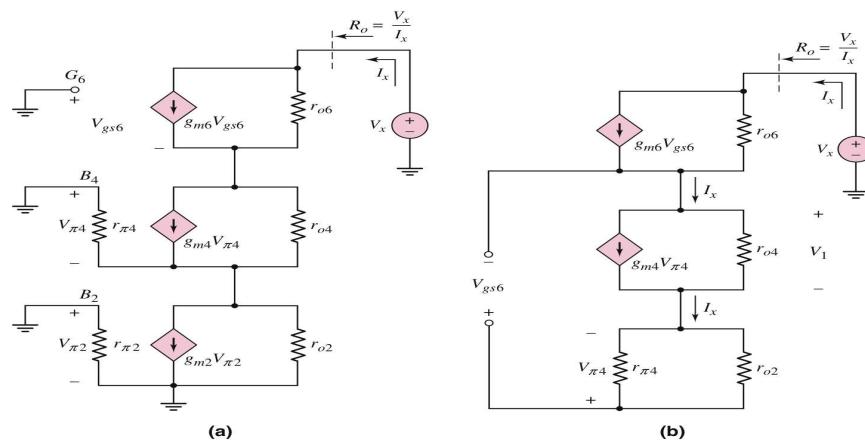
## Small-Signal Equivalent Circuit: BiMOS Double Cascode Current Source





Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.


Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-22

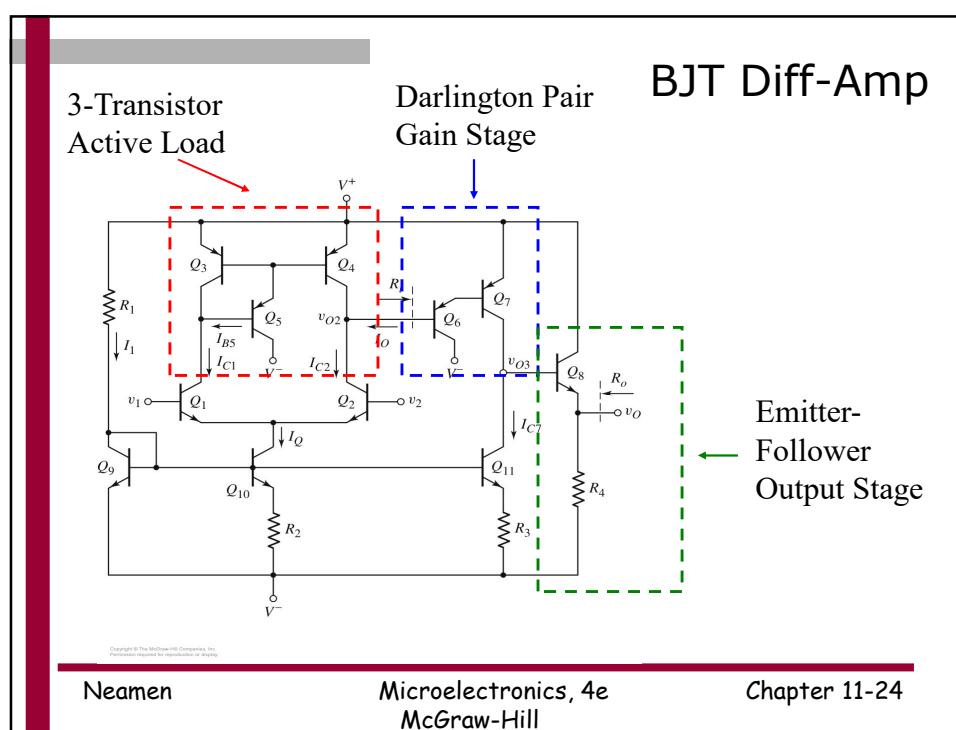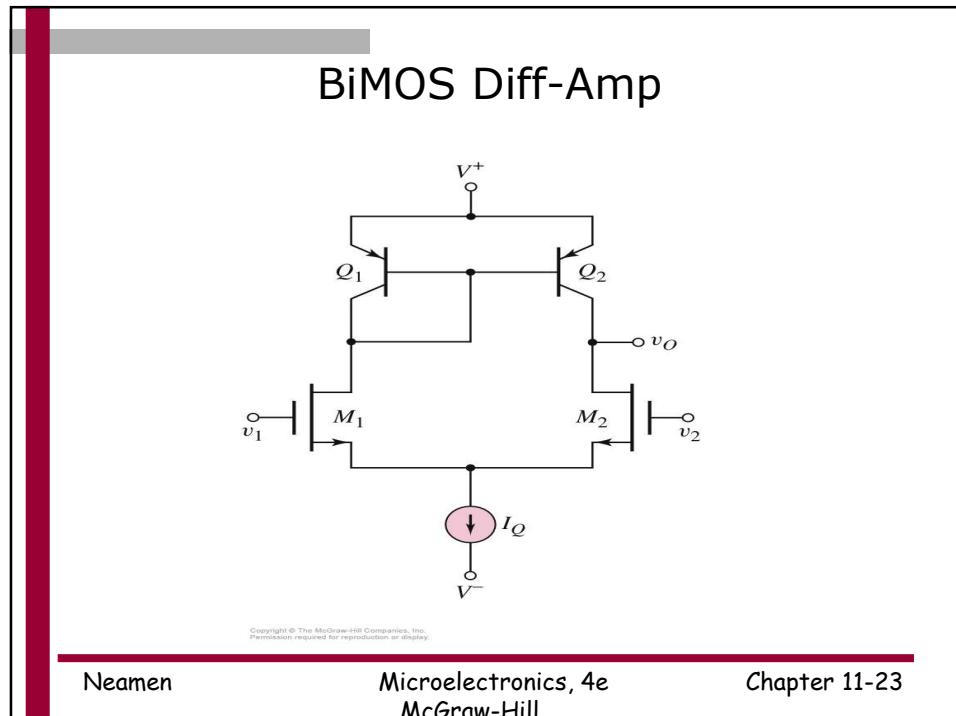

## BJT Op-Amp

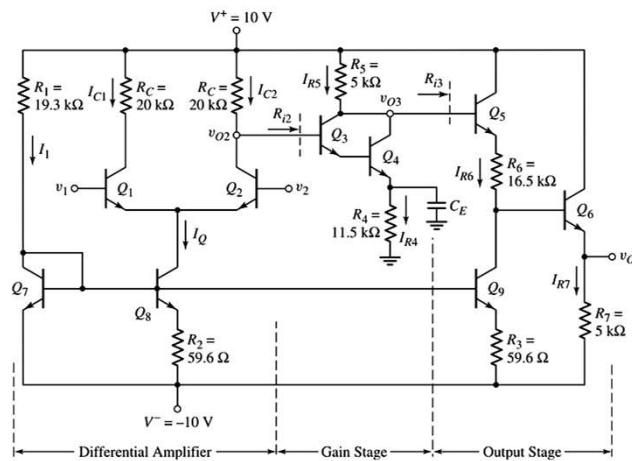


Neamen


Microelectronics, 4e  
McGraw-Hill

Chapter 11-25

## Frequency Response of Diff-Amp

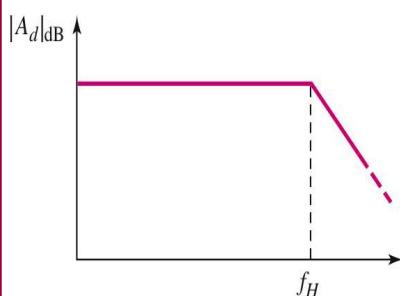

Differential-mode gain

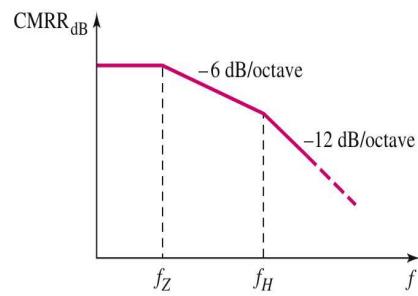



Common-mode rejection ratio (CMRR)

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-26
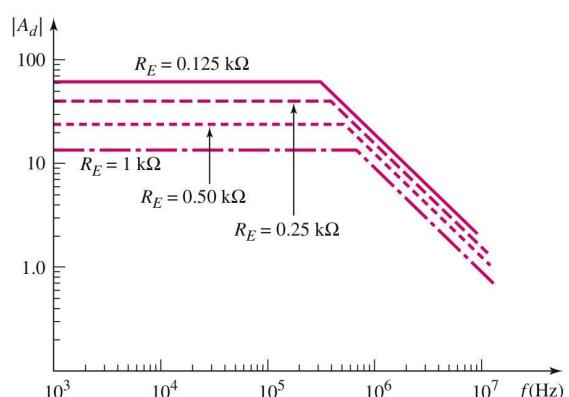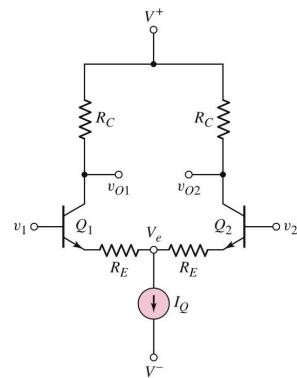
## BJT Diff-Amp with Emitter-Degeneration Resistors





Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-27
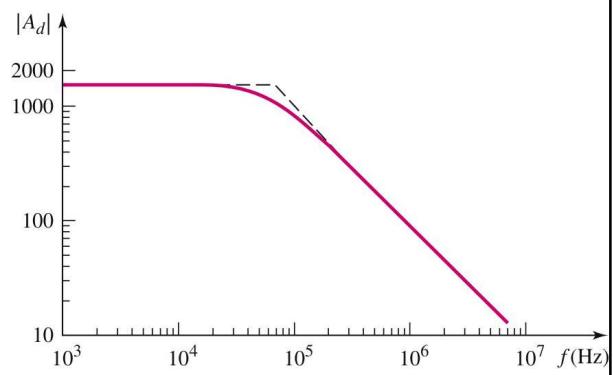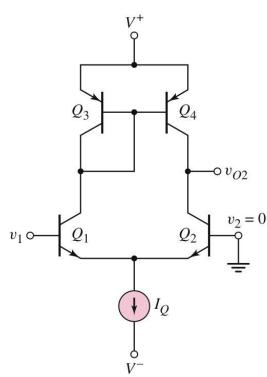
## BJT Diff-Amp with Active Load and Single-Sided Input



Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 11-28