

# Microelectronics Circuit Analysis and Design

Donald A. Neamen

## Chapter 4

### *Basic FET Amplifiers*

---

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-1

In this chapter, we will:



- ❑ Investigate a single-transistor circuit that can amplify a small, time-varying input signal
  - Develop small-signal models that are used in the analysis of linear amplifiers.
- ❑ Discuss and compare the three basic transistor amplifier configurations.
  - Analyze the common-source amplifier.
  - Analyze the source-follower amplifier.
  - Analyze the common-gate amplifier.
- ❑ Analyze multitransistor or multistage amplifiers.
- ❑ Develop the small-signal model of JFET devices and analyze basic JFET amplifiers.
- ❑ Design a two-stage MOSFET amplifier circuit.

---



Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-2

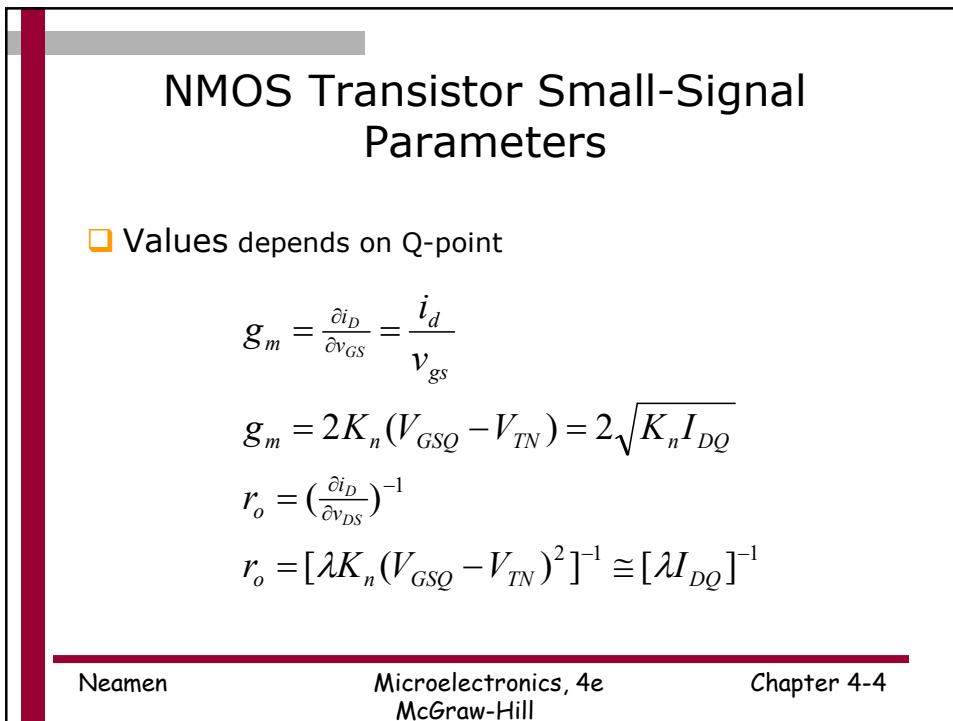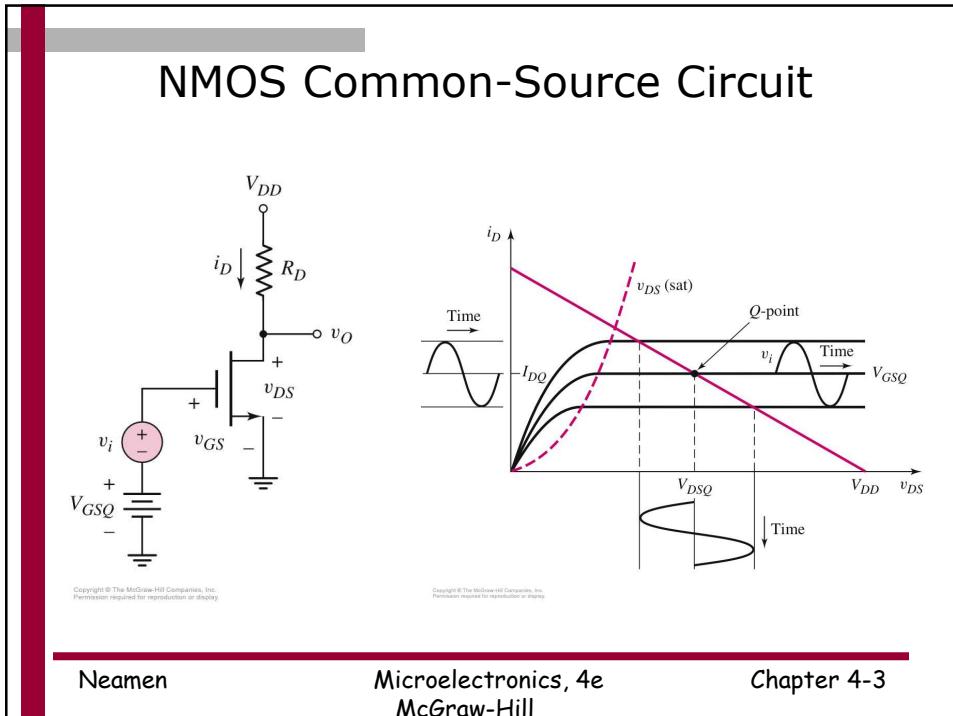
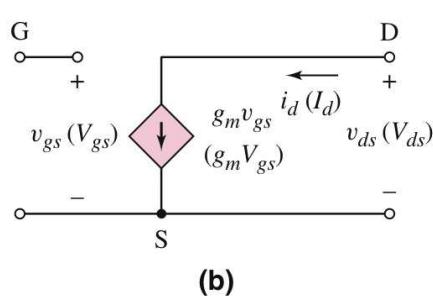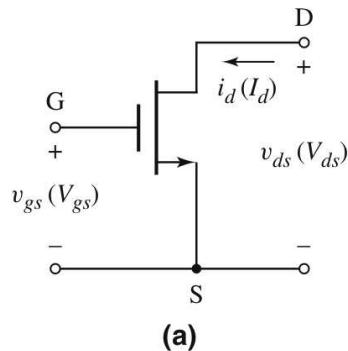
## Simple NMOS Small-Signal Equivalent Circuit





Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-5

## NMOS Common-Source Circuit

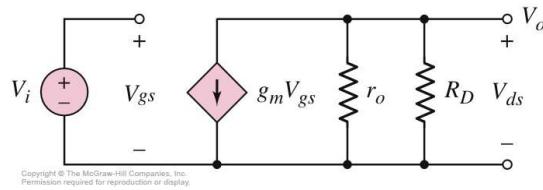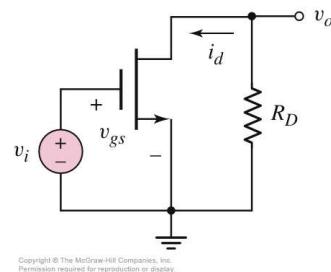

$$A_v = V_o / V_i = -g_m (r_o \parallel R_D)$$

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-6

## Problem-Solving Technique: MOSFET AC Analysis


1. Analyze circuit with only the dc sources to find quiescent solution. Transistor must be biased in saturation region for linear amplifier.
2. Replace elements with small-signal model.
3. Analyze small-signal equivalent circuit, setting dc sources to zero, to produce the circuit to the time-varying input signals only.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-7

## Modeling the Body Effects

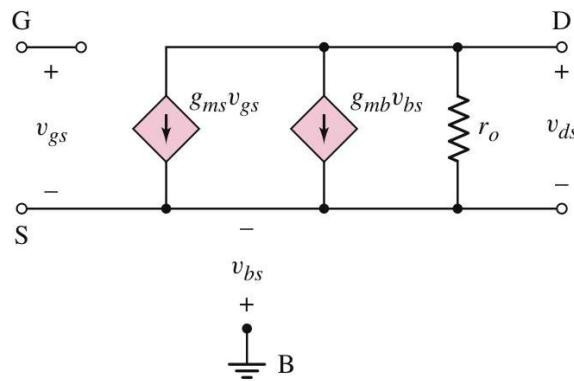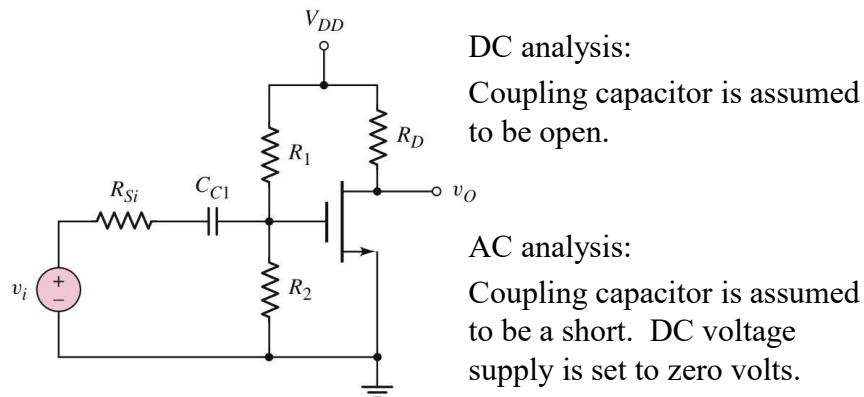

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-8

## Common-Source Configuration

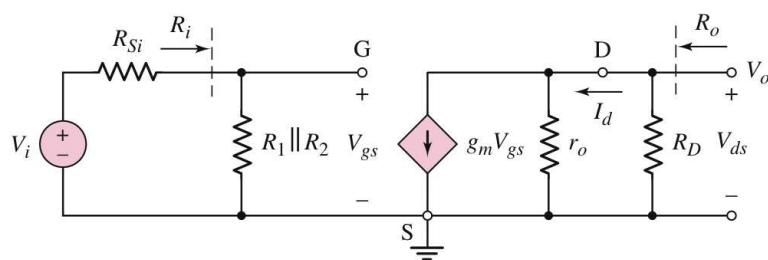

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-9

## Small-Signal Equivalent Circuit


Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.


$$A_v = V_o / V_i = -g_m (r_o \parallel R_D) \left( \frac{R_i}{R_i + R_{Si}} \right)$$

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-10

## DC Load Line

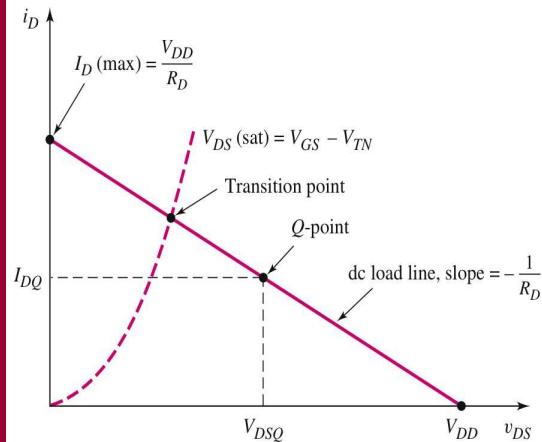

Q-point near the middle  
of the saturation region  
for maximum symmetrical  
output voltage swing.,.


Small AC input signal for  
output response to be  
linear.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-11

## Common-Source Amplifier with Source Resistor

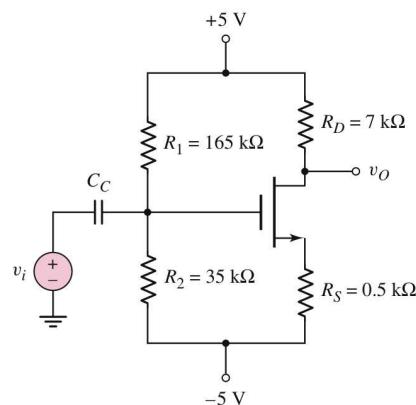
Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-12
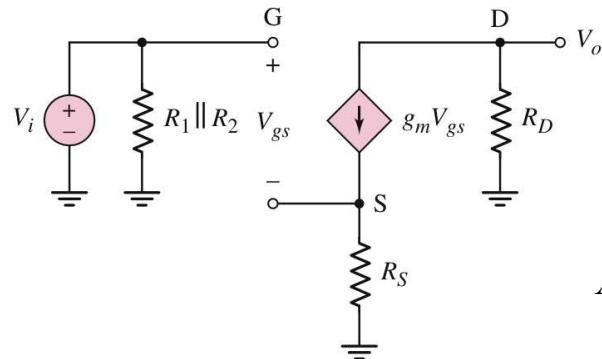
## Small-Signal Equivalent Circuit for Common-Source with Source Resistor



$$A_v = \frac{-g_m R_D}{1 + g_m R_S}$$


Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen


Microelectronics, 4e  
McGraw-Hill

Chapter 4-13
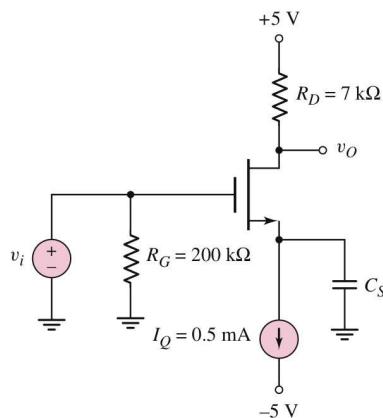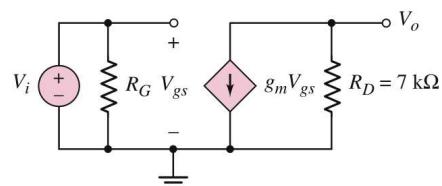
## Common-Source Amplifier with Bypass Capacitor



Small-signal equivalent circuit

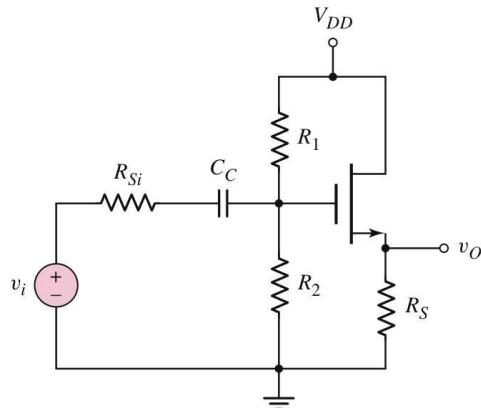

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-14

## NMOS Source-Follower or Common Drain Amplifier




Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-15
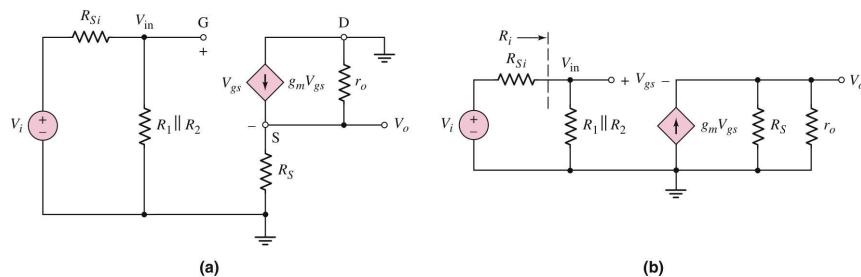
## Small-Signal Equivalent Circuit for Source Follower



Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.


$$A_v = \frac{R_s \| r_o}{\frac{1}{g_m} + R_s \| r_o} \left( \frac{R_i}{R_i + R_{Si}} \right)$$

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-16
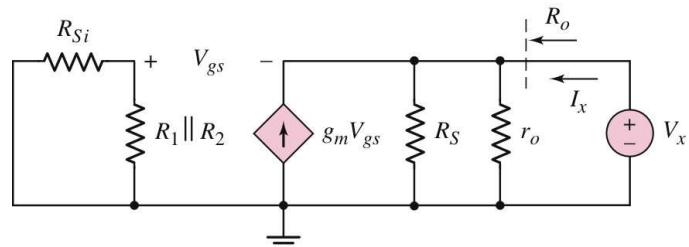
## Determining Output Impedance NMOS Source Follower




$$R_O = \frac{1}{g_m} \parallel R_S \parallel r_o$$

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-17

## Common-Gate Circuit

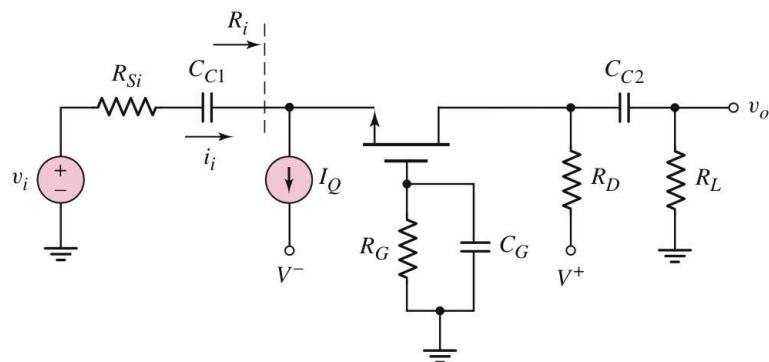


Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-18
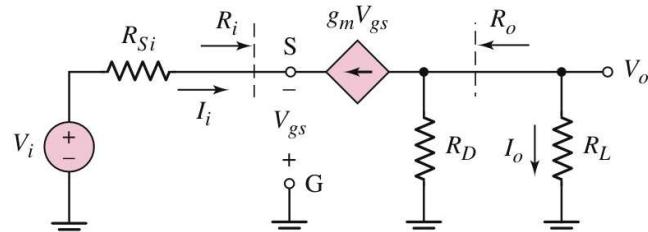
## Small-Signal Equivalent Circuit for Common Gate



Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

$$A_v = \frac{g_m (R_D \| R_L)}{1 + g_m R_{Si}} \quad A_i = \frac{I_o}{I_i} = \left( \frac{R_D}{R_D + R_L} \right) \left( \frac{g_m R_{Si}}{1 + g_m R_{Si}} \right)$$

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-19

## Comparison of 3 Basic Amplifiers



Configuration	Voltage Gain	Current Gain	Input Resistance	Output Resistance
Common Source	$A_v > 1$	—	$R_{TH}$	Moderate to high
Source Follower	$A_v \approx 1$	—	$R_{TH}$	Low
Common Gate	$A_v > 1$	$A_i \approx 1$	Low	Moderate to high

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-20
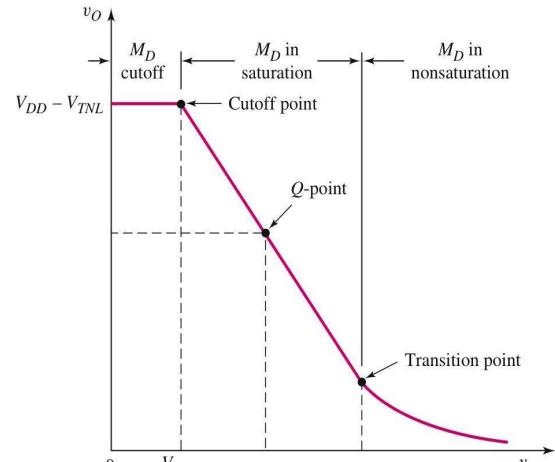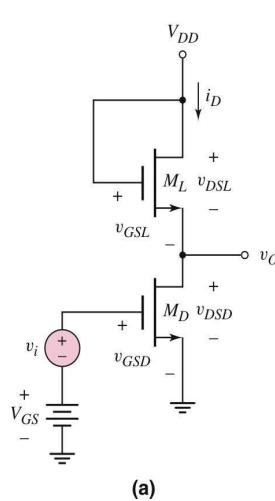
## NMOS Amplifier with Enhancement Load Device





Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-21
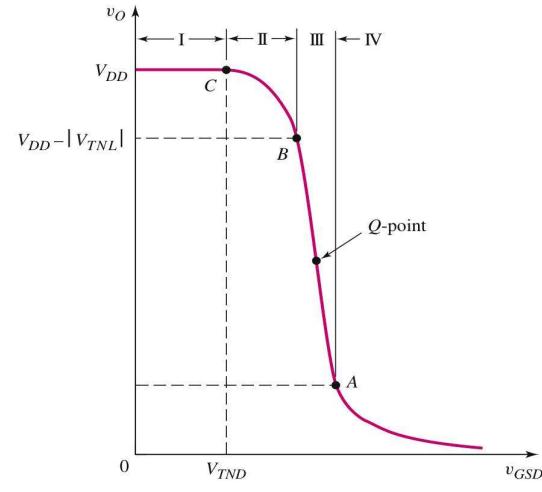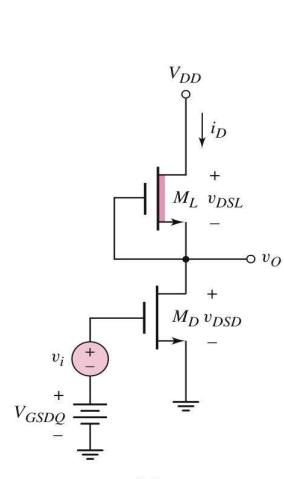
## NMOS Amplifier with Depletion Load Device





Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-22

## CMOS Common-Source Amplifier

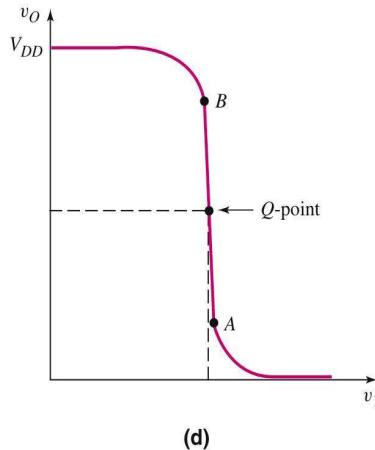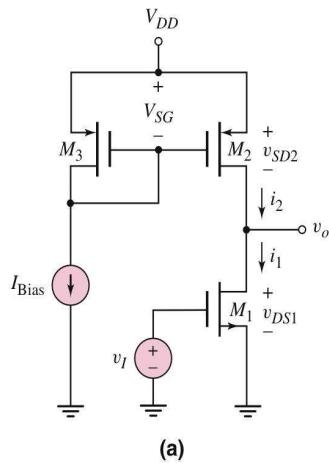


Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-23

## Small-Signal Equivalent Circuit for CMOS Common Source


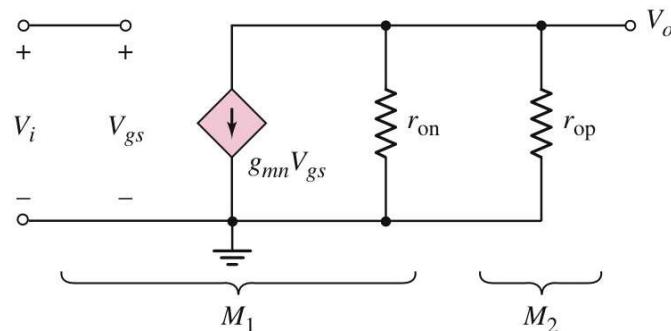
Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

$$A_v = -g_{mn} (r_{on} \parallel r_{op})$$


Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-24

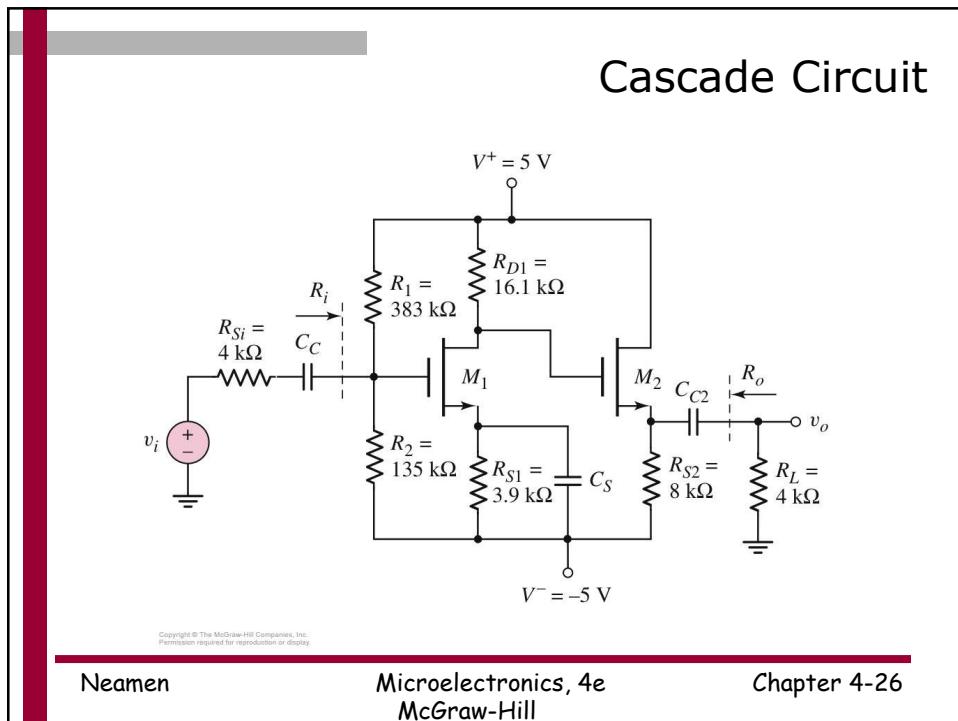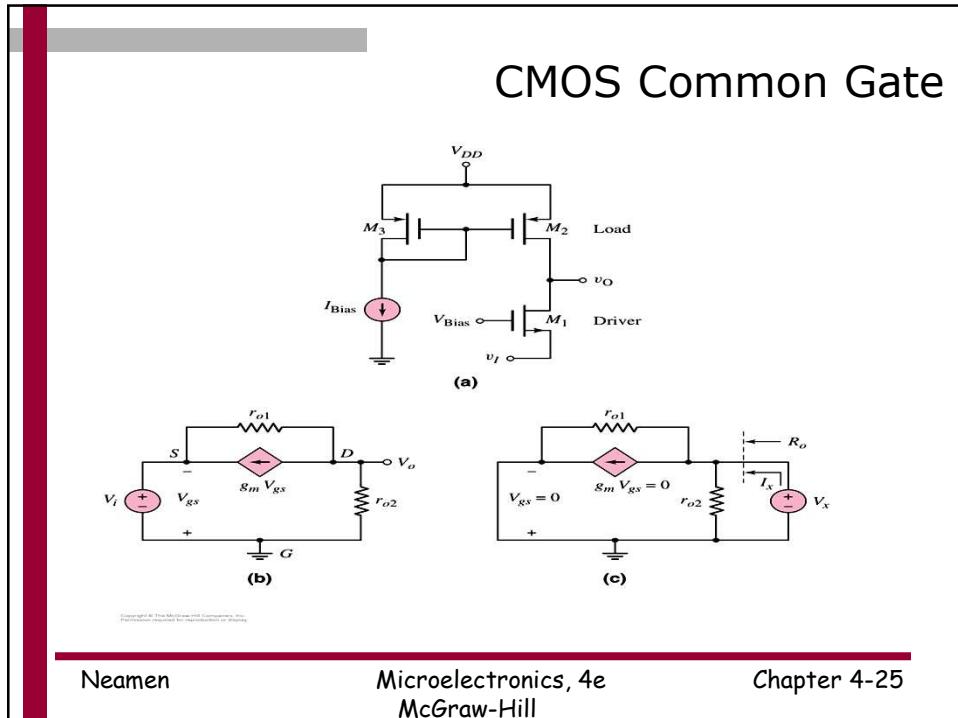
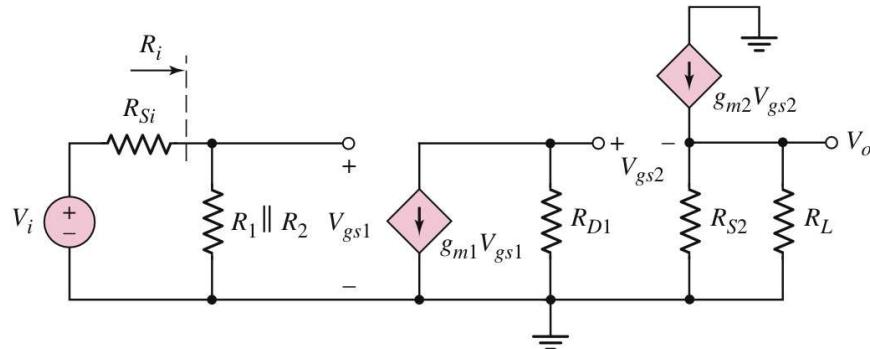
## Small-Signal Equivalent Circuit for Cascade Circuit




Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-27
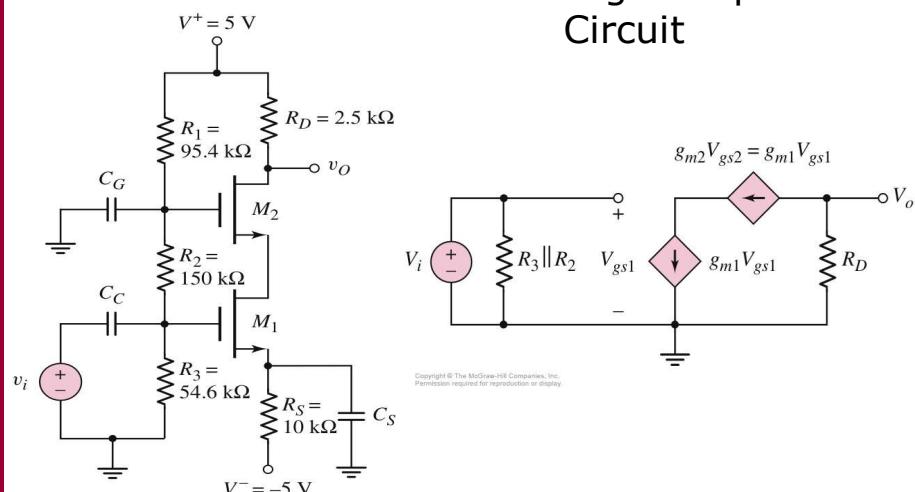
## Cascode Circuit with Small-Signal Equivalent Circuit





Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-28
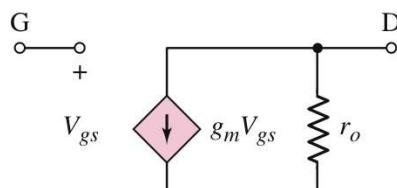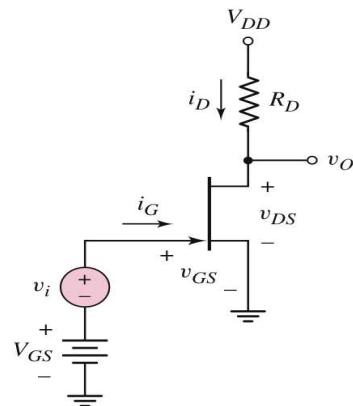
## JFET Common-Source Amplifier with Small-Signal Equivalent Circuit



Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Neamen

Microelectronics, 4e  
McGraw-Hill

Chapter 4-29