

Microelectronics Circuit Analysis and Design

Donald A. Neamen

Chapter 5

The Bipolar Junction Transistor

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-1

In this chapter, we will:


- ❑ Discuss the physical structure and operation of the bipolar junction transistor.
- ❑ Understand the dc analysis and design techniques of bipolar transistor circuits.
- ❑ Examine three basic applications of bipolar transistor circuits.
- ❑ Investigate various dc biasing schemes of bipolar transistor circuits, including integrated circuit biasing.
- ❑ Consider the dc biasing of multistage or multi-transistor circuits.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-2

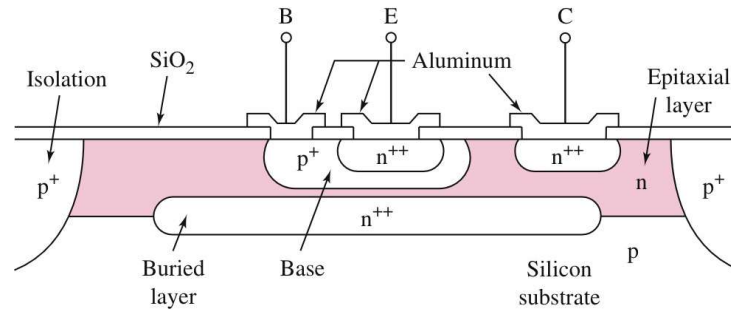Cross Section of Integrated Circuit npn Transistor



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-3

Modes of Operation


- Forward-Active
 - B-E junction is forward biased
 - B-C junction is reverse biased
- Saturation
 - B-E and B-C junctions are forward biased
- Cut-Off
 - B-E and B-C junctions are reverse biased
- Inverse-Active (or Reverse-Active)
 - B-E junction is reverse biased
 - B-C junction is forward biased

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-4

npn BJT in Forward-Active

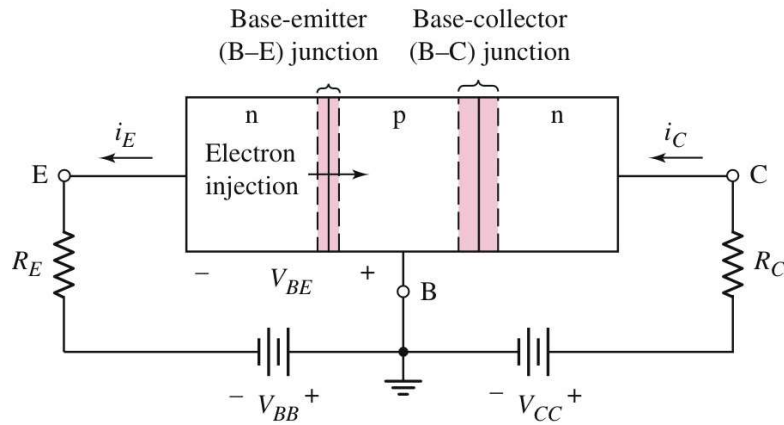


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-5

Electrons and Holes in npn BJT

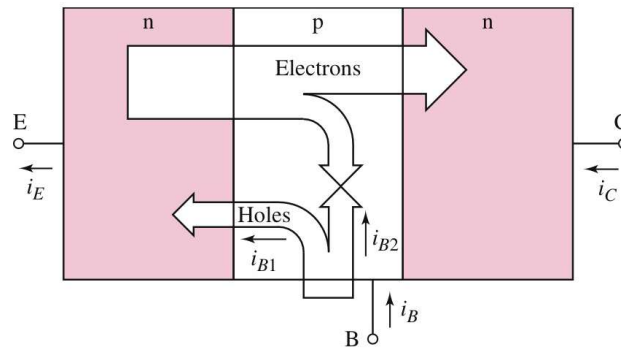


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-6

Electrons and Holes in pnp BJT

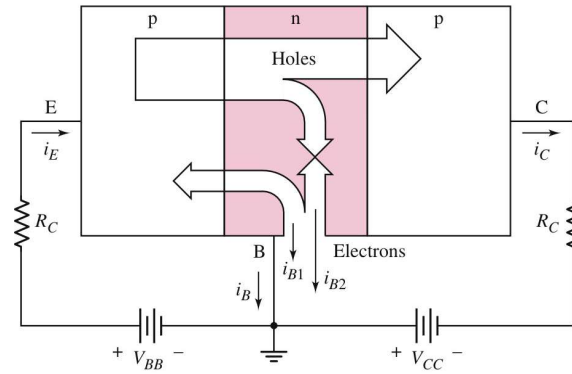


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-7

Circuit Symbols and Current Conventions

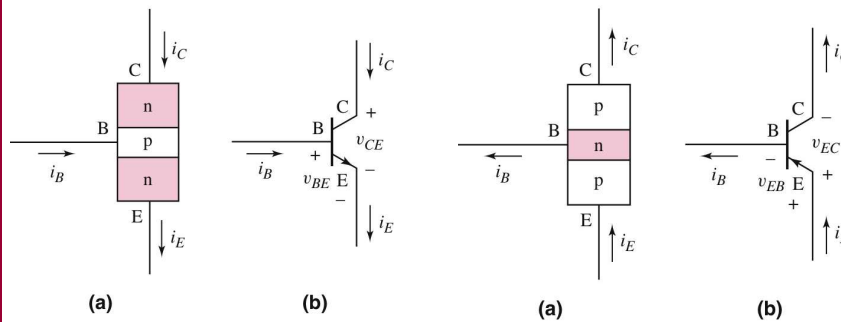

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-8

Current Relationships

$$i_E = i_C + i_B$$

$$i_C = \beta i_B$$

$$i_E = (1 + \beta) i_B$$

$$i_C = \alpha i_E$$


$$\beta = \frac{\alpha}{1 - \alpha}$$

Neamen


Microelectronics, 4e
McGraw-Hill

Chapter 5-9


Common-Emitter Configurations

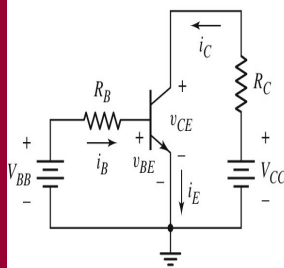

(a)

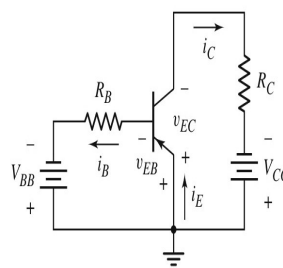

(b)

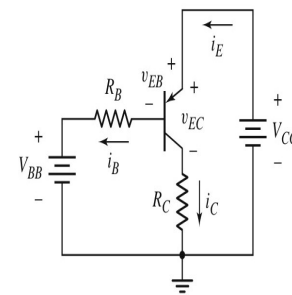

(c)


Copyright © The McGraw-Hill Companies, Inc.
Permissions required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-10

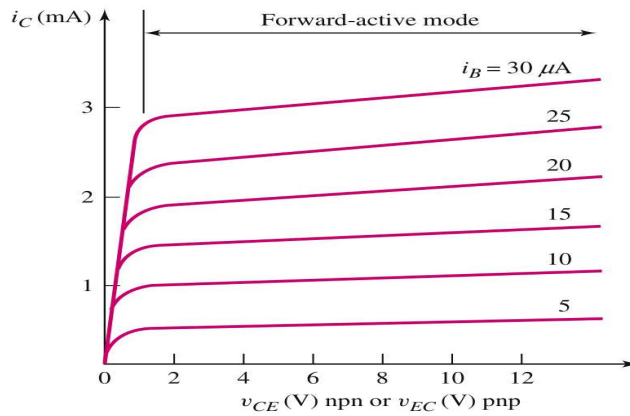Current-Voltage Characteristics of a Common-Emitter Circuit




Copyright © The McGraw-Hill Companies, Inc. Permission is required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-11

Early Voltage/Finite Output Resistance

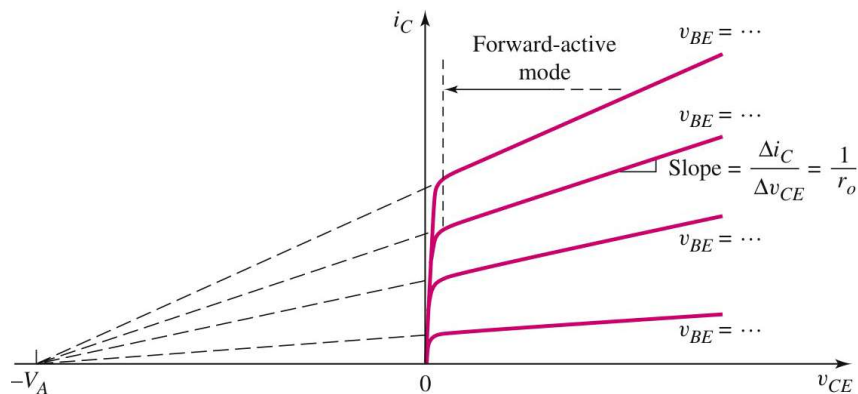


Copyright © The McGraw-Hill Companies, Inc. Permission is required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-12

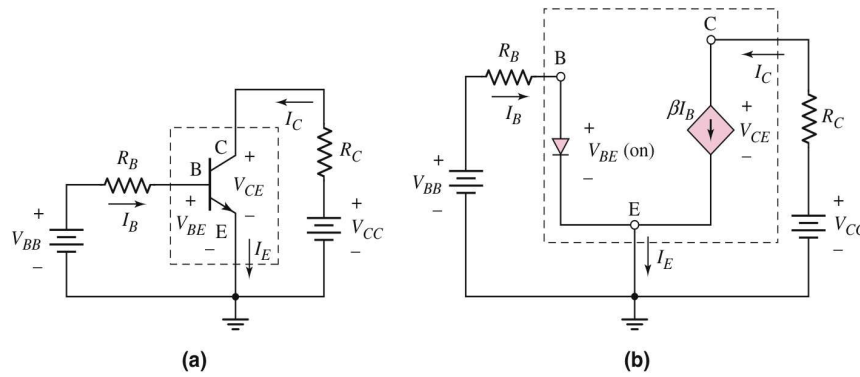DC Equivalent Circuit for npn Common Emitter




Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-13

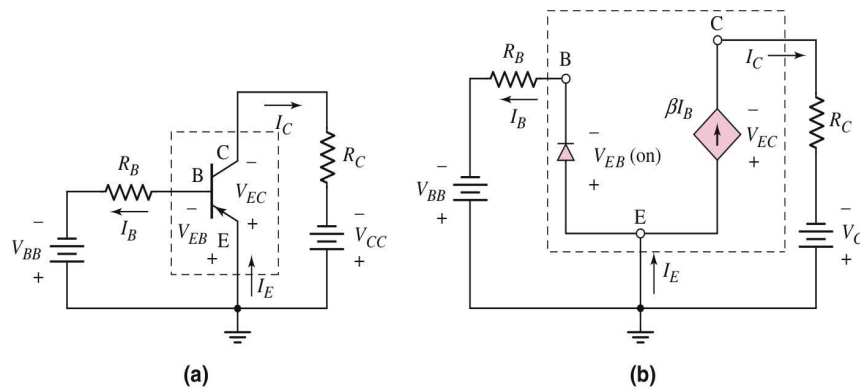DC Equivalent Circuit for pnp Common Emitter




Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-14

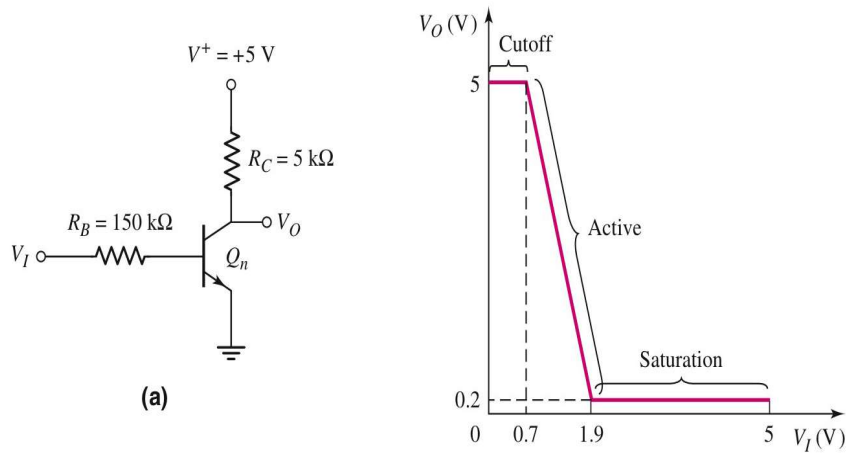Voltage Transfer Characteristic for npn Circuit




Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-17

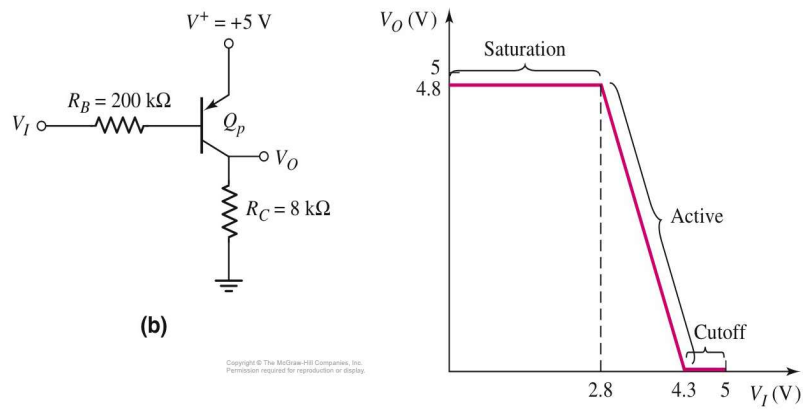Voltage Transfer Characteristic for pnp Circuit




Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-18

Digital Logic

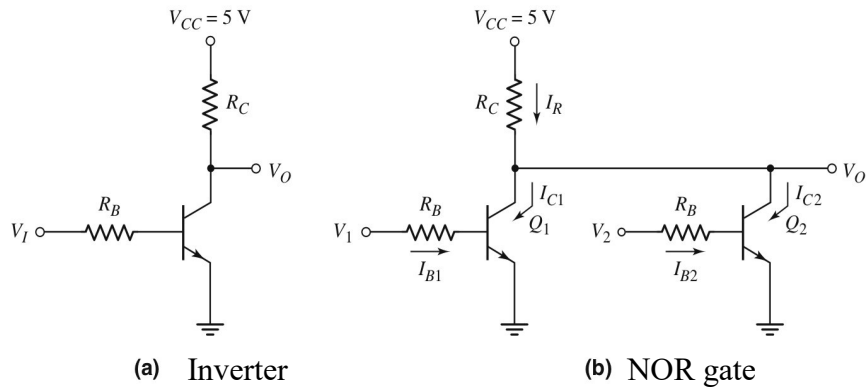


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-19

Bipolar Inverter as Amplifier

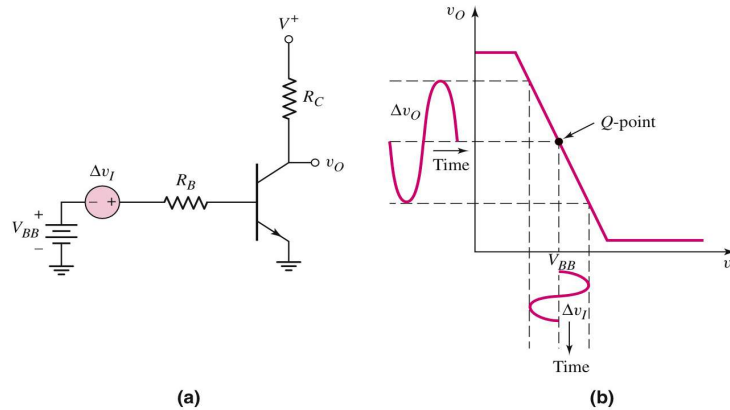


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-20

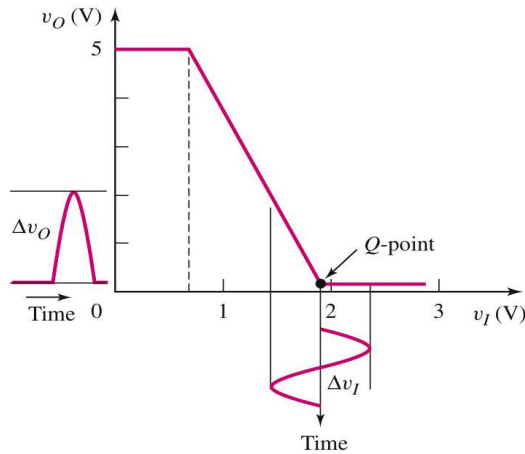Effect of Improper Biasing on Amplified Signal Waveform




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-21

Single Base Resistor Biasing

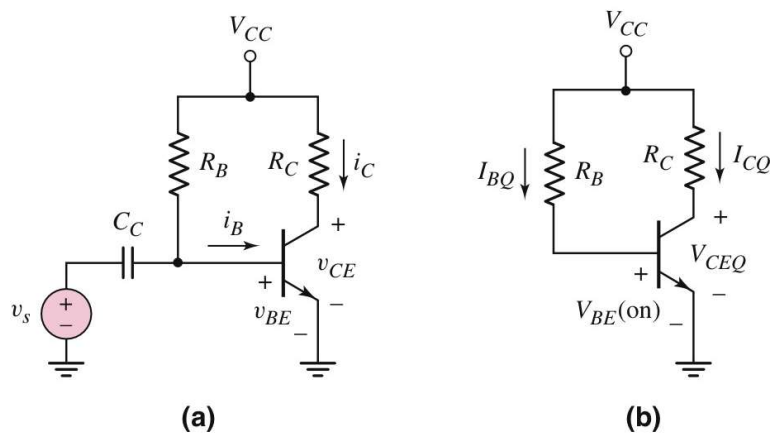


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen


Microelectronics, 4e
McGraw-Hill

Chapter 5-22

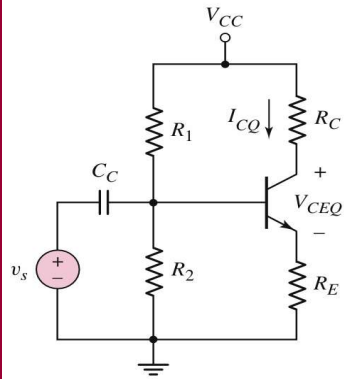Common Emitter with Voltage Divider Biasing and Emitter Resistor



(a)

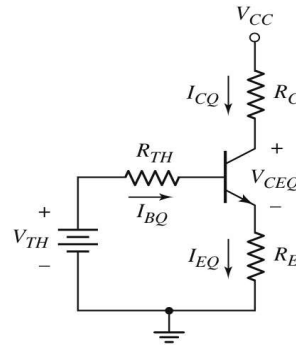

(b) $V_{TH} = [R_2 / (R_1 + R_2)] V_{CC}$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-23

Integrated Circuit Biasing
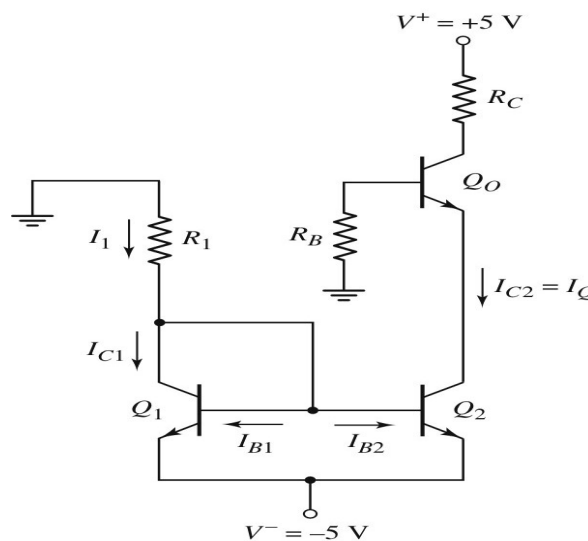
$$I_C = I_Q = \frac{I_1}{1 + \frac{2}{\beta}}$$




Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-24

Multistage Cascade Transistor Circuit

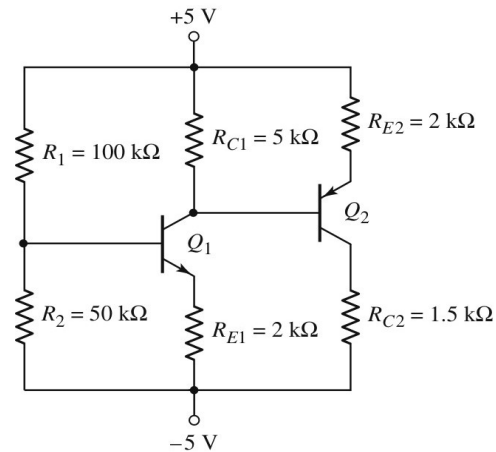


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-25

Multistage Cascode Transistor Circuit

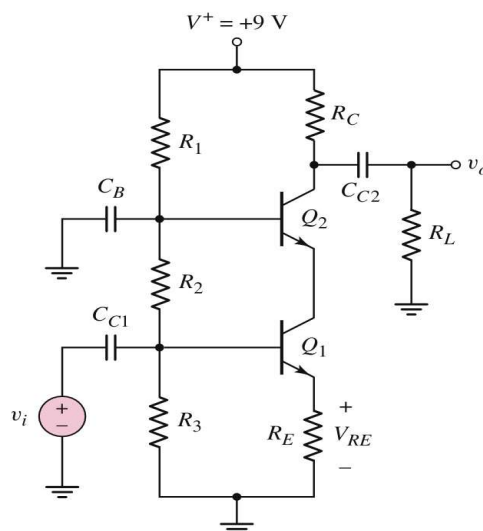

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 5-26