

Microelectronics Circuit Analysis and Design

Donald A. Neamen

Chapter 6

Basic BJT Amplifiers

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-1

In this chapter, we will:



- ❑ Understand the concept of an analog signal and the principle of a linear amplifier.
 - Investigate how a transistor circuit can amplify a small, time-varying input signal.
- ❑ Discuss and compare the three basic transistor amplifier configurations.
 - Analyze the common-emitter amplifier.
 - Understand the ac load line & determine the maximum symmetrical swing of the output.
 - Analyze the emitter-follower amplifier.
 - Analyze the common-base amplifier.
- ❑ Analyze multitransistor or multistage amplifiers.
- ❑ Understand the concept of signal power gain in an amplifier

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-2

Common Emitter with Time-Varying Input

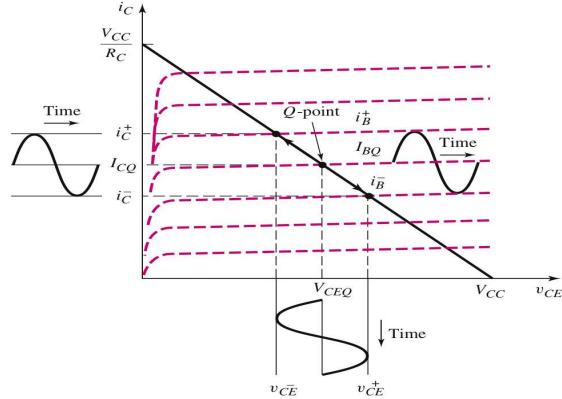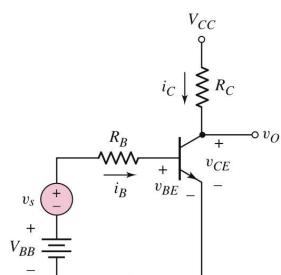


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-3

I_B Versus V_{BE} Characteristic
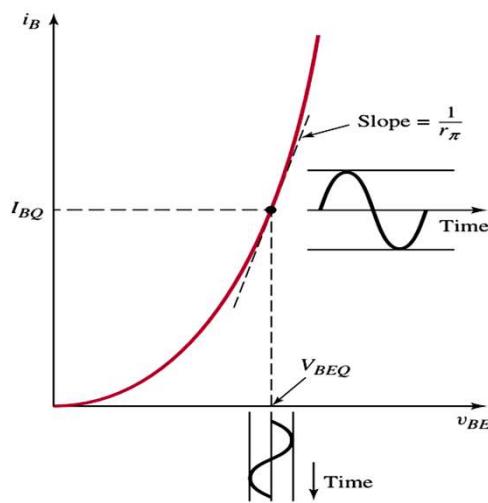
$$i_B \cong I_{BQ} \left(1 + \frac{v_{be}}{V_T} \right) = I_B + i_b$$




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-4

ac Equivalent Circuit for Common Emitter

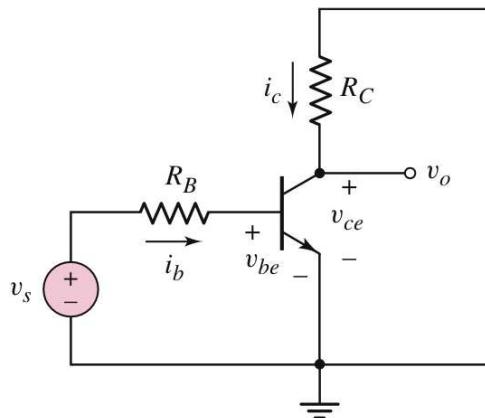


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-5

Small-Signal Hybrid π Model for npn BJT

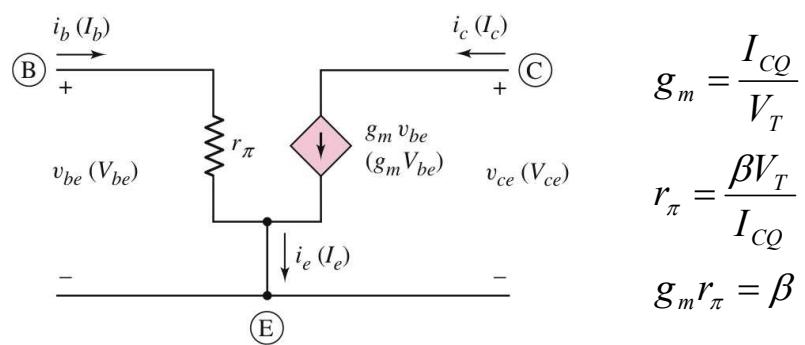

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.


Phasor signals are shown in parentheses.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-6

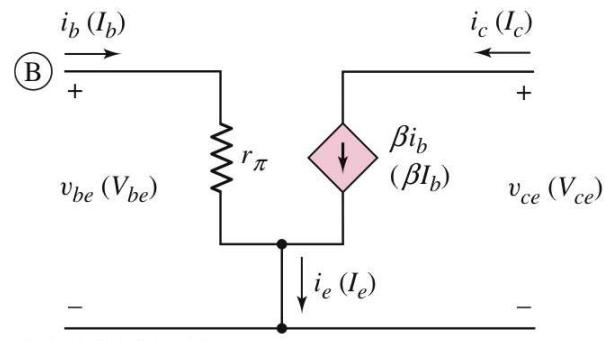Small-Signal Equivalent Circuit Using Common-Emitter Current Gain




Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-7

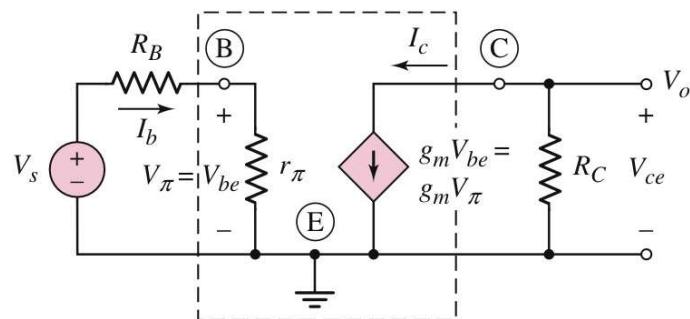Small-Signal Equivalent Circuit for npn Common Emitter circuit



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$A_v = -(g_m R_C) \left(\frac{r_\pi}{r_\pi + R_B} \right)$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-8

Problem-Solving Technique: BJT AC Analysis

1. Analyze circuit with only dc sources to find Q point.
2. Replace each element in circuit with small-signal model, including the hybrid π model for the transistor.
3. Analyze the small-signal equivalent circuit after setting dc source components to zero.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-9

Transformation of Elements


| Element | DC Model | AC Model |
|-------------------------------------|--|-----------------|
| Resistor | R | R |
| Capacitor | Open | C |
| Inductor | Short | L |
| Diode | $+V_g, r_f -$  | $r_d = V_T/I_D$ |
| Independent Constant Voltage Source | $+ V_s -$  | Short |
| Independent Constant Current Source | I_s  | Open |

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-10

Hybrid π Model for npn with Early Effect

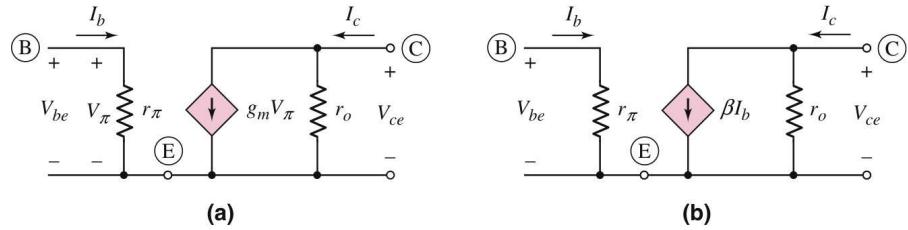

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.


$$r_o = \frac{V_A}{I_{CQ}}$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-11

Hybrid π Model for pnp with Early Effect

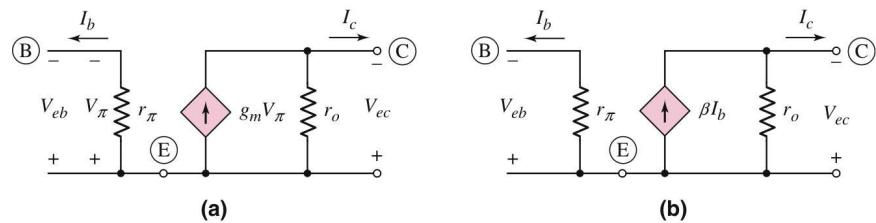


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-12

Expanded Hybrid π Model for npn

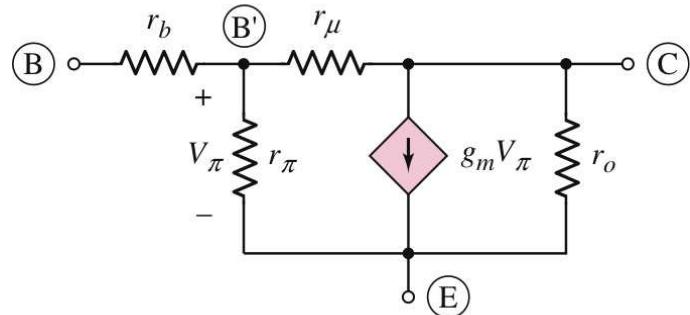



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-13

h-Parameter Model for npn

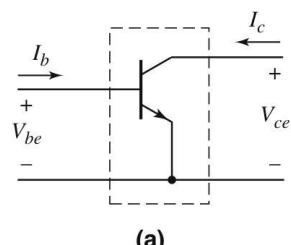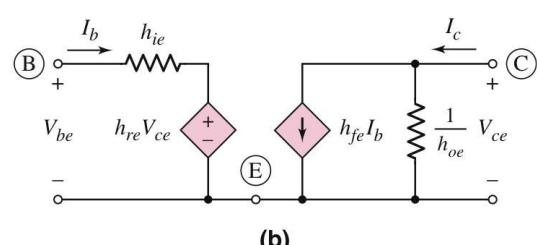(a)
Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$h_{ie} = r_b + r_\pi \parallel r_\mu$$

$$h_{fe} = \beta$$

$$h_{re} \cong \frac{r_\pi}{r_\mu}$$

$$h_{oe} = \frac{1+\beta}{r_\mu} + \frac{1}{r_o}$$


Neamen

Microelectronics, 4e
McGraw-Hill


Chapter 6-14

4 Equivalent 2-port Networks

Voltage Amplifier

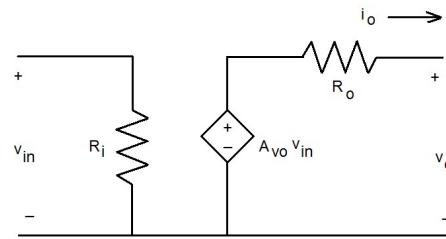

Current Amplifier

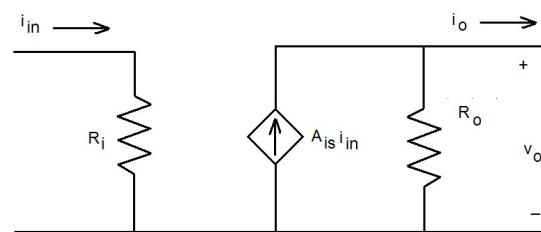


Neamen

Microelectronics, 4e
McGraw-Hill


Chapter 6-15

4 Equivalent 2-port Networks

Transconductance Amplifier

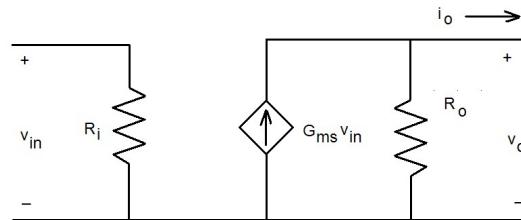

Transresistance Amplifier

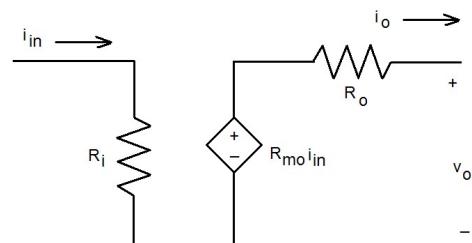


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-16

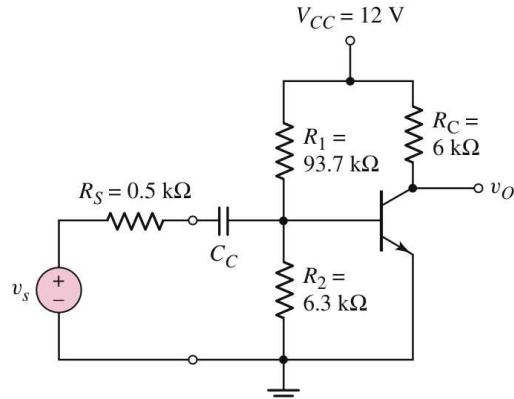Common Emitter with Voltage-Divider Bias and a Coupling Capacitor




Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-17

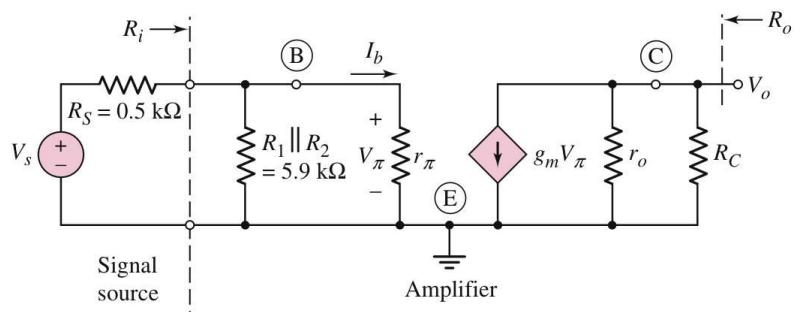Small-Signal Equivalent Circuit – Coupling Capacitor Assumed a Short




Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-18

npn Common Emitter with Emitter Resistor

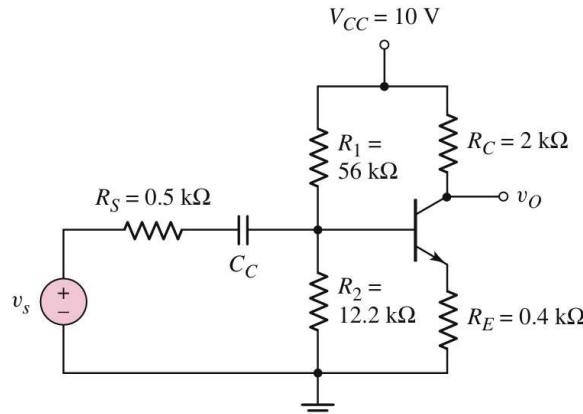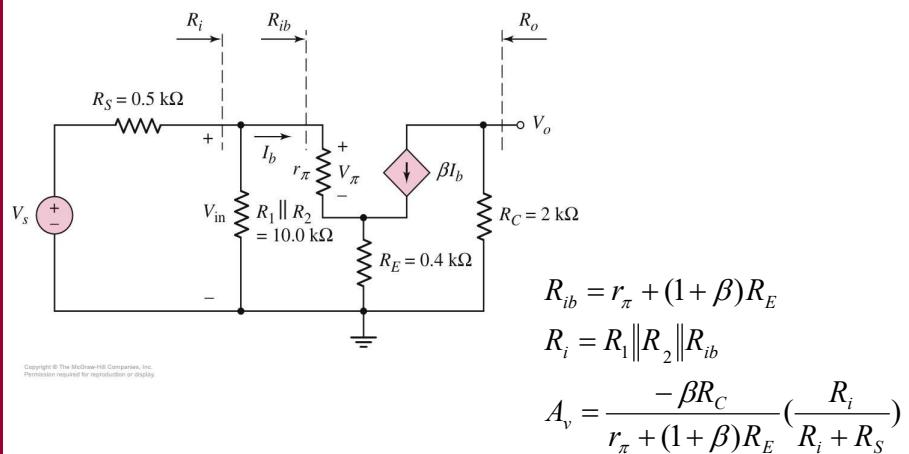

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-19

Small-Signal Equivalent Circuit: Common Emitter with R_E




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-20

R_E and Emitter Bypass Capacitor

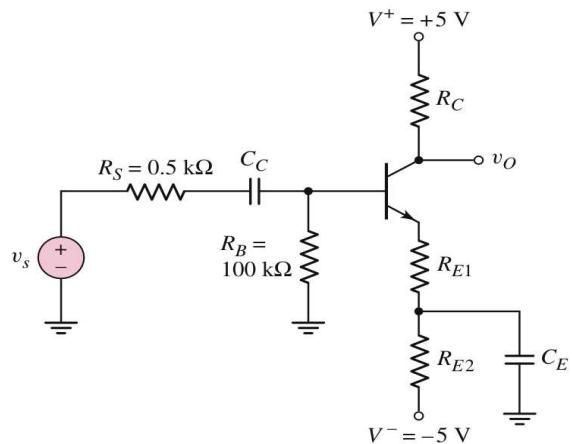


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-21

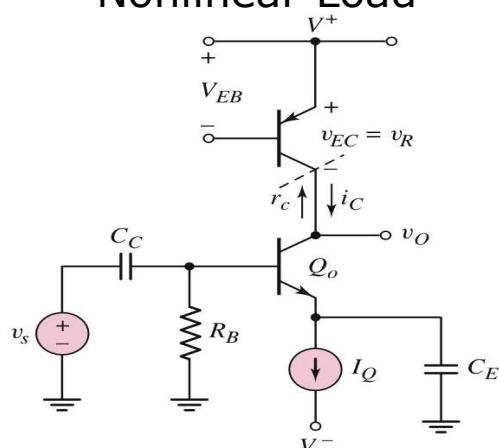Current Source Biasing and Nonlinear Load




(c)

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-22

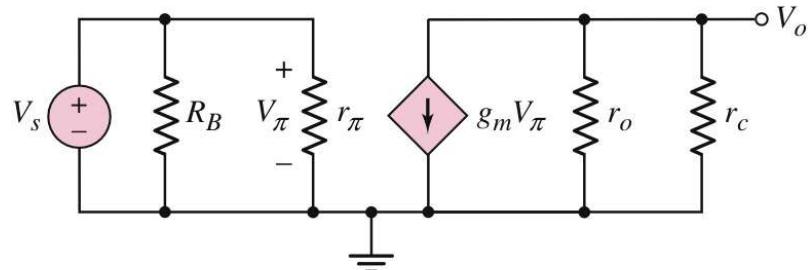Small-Signal Equivalent Circuit with Current Biasing and Nonlinear Load



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.


$$A_v = -g_m (r_o \parallel r_c)$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-23

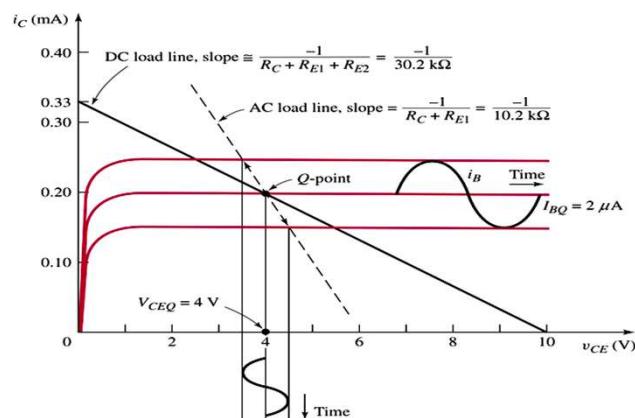dc AND ac Load Lines: R_E and Emitter Bypass Capacitor



Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-24

Problem-Solving Technique: Maximum Symmetrical Swing


1. Write dc load line equation that relates I_{CQ} and V_{CEQ} .
2. Write ac load line equations that relates i_c and v_{ce}
3. In general, $i_c = I_{CQ} - I_C(\min)$, where $I_C(\min)$ is zero or other minimum collector current.
4. In general, $v_{ce} = V_{CEQ} - V_{CE}(\min)$, where $V_{CE}(\min)$ is some specified minimum collector-emitter voltage.
5. Combine above 4 equations to find optimum I_{CQ} and V_{CEQ} .

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-25

Common-Collector or Emitter-Follower Amplifier

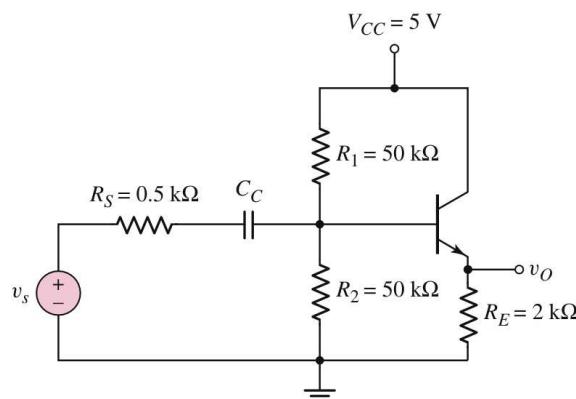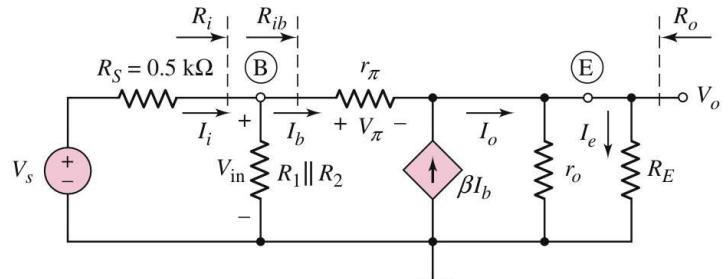

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-26

Small-Signal Equivalent Circuit: Emitter Follower



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$R_{ib} = r_\pi + (1 + \beta)(r_o \| R_E)$$

$$R_i = R_1 \| R_2 \| R_{ib}$$


$$A_v = \frac{(1 + \beta)(r_o \| R_E)}{r_\pi + (1 + \beta)(r_o \| R_E)} \left(\frac{R_i}{R_i + R_S} \right)$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-27

Output Resistance: Emitter Follower

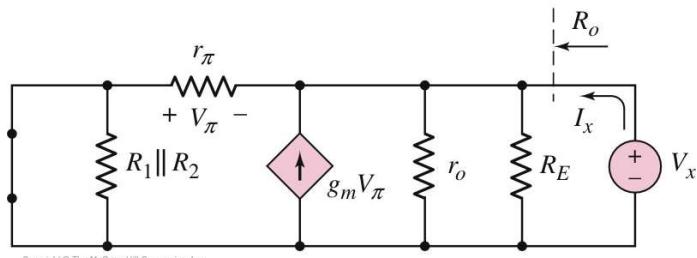

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.


$$R_o = \frac{r_\pi}{1 + \beta} \| R_E \| r_o$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-28

Common-Base Amplifier

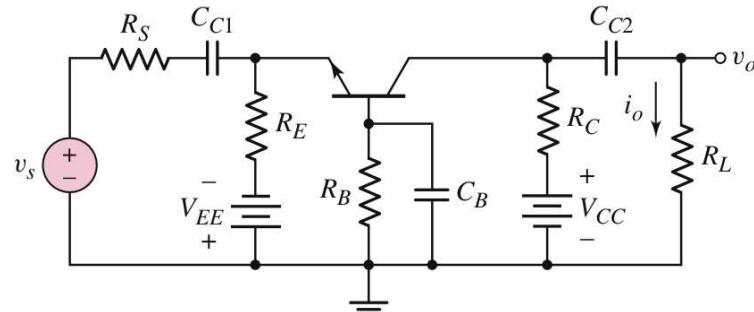


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen


Microelectronics, 4e
McGraw-Hill

Chapter 6-29

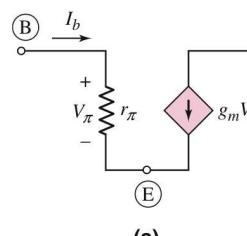Small-Signal Equivalent Circuit: Common Base



(a)

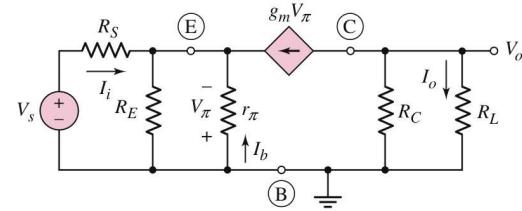

(b)

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$A_v = g_m (R_C \parallel R_L)$$


$$A_i = g_m \left(\frac{R_C}{R_C + R_L} \right) \left[\frac{r_\pi}{1 + \beta} \parallel R_E \right]$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-30

Input Resistance: Common Base

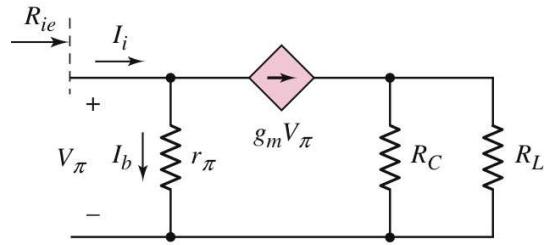


$$R_{ie} = r_\pi / (1 + \beta)$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-31

Output Resistance: Common Base

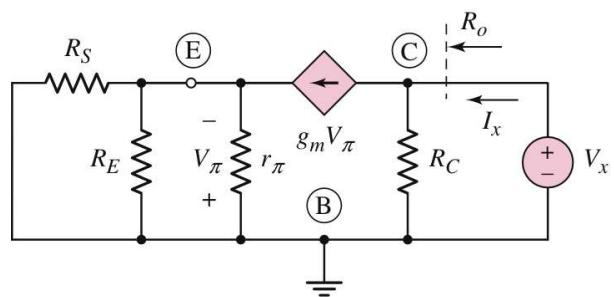


$$R_o = R_C$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-32

Common Emitter Cascade Amplifier

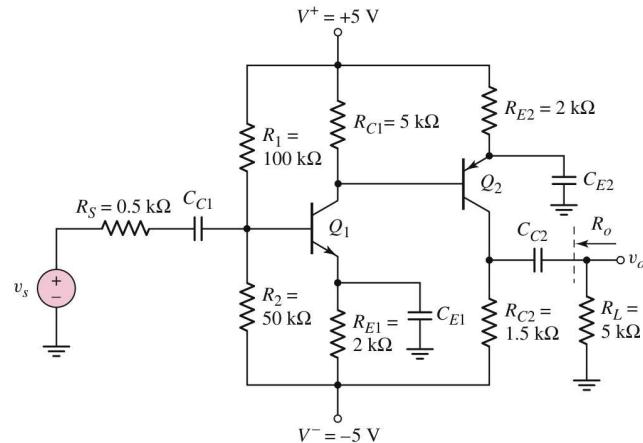


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-33

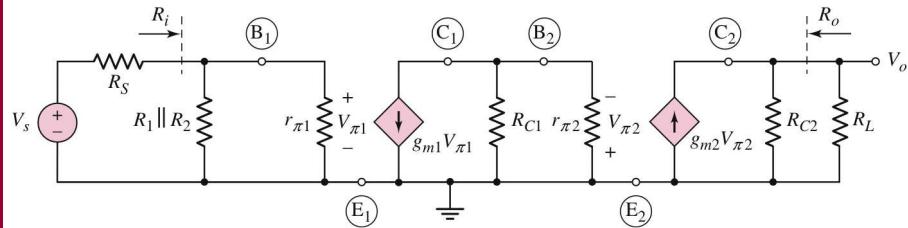Small-Signal Equivalent Circuit: Cascade Amplifier




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-34

Darlington Pair

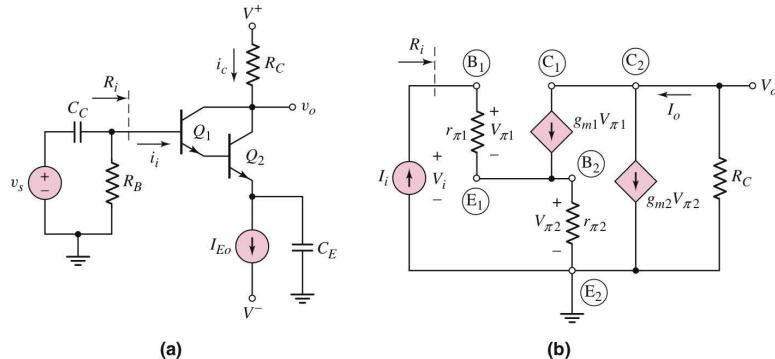


$$A_i \equiv \beta_1 \beta_2$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-35

Cascode Amplifier

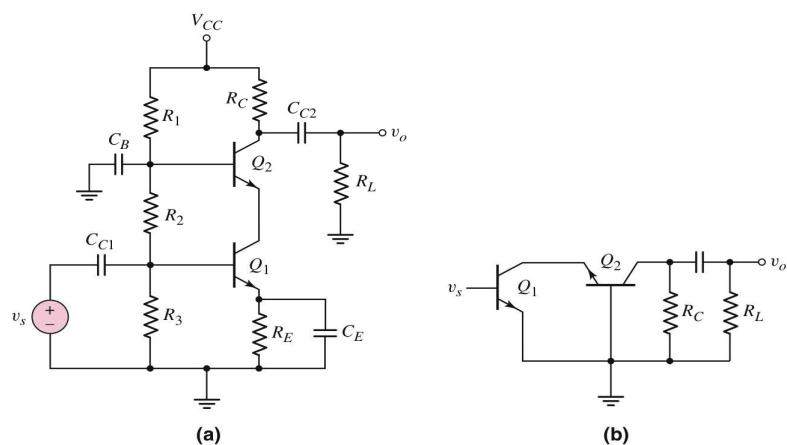


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 6-36

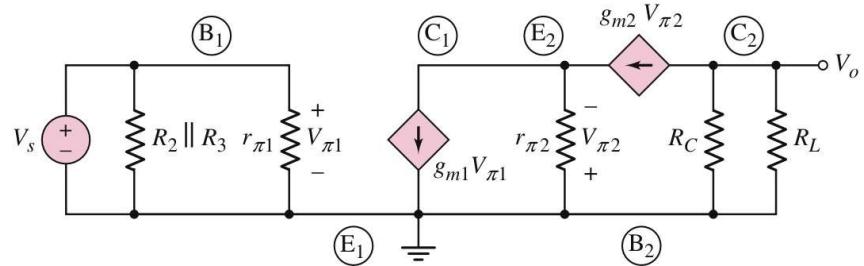Small-Signal Equivalent Circuit: Cascode Amplifier



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$A_v \cong -g_{m1}(R_C \| R_L)$$