

Microelectronics Circuit Analysis and Design

Donald A. Neamen

Chapter 7

Frequency Response

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-1

In this chapter, we will:


- Discuss the general frequency response characteristics of amplifiers.
- Derive the system transfer functions
 - Develop the Bode diagrams of the magnitude and phase of the transfer functions.
- Analyze the frequency response of transistor circuits with capacitors.
 - Determine the Miller effect and Miller capacitance.
- Determine the high-frequency response of basic transistor circuit configurations.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-2

Amplifier Gain Versus Frequency

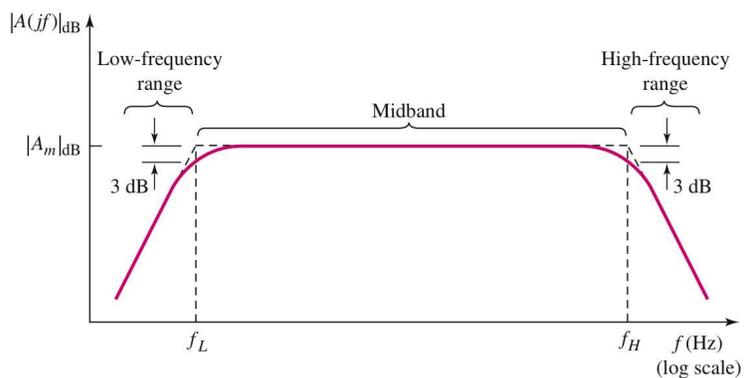

Copyright © The McGraw-Hill Companies, Inc.
Permission is required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-3

Transfer Functions of the Complex Frequency


Name of Function	Expression
Voltage Transfer Function	$T(s) = V_o(s)/V_i(s)$
Current Transfer Function	$I_o(s)/I_i(s)$
Transresistance Function	$V_o(s)/I_i(s)$
Transconductance Function	$I_o(s)/V_i(s)$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-4

Series Coupling Capacitor Circuit

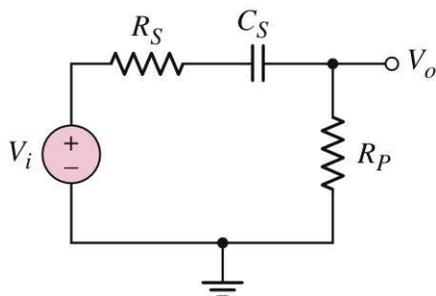

$$T(s) = K_2 \left(\frac{s\tau}{1 + s\tau} \right)$$

$$\tau = (R_S + R_P)C_S$$


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-5

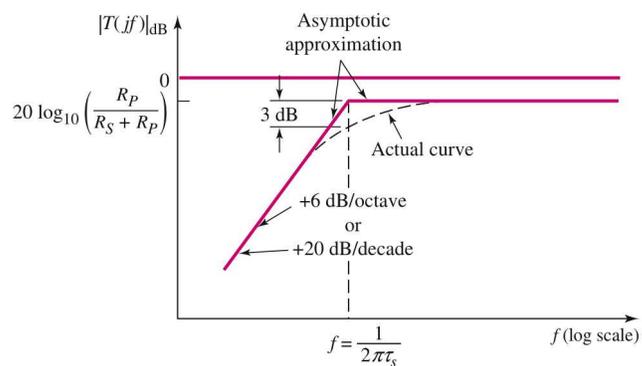Bode Plot of Voltage Transfer Function Magnitude: Series Coupling Capacitor Circuit




Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-6

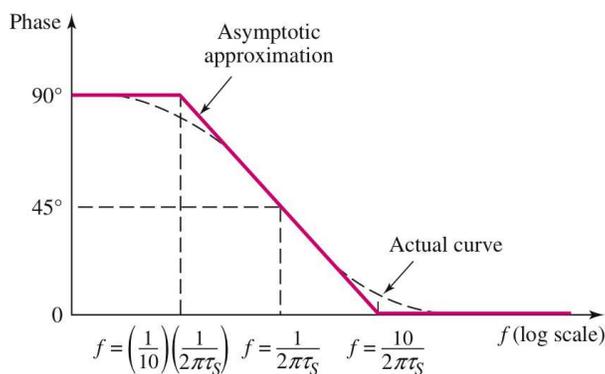Bode Plot of Voltage Transfer Function Phase: Series Coupling Capacitor Circuit




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-7

Parallel Load Capacitor Circuit

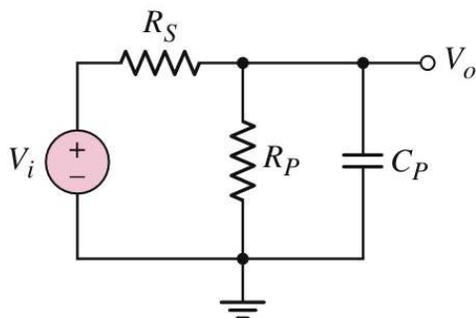

$$T(s) = K_1 \left(\frac{1}{1 + s\tau} \right)$$

$$\tau = (R_S \parallel R_P) C_P$$


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-8

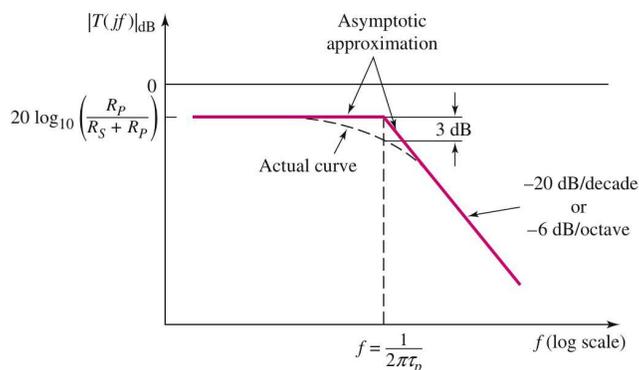Bode Plot of Voltage Transfer Function Magnitude: Parallel Load Capacitor Circuit




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-9

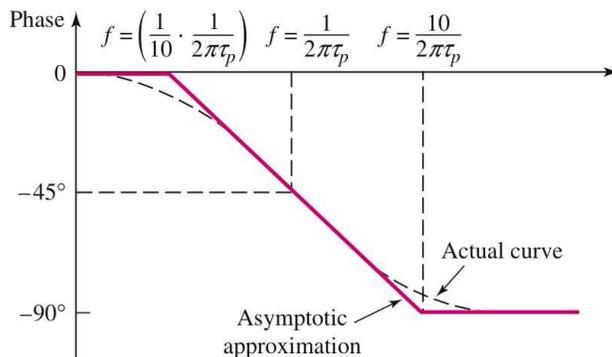Bode Plot of Voltage Transfer Function Phase: Parallel Load Capacitor Circuit




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-10

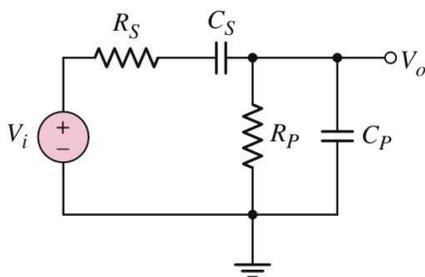Circuit with Series Coupling and Parallel Load Capacitor



Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

$$\tau_S = (R_S + R_P)C_S$$

$$\tau_P = (R_S \parallel R_P)C_P$$

$$f_L = \frac{1}{2\pi\tau_S}$$


$$f_H = \frac{1}{2\pi\tau_P}$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-11

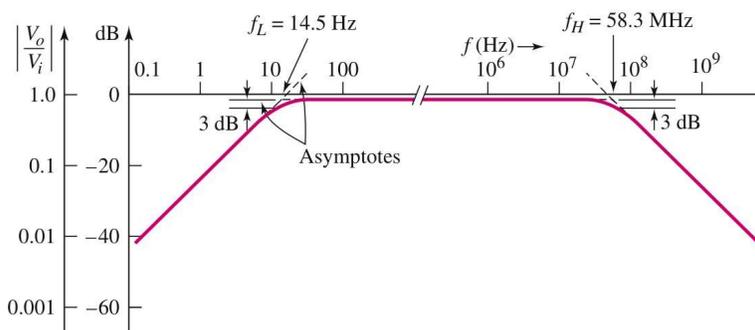Bode Plot of Magnitude of Voltage Transfer Function: Series Coupling and Parallel Load Capacitor





Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-12

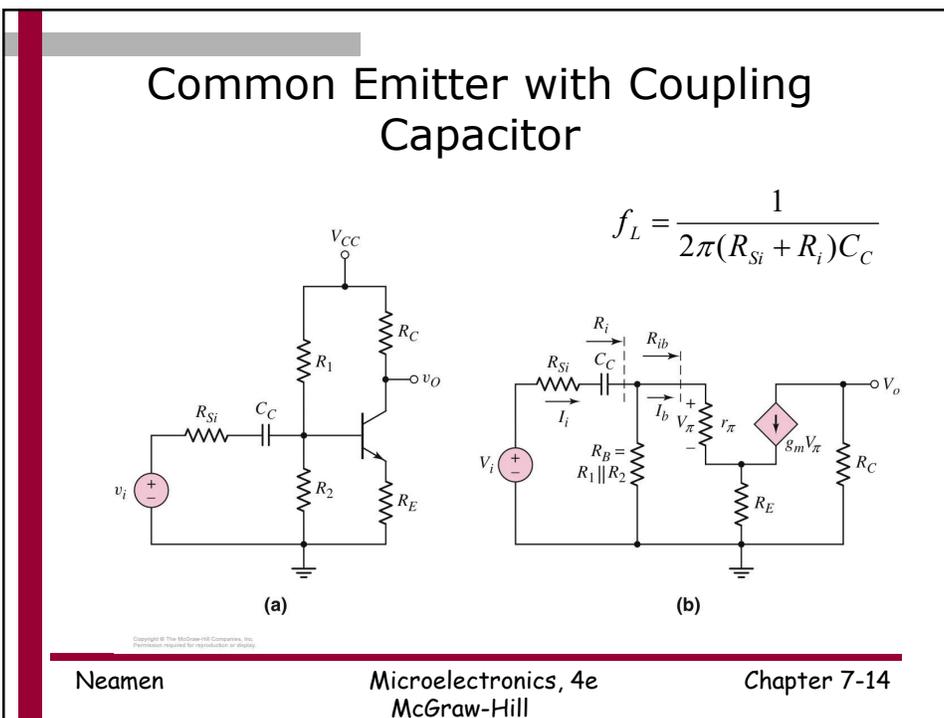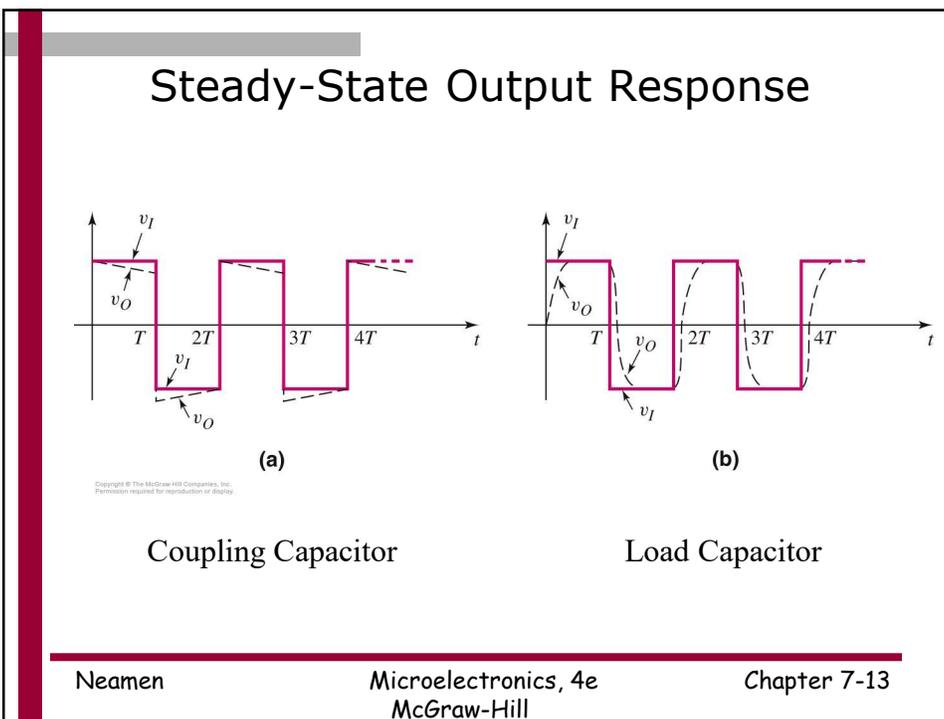

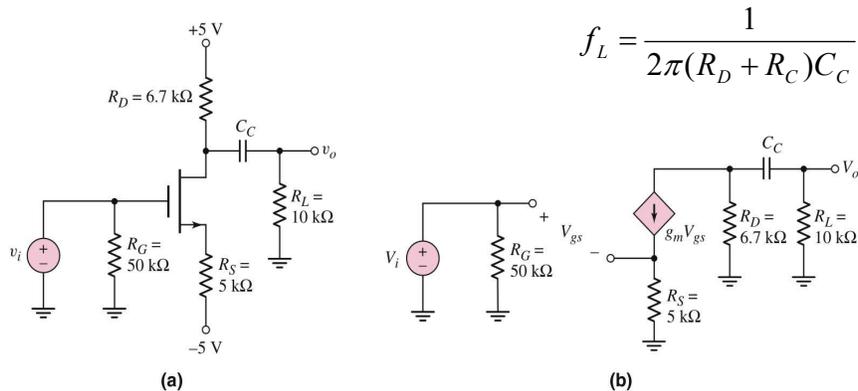Common Source with Output Coupling Capacitor




$$f_L = \frac{1}{2\pi(R_D + R_C)C_C}$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-15

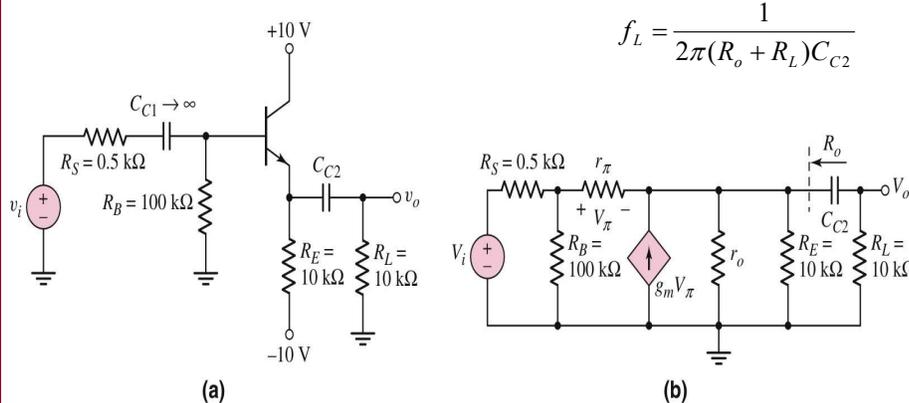Emitter Follower with Output Coupling Capacitor



$$f_L = \frac{1}{2\pi(R_o + R_L)C_{C2}}$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-16

Problem-Solving Technique: Bode Plot of Gain Magnitude


1. Determine whether capacitor is producing a low-pass or high-pass circuit.
 - a. Sketch general shape of Bode plot
2. Corner frequency is $f = 1/(2\pi\tau)$ where $\tau = R_{eq}C$
 - a. R_{eq} is resistance seen by capacitor
3. Maximum gain magnitude is midband gain.
 - a. Coupling and bypass capacitors act as shorts
 - b. Load capacitors act as opens

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-17

Common Source with Load Capacitor

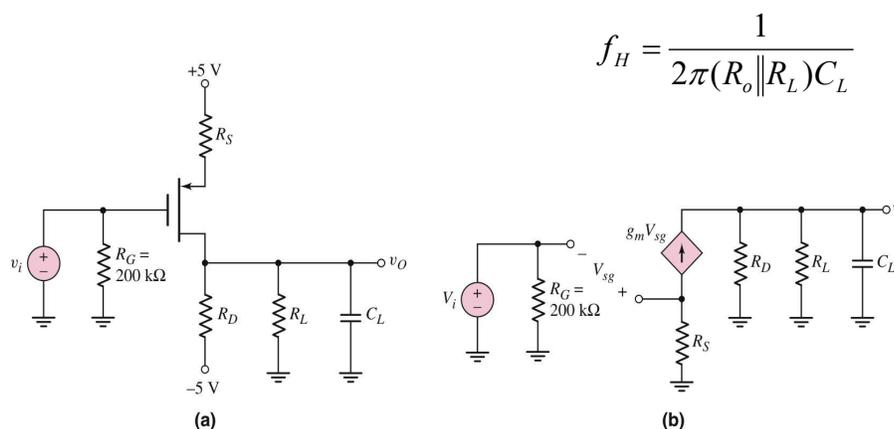


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-18

Coupling and Parallel Load Capacitors

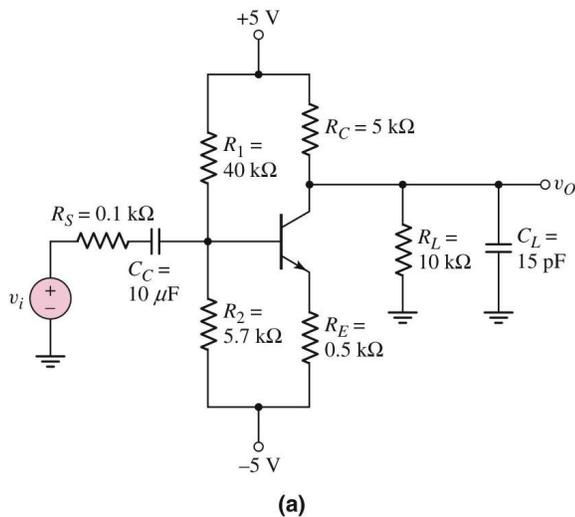


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-19

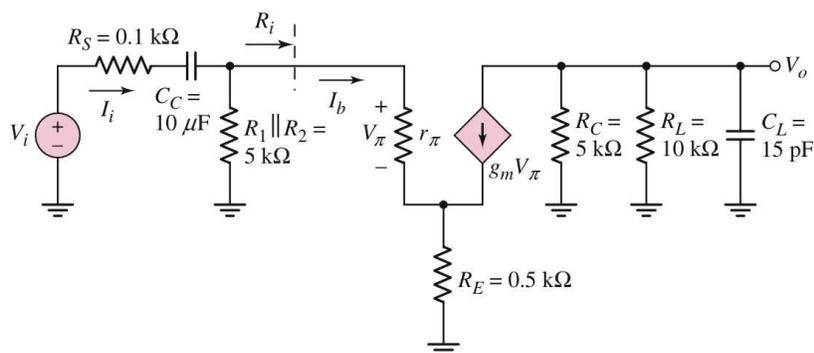Small-Signal Equivalent Circuit: Coupling and Parallel Load Capacitor



$$f_L = \frac{1}{2\pi[R_S + (R_1 \parallel R_2 \parallel R_i)]C_C} \quad (b)$$


$$f_H = \frac{1}{2\pi(R_C \parallel R_L)C_P}$$

Neamen

Microelectronics, 4e
McGraw-Hill


Chapter 7-20

Emitter Bypass Capacitor

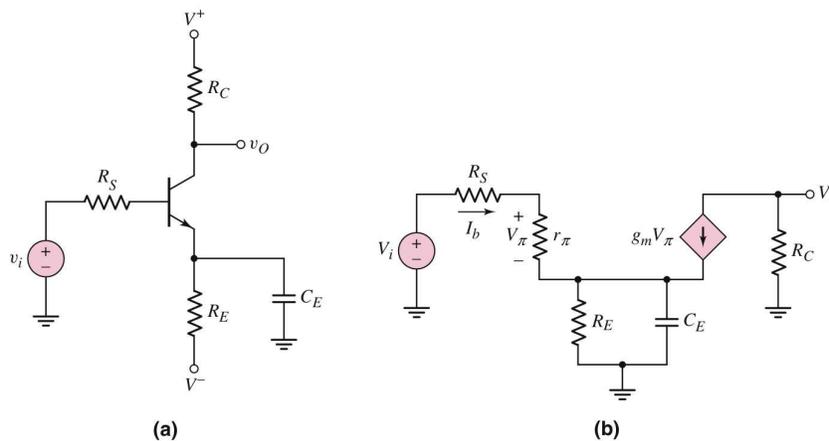

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

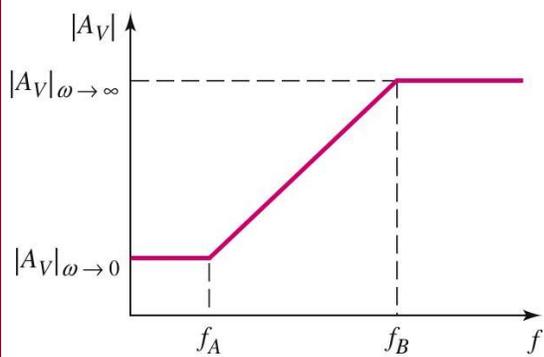Bode Plot of Voltage Gain Magnitude: Emitter Bypass Capacitor




Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$|A_V|_{\omega \rightarrow 0} = \frac{g_m r_\pi R_C}{R_S + r_\pi + (1 = \beta) R_E}$$

$$|A_V|_{\omega \rightarrow \infty} = \frac{g_m r_\pi R_C}{R_S + r_\pi}$$

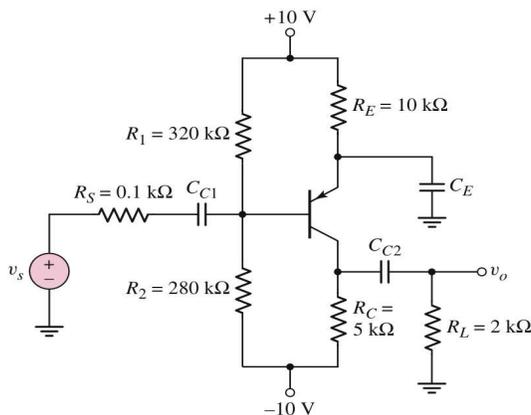Two Coupling Capacitors and a Emitter Bypass Capacitor




Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-23

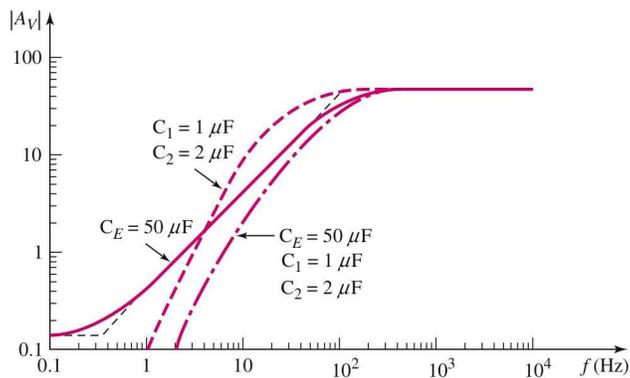PSpice Results for Two Coupling Capacitors and a Emitter Bypass Capacitor




Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-24

Expanded Hybrid π Equivalent Circuit

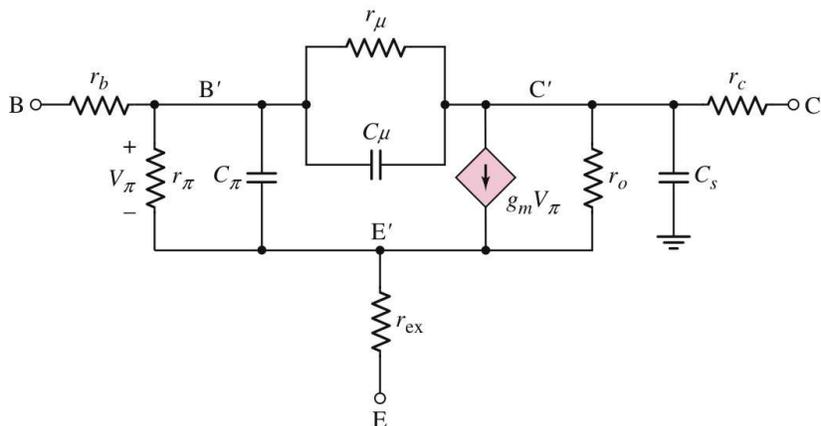


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-25

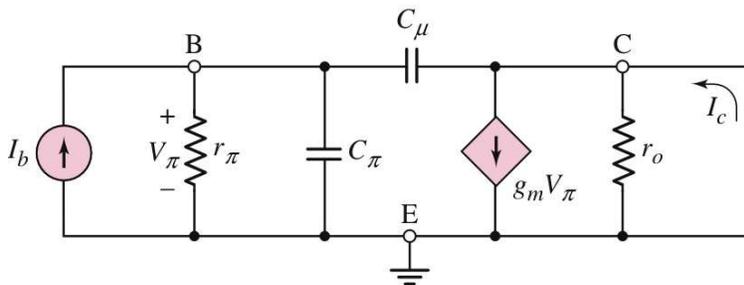Short-Circuit Current Gain: Analysis of Frequency Response of BJT





Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-26

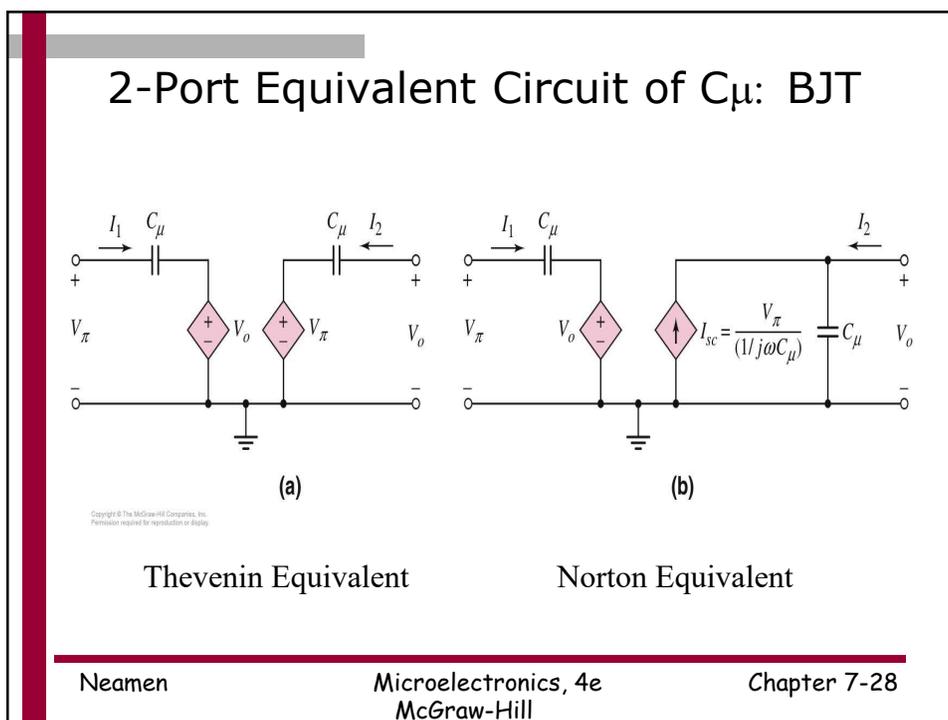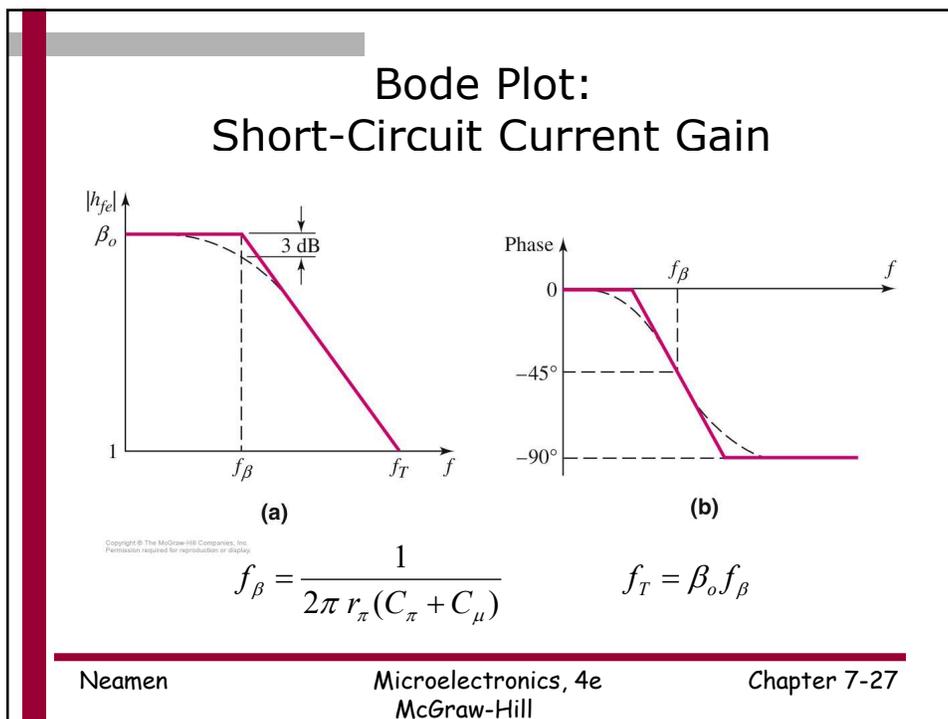

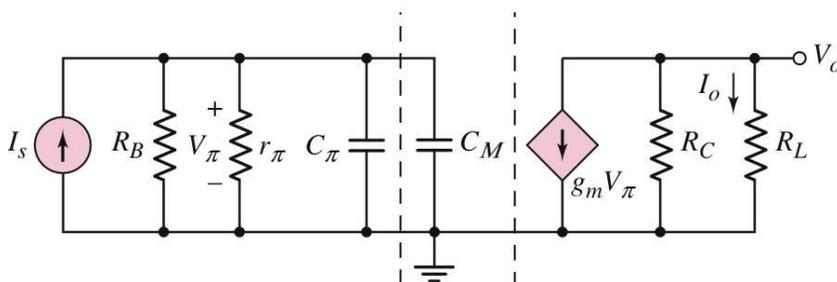Small-Signal Equivalent Circuit with Miller Capacitance: BJT



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.


$$C_M = C_{\mu} [1 + g_m (R_C || R_L)]$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-29

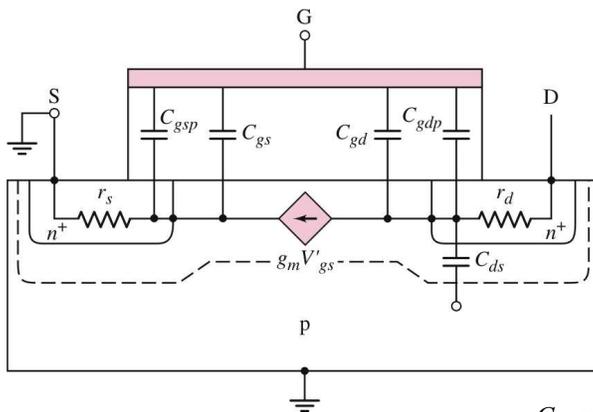Inherent Resistances and Capacitances in n-Channel MOSFET



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.


$$C_{gs} \cong C_{gd} \cong \frac{1}{2} W L C_{ox}$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-30

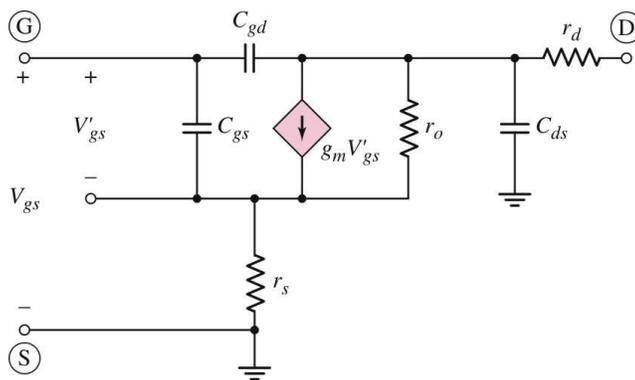Equivalent Circuit for n-Channel Common Source MOSFET




Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-31

Unity-Gain Bandwidth

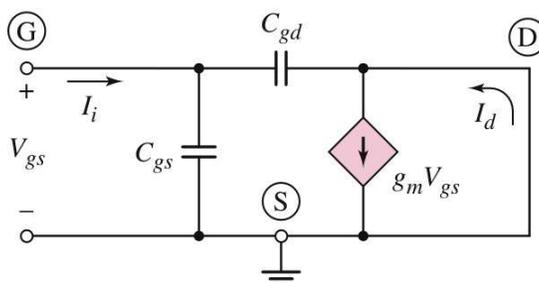

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.


$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-32

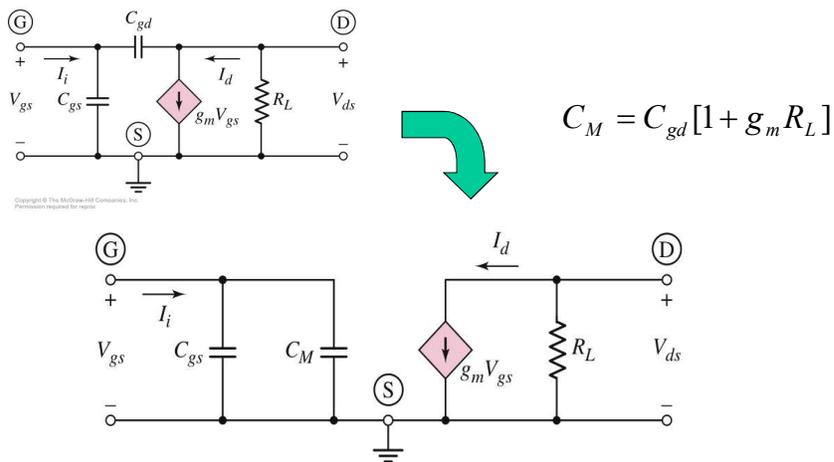Small-Signal Equivalent Circuit with Miller Capacitance: MOSFET




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-33

Common-Emitter Amplifier

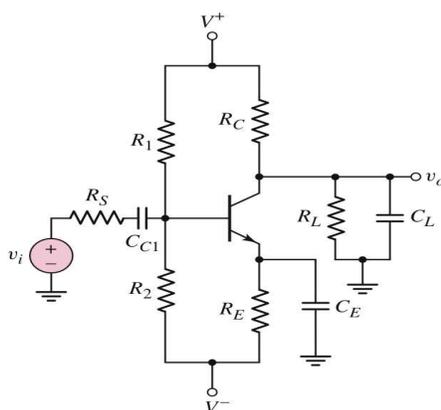


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-34

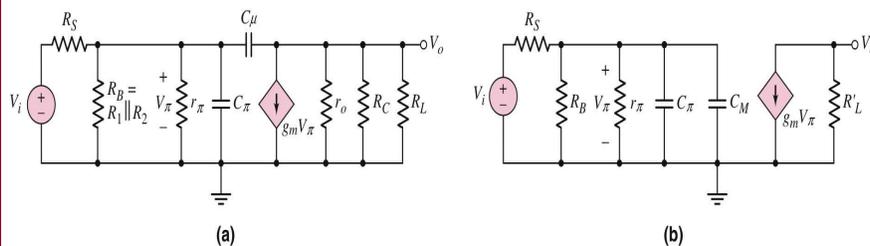High-Frequency Equivalent Circuit: Common Emitter




$$f_H = \frac{1}{2\pi[r_\pi \parallel R_B \parallel R_S](C_\pi + C_\mu)}$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-35

PSpice Results for Common Emitter

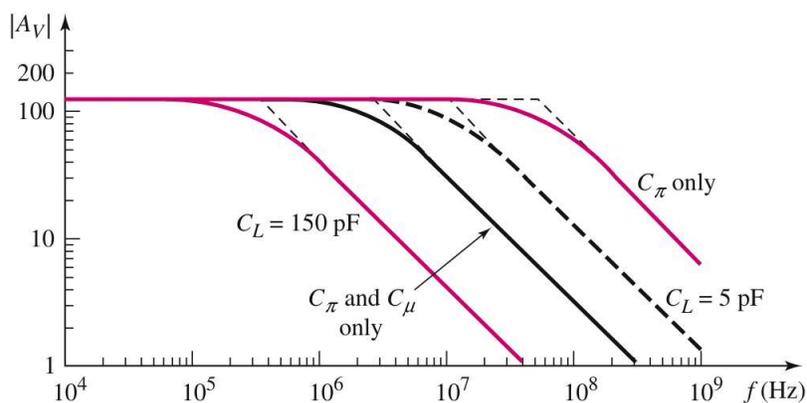


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-36

Common-Base Amplifier

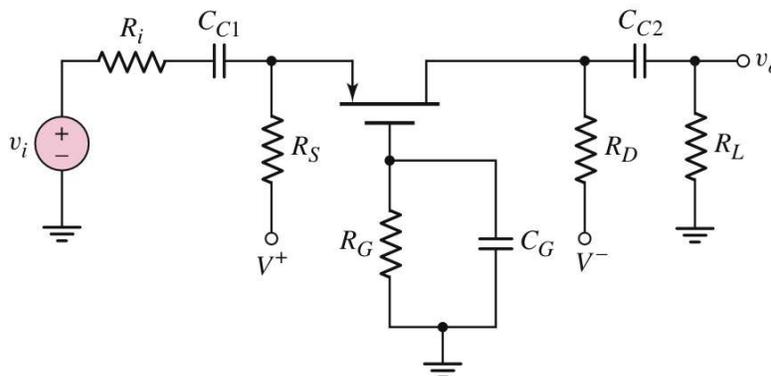


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-37

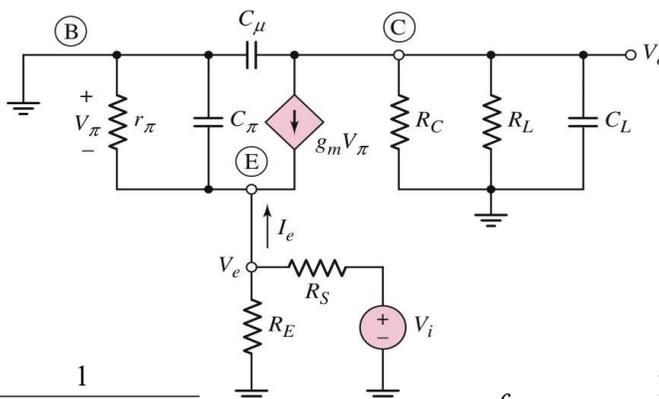High-Frequency Equivalent Circuit: Common Base



$$f_{H\pi} = \frac{1}{2\pi \left[\frac{r_{\pi}}{1+\beta} \parallel R_B \parallel R_S \right] C_{\pi}}$$

(a)


$$f_{H\mu} = \frac{1}{2\pi (R_C \parallel R_L) C_{\mu}}$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-38

PSpice Results for Common Emitter

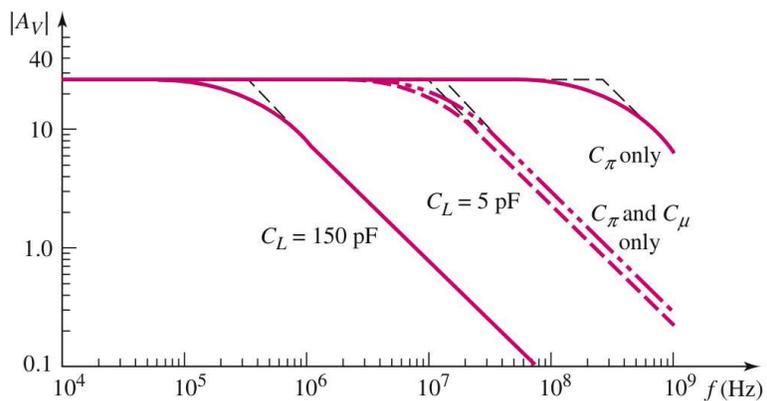


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-39

Cascode Circuit

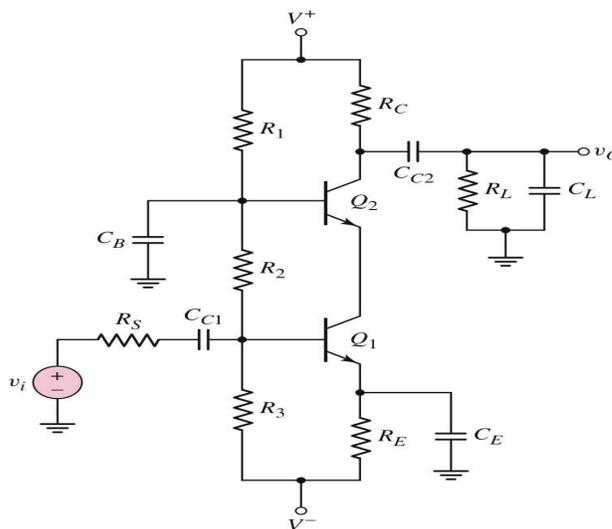


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-40

Emitter-Follower Circuit

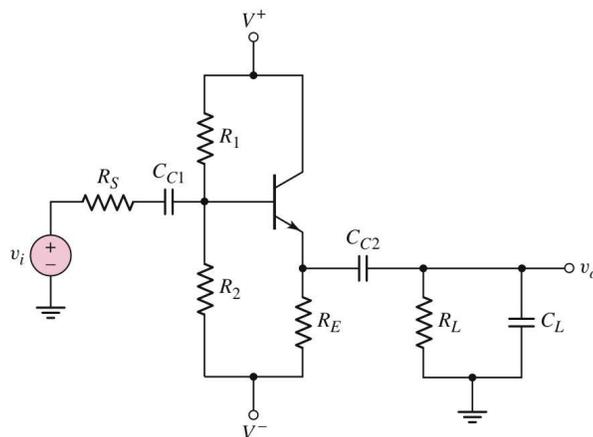


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-43

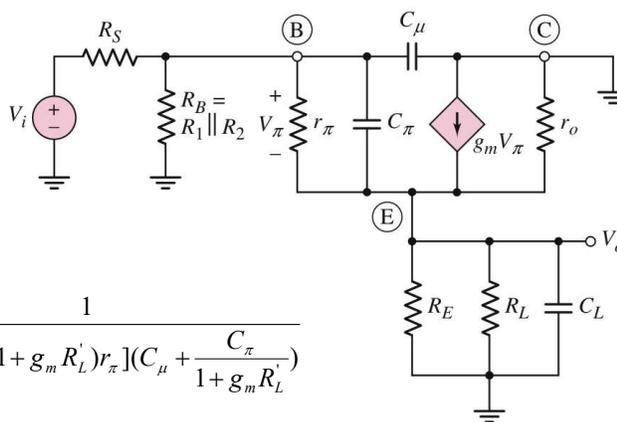High-Frequency Equivalent Circuit: Emitter Follower



$$f_H \cong \frac{1}{2\pi[R_S \parallel R_B \parallel (1 + g_m R'_L)r_\pi](C_\mu + \frac{C_\pi}{1 + g_m R'_L})}$$

(a)

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 7-44

