

Microelectronics Circuit Analysis and Design

Donald A. Neamen

Chapter 9

*Ideal Operational Amplifiers
and Op-Amp Circuits*

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-1

In this chapter, we will:


- Develop the parameters and characteristics of the ideal operational amplifier, and determine the analysis method of ideal op-amp circuits.
 - inverting operational amplifier
 - summing operational amplifier
 - noninverting operational amplifier
- Analyze several ideal op-amp circuits including the difference amplifier and the instrumentation amplifier.
- Design several ideal op-amp circuits with given design specifications.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-2

Ideal Op-Amp Equivalent Circuit

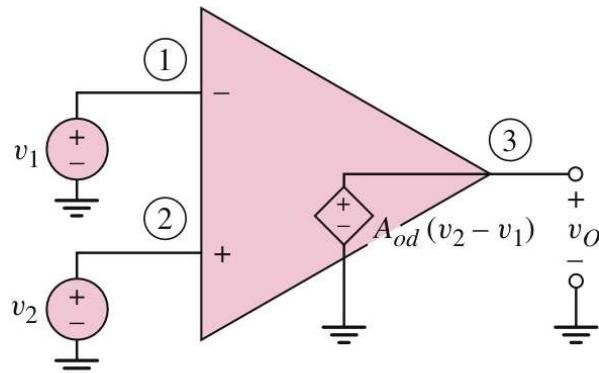


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-3

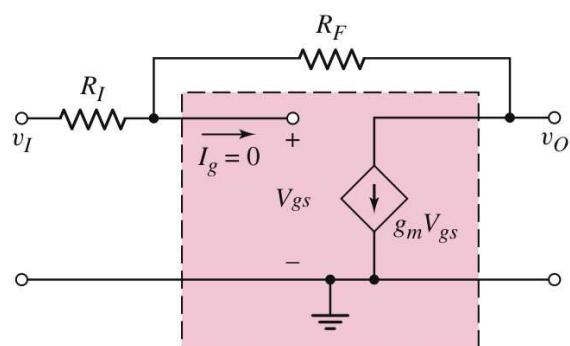Small-Signal Equivalent Circuit: MOSFET with Input and Output Feedback



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.


$$\frac{v_O}{v_I} = -\frac{R_F}{R_I}$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-4

Output Impedance : MOSFET with Input and Output Feedback

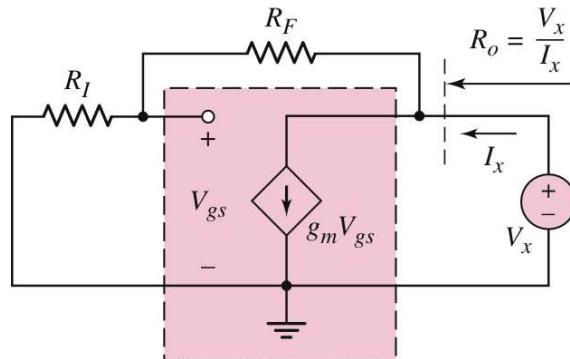
Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$R_o = \frac{R_I + R_F}{1 + g_m R_I}$$


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-5

Ideal Op-Amp Characteristics

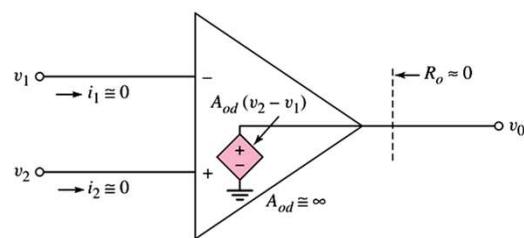1. Internal differential gain A_{od} is infinite.
2. Differential input voltage ($v_2 - v_1$) is zero.
3. Effective input resistance is infinite.
4. Output resistance is zero, so output voltage is connected directly to dependent voltage source.





Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-6

Equivalent Circuit of Op-Amp

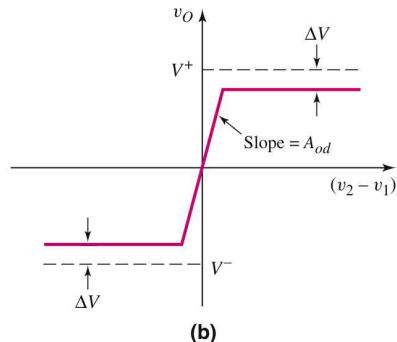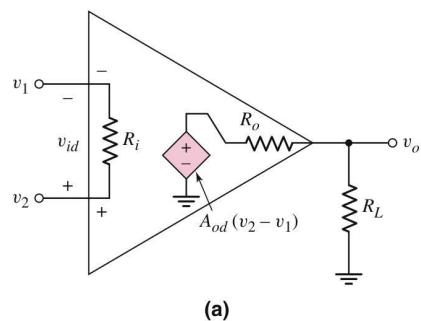


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-7

Inverting Op-Amp

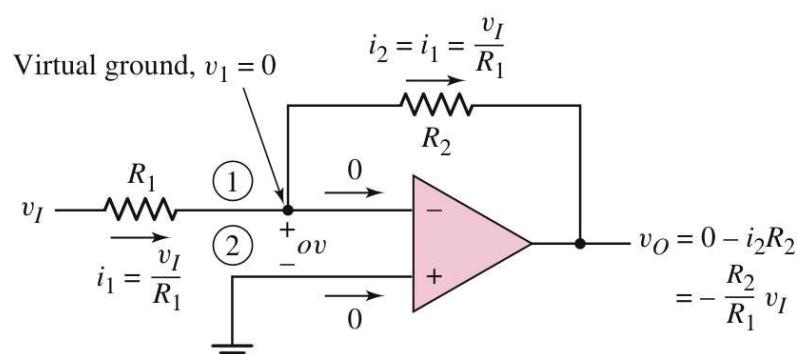

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-8

Problem-Solving Technique: Ideal Op-Amp Circuits

1. If noninverting terminal is grounded, then inverting terminal is virtual ground.
 - a. Sum currents at node assuming no current enters Op Amp.
2. If noninverting terminal is not grounded, then inverting terminal voltage is equal to that of the noninverting terminal.
 - a. Sum currents at node assuming no current enters Op Amp.
3. Output voltage is determined from either Step 1 or 2.


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-9

Inverting Op-Amp with T-Network

$$A_v = -\frac{R_2}{R_1} \left(1 + \frac{R_3}{R_4} + \frac{R_3}{R_2}\right)$$

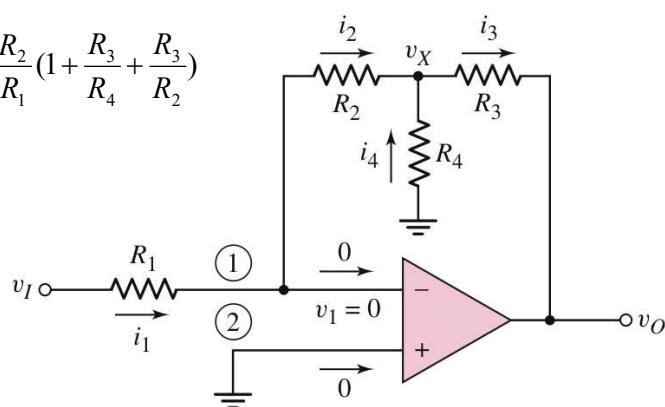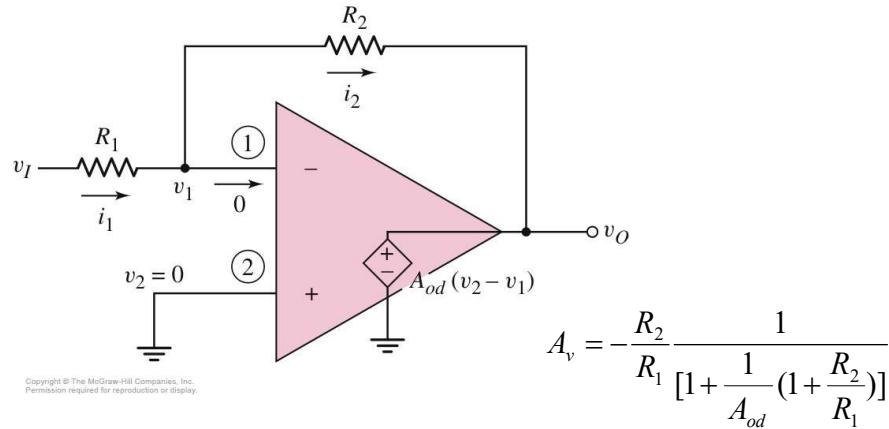

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-10

Inverting Op-Amp with Finite Differential-Mode Gain




Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-11

Summing Op-Amp

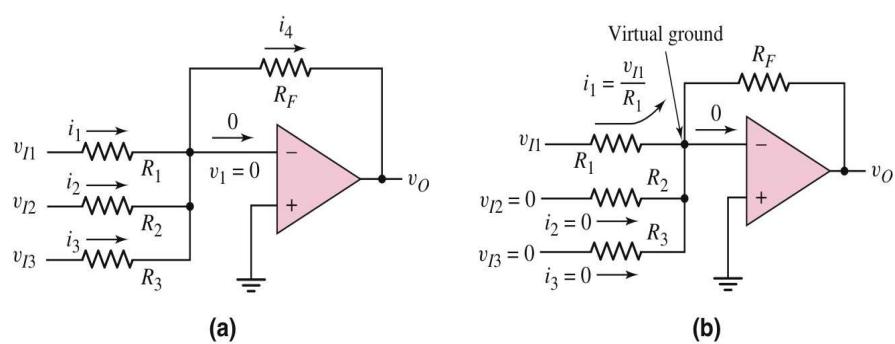


$$v_O = -\left(\frac{R_F}{R_1}v_{I1} + \frac{R_F}{R_2}v_{I2} + \frac{R_F}{R_3}v_{I3}\right)$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-12

Noninverting Op-Amp

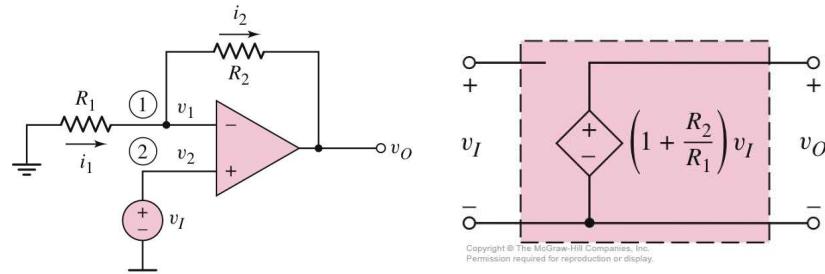


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-13

Voltage Follower

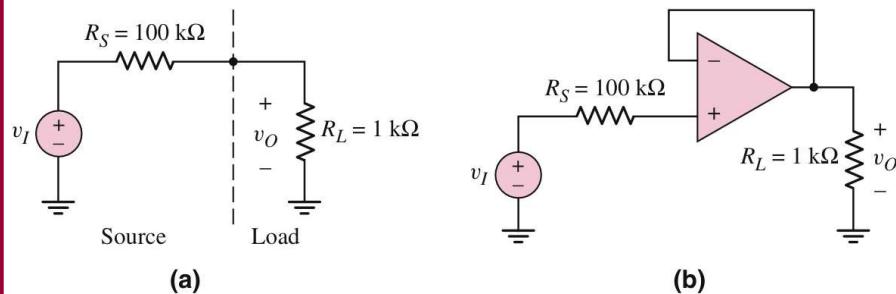


$$\frac{v_O}{v_I} = \frac{R_L}{R_L + R_S}$$

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-14

Current-to-Voltage Converter

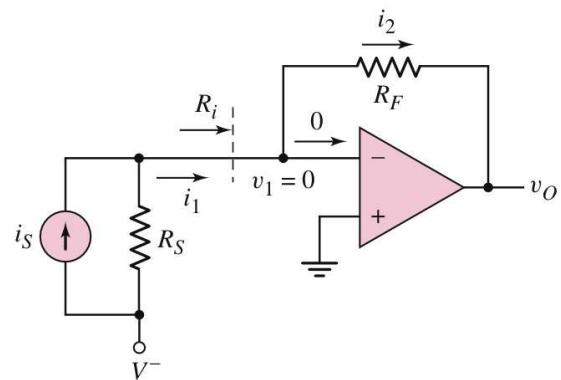


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-15

Voltage-to-Current Converter

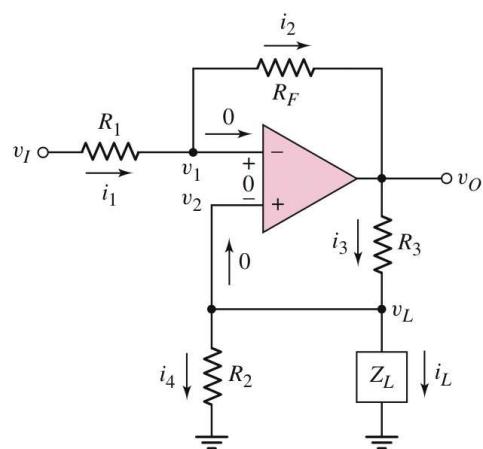


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-16

Op-Amp Difference Amplifier

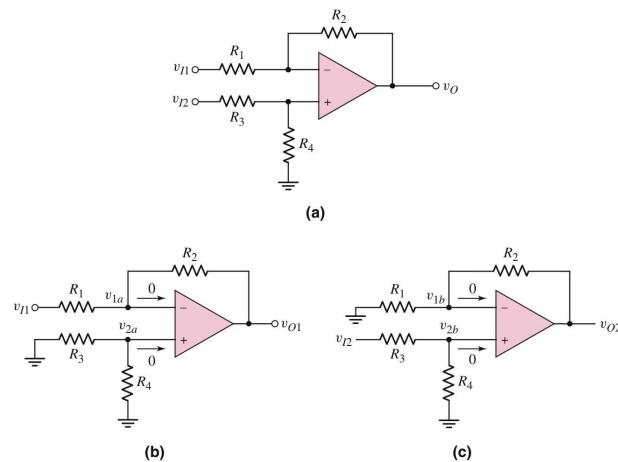


Neamen

Copyright © The McGraw-Hill Companies, Inc.
Microelectronics, 4e
Permission required for reproduction or display
McGraw-Hill

Chapter 9-17

Instrumentation Amplifier


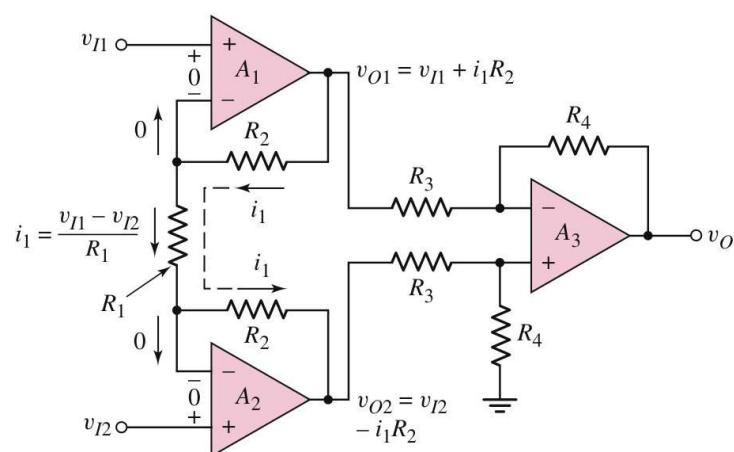


Neamen

Copyright © The McGraw-Hill Companies, Inc.
Microelectronics, 4e
Permission required for reproduction or display
McGraw-Hill

Chapter 9-18

Op-Amp Integrator and Differentiator

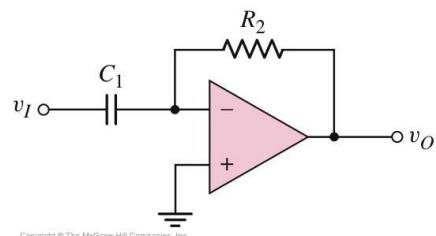
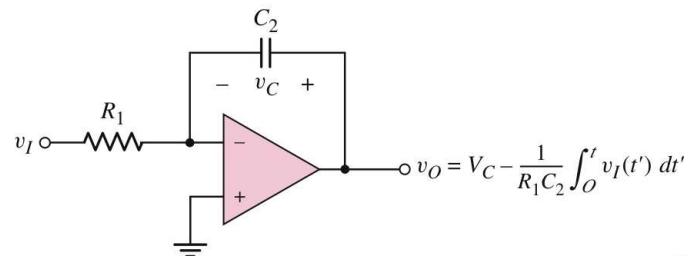


Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-19

Precision Half-Wave Rectifier

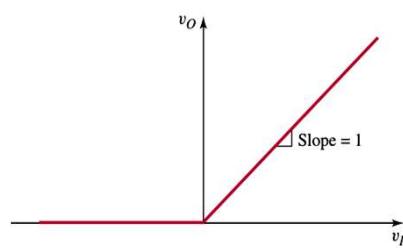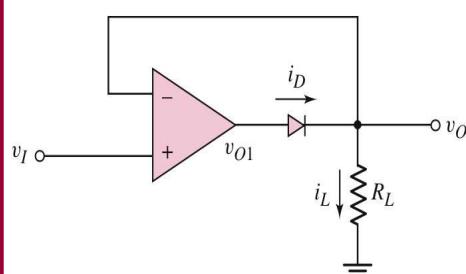


Neamen


Microelectronics, 4e
McGraw-Hill

Chapter 9-20

Log and Antilog Amplifiers

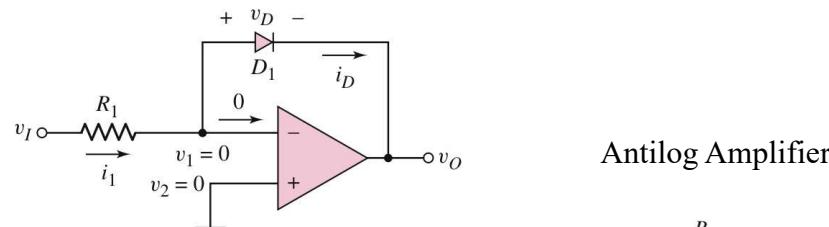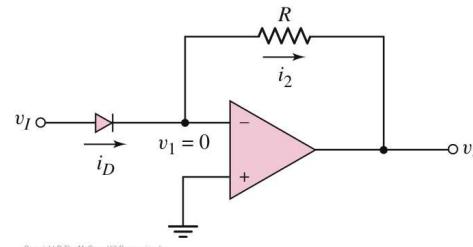

Log Amplifier


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-21

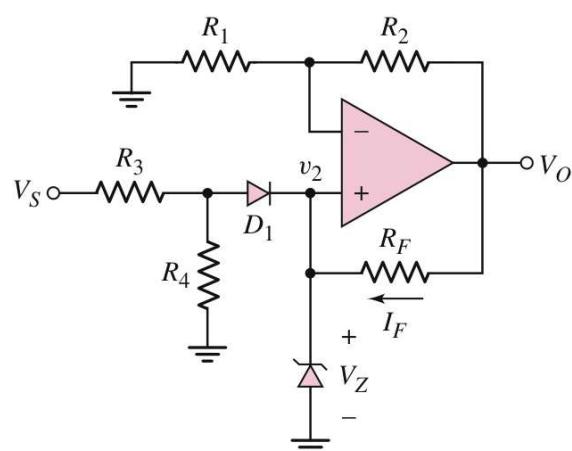Op-Amp Voltage Reference Circuit


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Neamen

Microelectronics, 4e
McGraw-Hill

Chapter 9-22