



Laboratorij za načrtovanje integriranih vezij



FE

UNIVERZA V LJUBLJANI
Fakulteta za elektrotehniko


Linearna elektronska vezja

Frekvenčni odziv


In this chapter, we will:

- ▶ Discuss the general frequency response characteristics of amplifiers.
- ▶ Derive the system transfer functions
 - ▶ Develop the Bode diagrams of the magnitude and phase of the transfer functions.
- ▶ Analyze the frequency response of transistor circuits with capacitors.
 - ▶ Determine the Miller effect and Miller capacitance.
- ▶ Determine the high-frequency response of basic transistor circuit configurations.


Amplifier Gain Versus Frequency

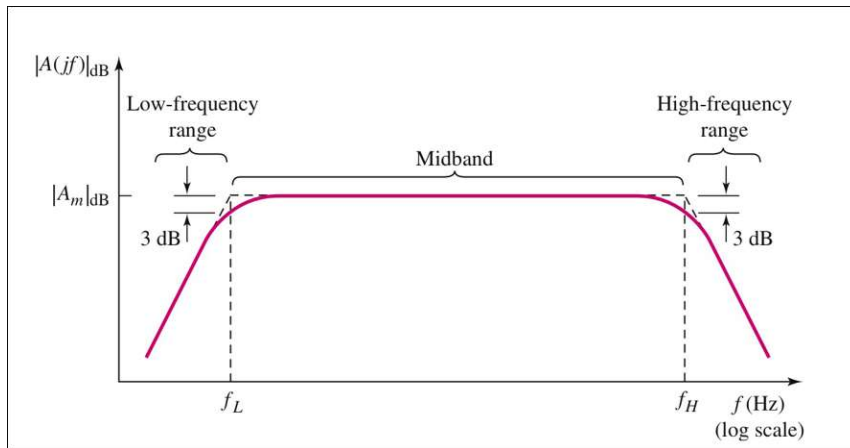


Series Coupling Capacitor Circuit

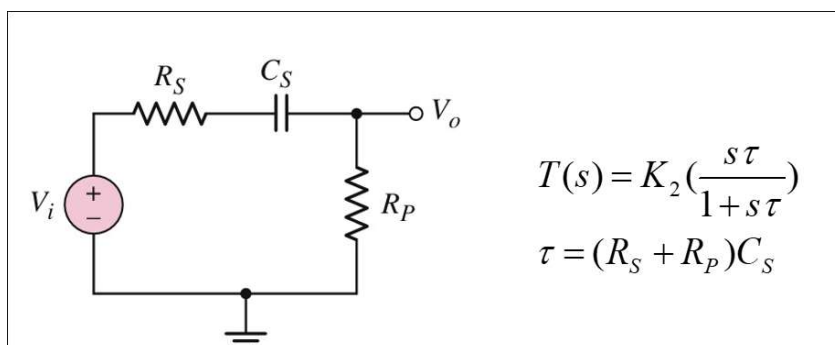

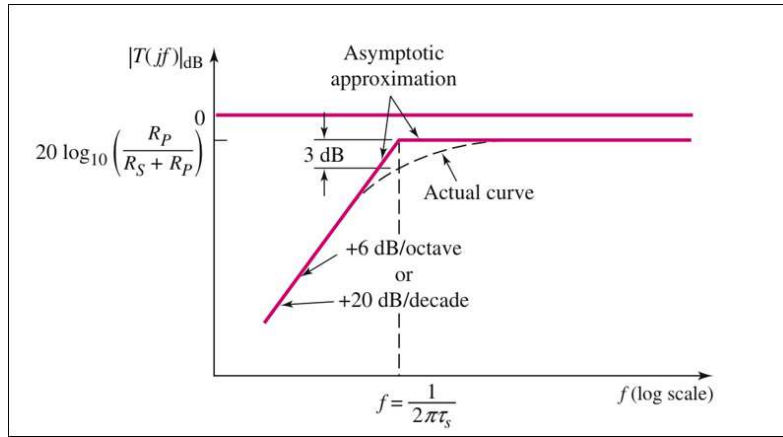
Bode Plot of Voltage Transfer Function (Magnitude)



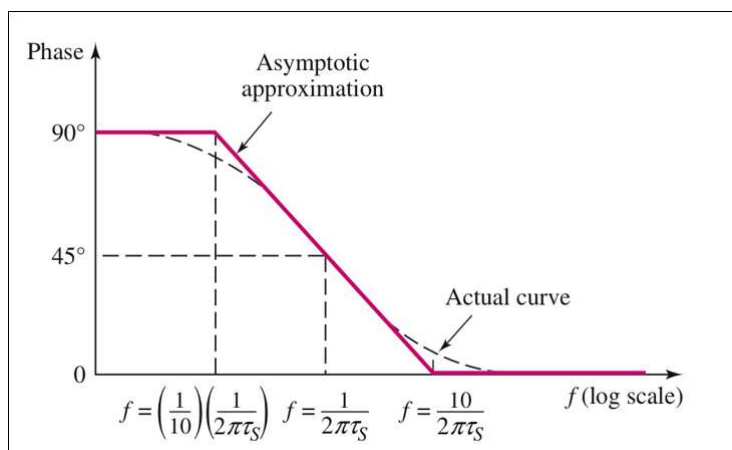
Bode Plot of Voltage Transfer Function (Phase)




Parallel Load Capacitor Circuit

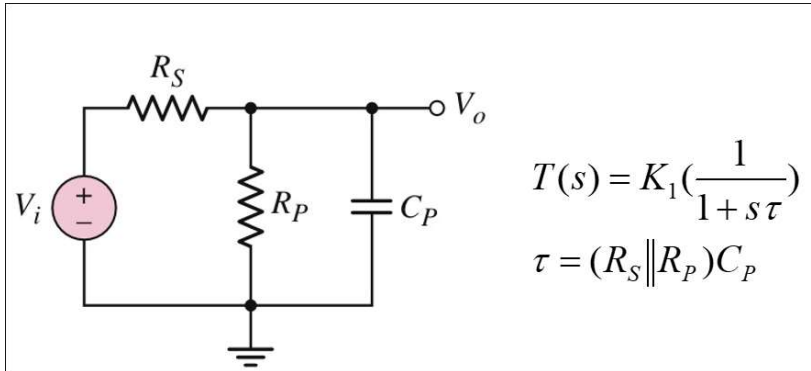

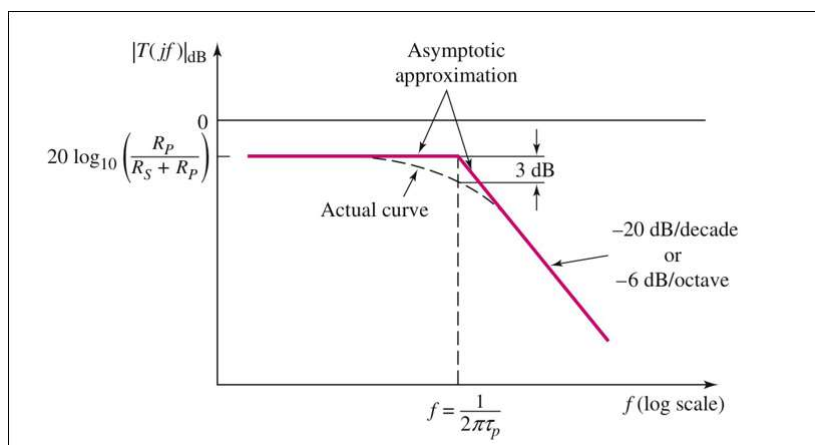
Bode Plot of Voltage Transfer Function (Magnitude)



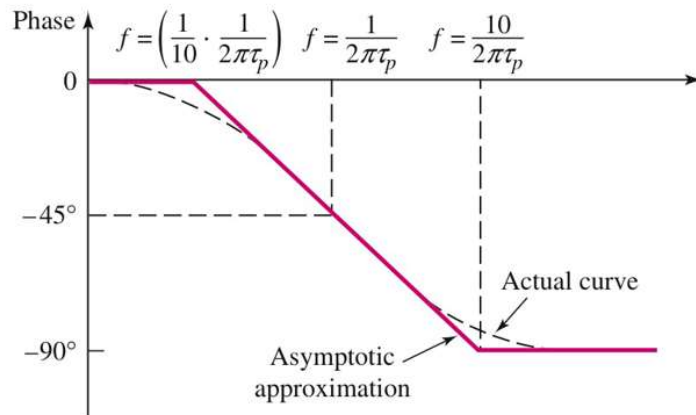Bode Plot of Voltage Transfer Function (Phase)



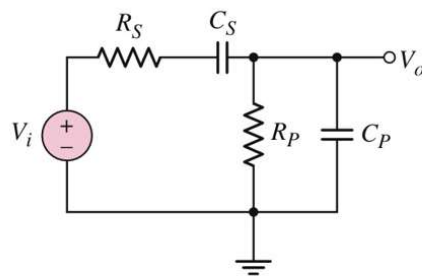Circuit with Series Coupling and Parallel Load Capacitor



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.


$$\tau_S = (R_S + R_P)C_S$$

$$\tau_P = (R_S \parallel R_P)C_P$$


$$f_L = \frac{1}{2\pi\tau_S}$$

$$f_H = \frac{1}{2\pi\tau_P}$$

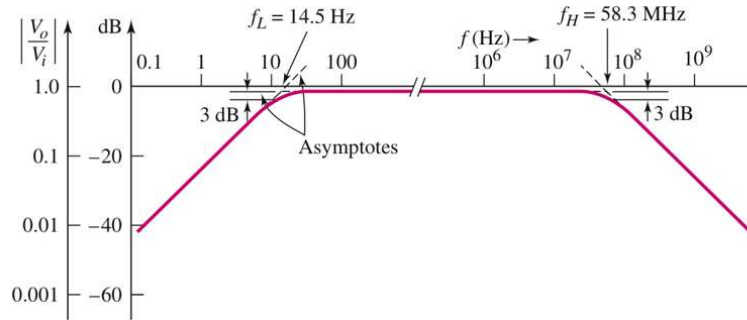
Bode Plot of Magnitude of Voltage Transfer Function




Common Emitter with Coupling Capacitor

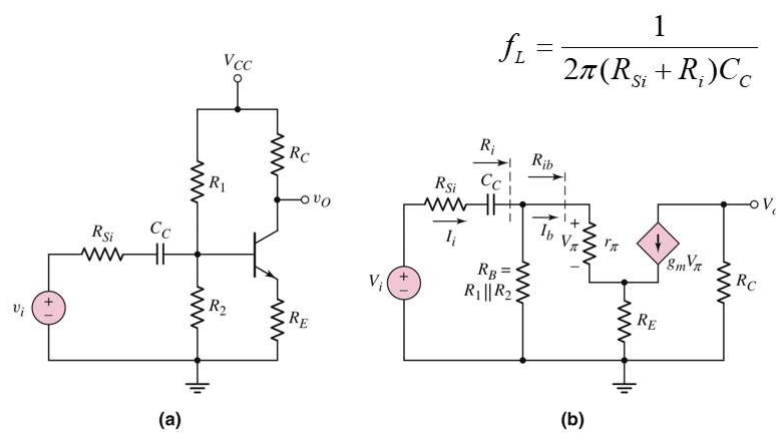

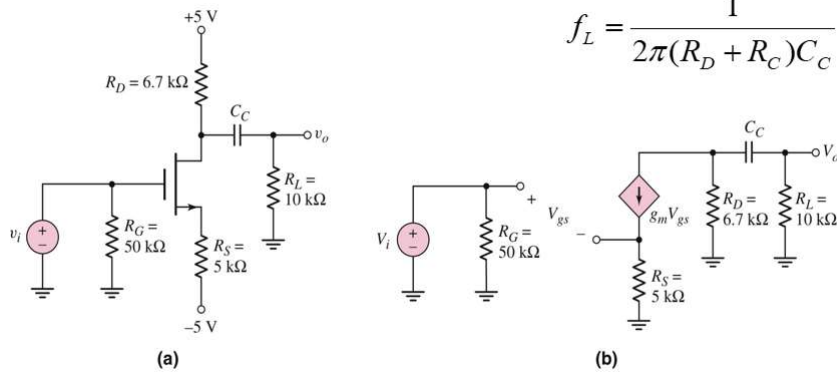Common Source with Output Coupling Capacitor



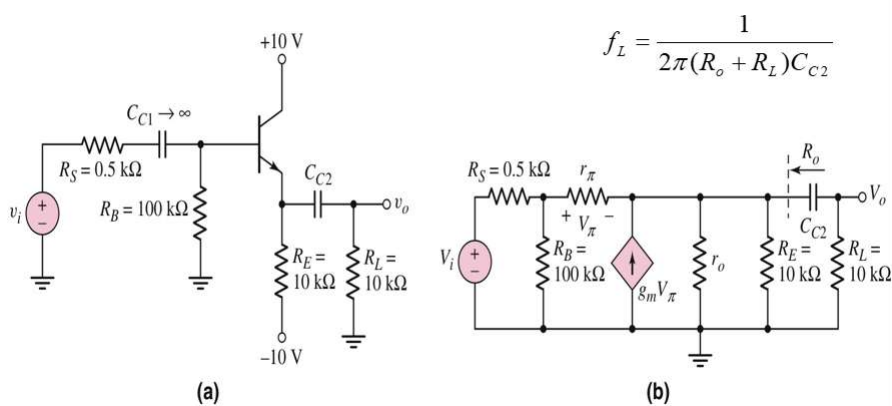
Emitter Follower with Output Coupling Capacitor




Problem-Solving Technique: Bode Plot of Gain Magnitude

- ▶ Determine whether capacitor is producing a low-pass or high-pass circuit.
 - ▶ Sketch general shape of Bode plot
- ▶ Corner frequency is $f = 1/(2\pi\tau)$ where $\tau = R_{eq}C$
 - ▶ R_{eq} is resistance seen by capacitor
- ▶ Maximum gain magnitude is midband gain.
 - ▶ Coupling and bypass capacitors act as shorts
 - ▶ Load capacitors act as opens


Common Source with Load Capacitor

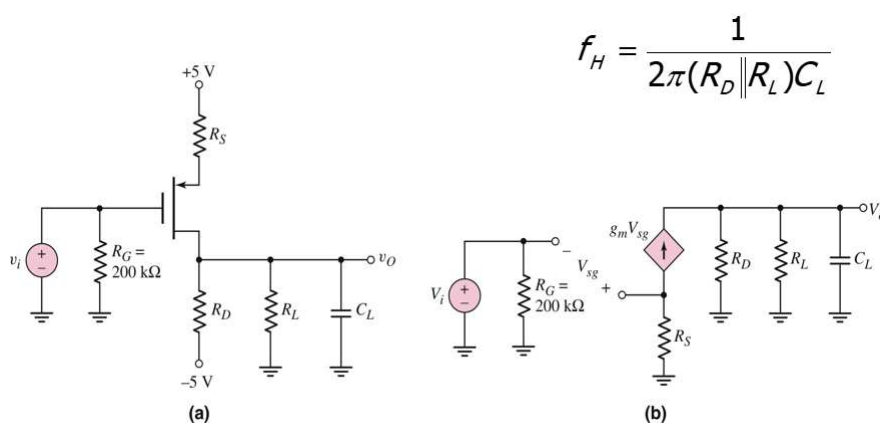

Coupling and Parallel Load Capacitors

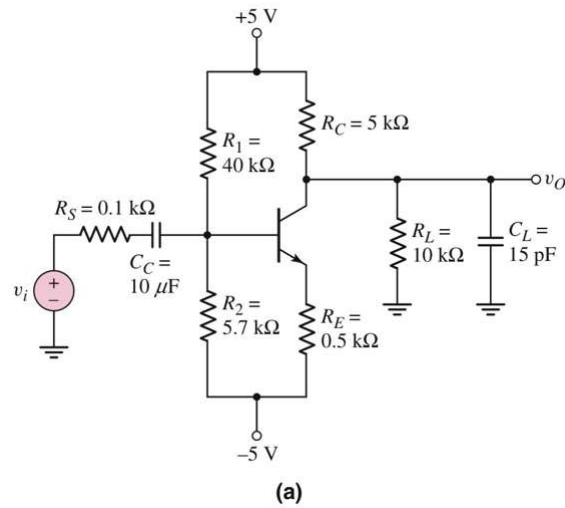

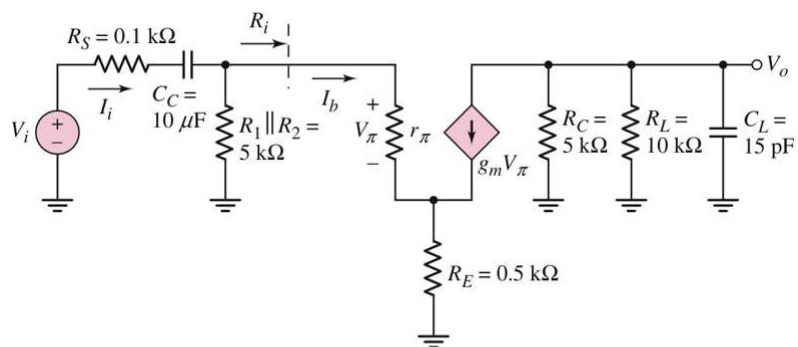
Small-Signal Equivalent Circuit:
Coupling and Parallel Load Capacitor




$$f_L = \frac{1}{2\pi[R_S + (R_1 || R_2 || R_i)]C_C} \quad (b)$$

$$f_H = \frac{1}{2\pi(R_C || R_L)C_P}$$

Emitter Bypass Capacitor

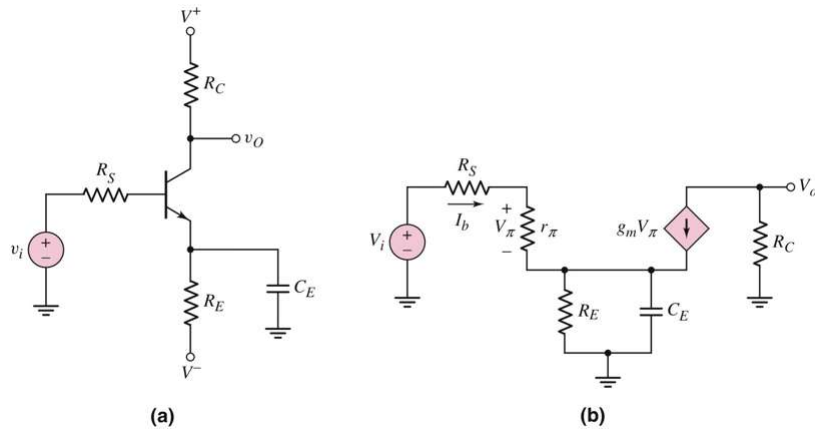

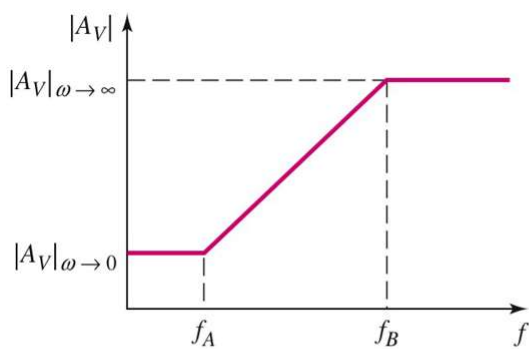Bode Plot of Voltage Gain Magnitude: Emitter Bypass Capacitor




Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.


$$|A_V|_{\omega \rightarrow 0} = \frac{g_m r_\pi R_C}{R_S + r_\pi + (1 + \beta) R_E}$$

$$|A_V|_{\omega \rightarrow \infty} = \frac{g_m r_\pi R_C}{R_S + r_\pi}$$

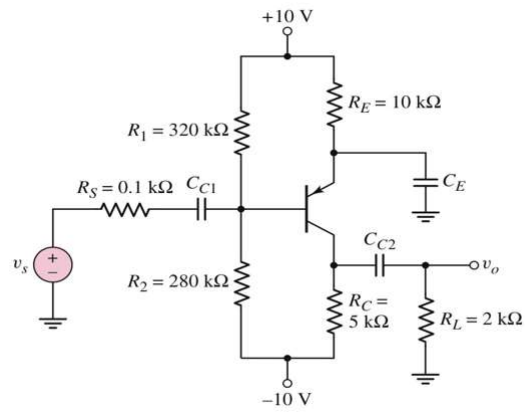
Two Coupling Capacitors and a Emitter Bypass Capacitor



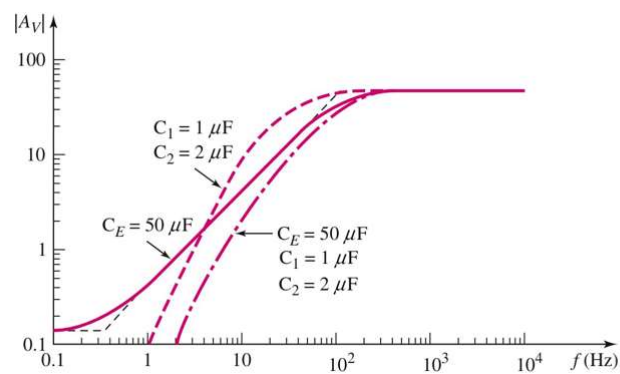
PSpice Results for Two Coupling Capacitors and a Emitter Bypass Capacitor




Expanded Hybrid π Equivalent Circuit

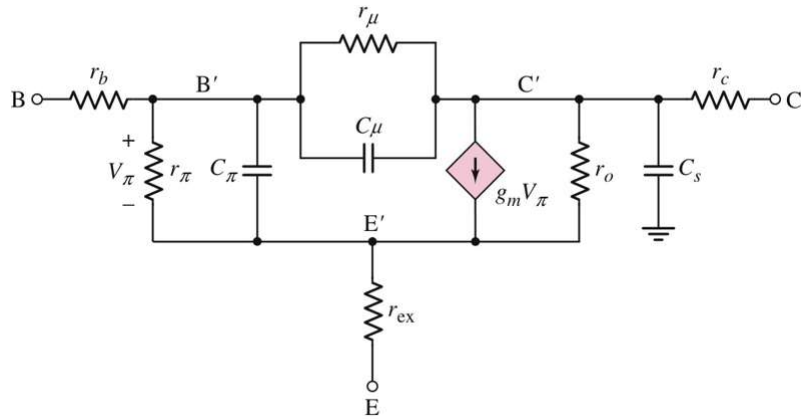

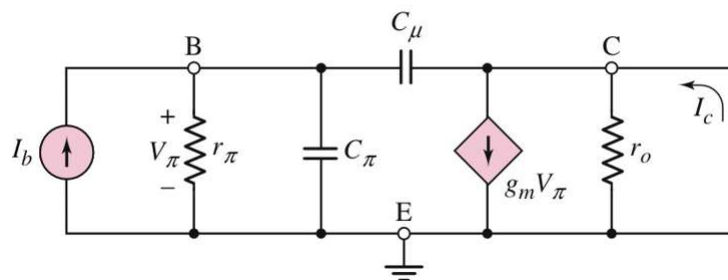Short-Circuit Current Gain: Analysis of Frequency Response of BJT



Bode Plot: Short-Circuit Current Gain

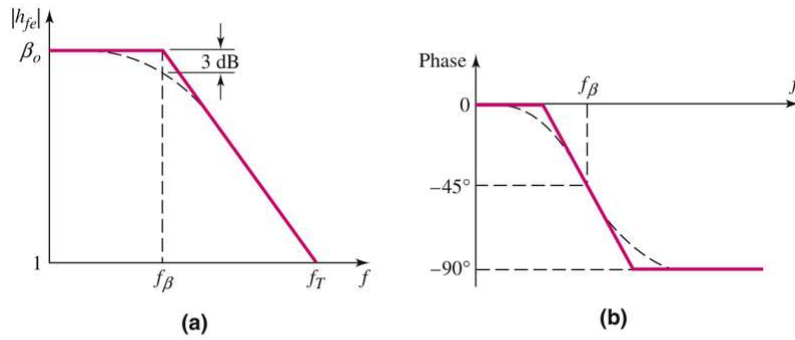


Copyright © The McGraw-Hill Companies, Inc.
Permission is granted for reproduction or display.

$$f_{\beta} = \frac{1}{2\pi r_{\pi}(C_{\pi} + C_{\mu})}$$

$$f_T = \beta_o f_{\beta}$$

2-Port Equivalent Circuit of C_{μ} : BJT

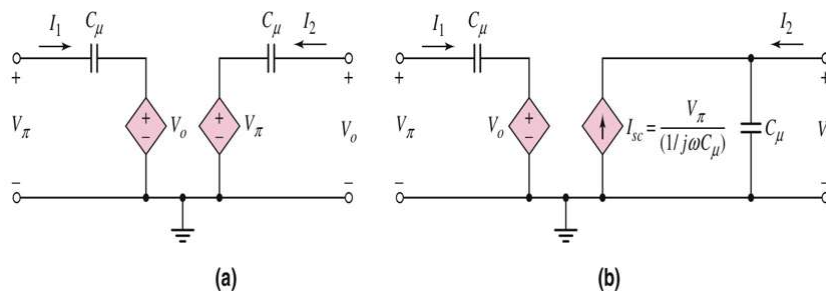


Copyright © The McGraw-Hill Companies, Inc.
Permission is granted for reproduction or display.

Thevenin Equivalent

Norton Equivalent

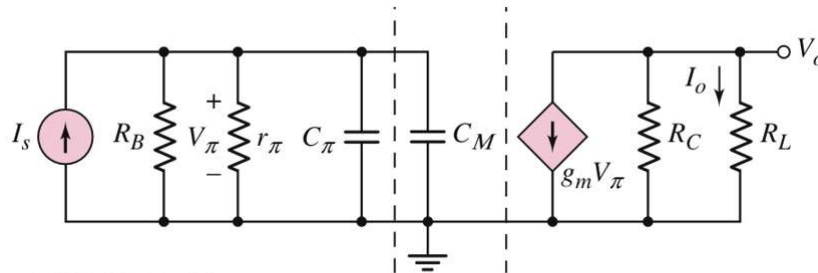
Small-Signal Equivalent Circuit with Miller Capacitance: BJT



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$C_M = C_{\mu} [1 + g_m (R_C || R_L)]$$

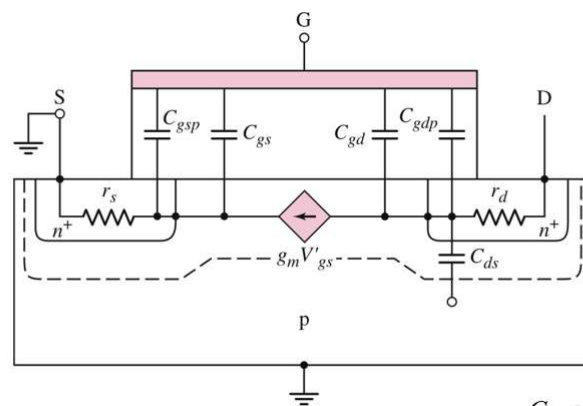
Inherent Resistances and Capacitances in n-Channel MOSFET




Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$C_{gs} \cong C_{gd} \cong \frac{1}{2} W L C_{ox}$$

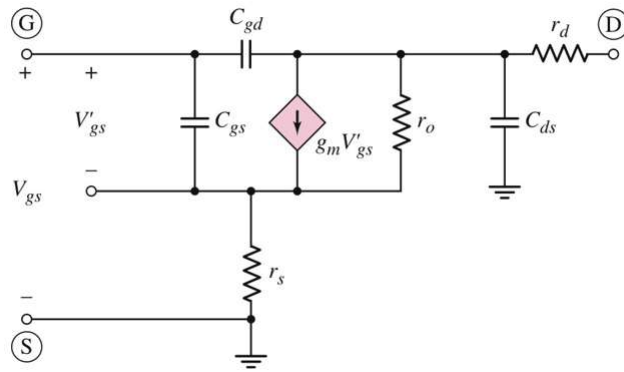Equivalent Circuit for n-Channel Common Source MOSFET




Unity-Gain Bandwidth

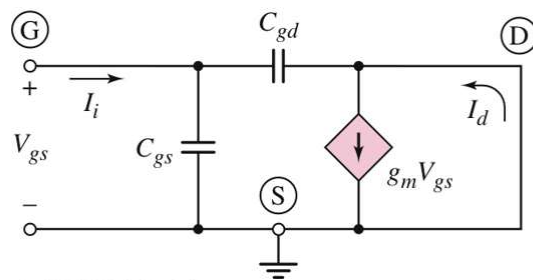


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

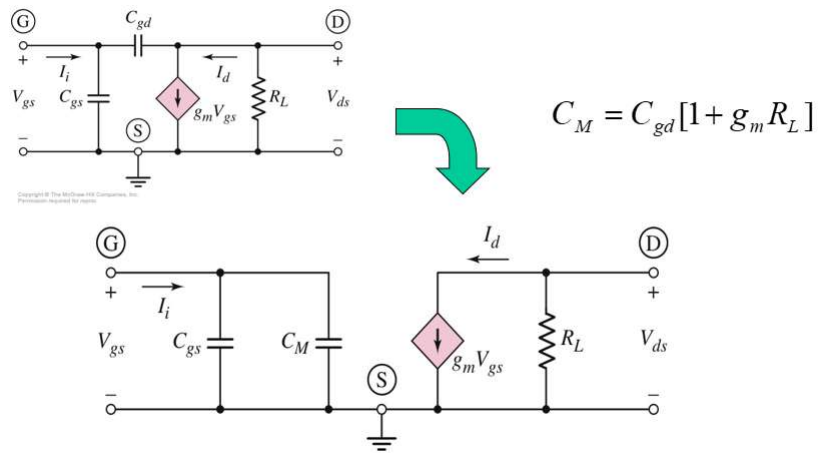
Small-Signal Equivalent Circuit with Miller Capacitance: MOSFET



Common-Emitter Amplifier

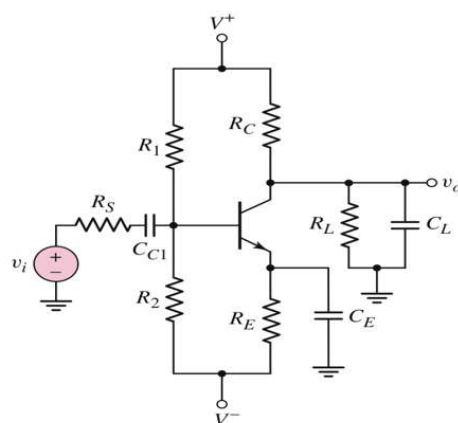


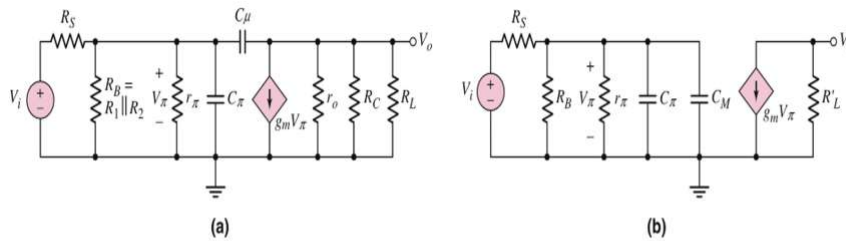High-Frequency Equivalent Circuit: Common Emitter




$$f_H = \frac{1}{2\pi[r_{\pi} \parallel R_B \parallel R_S](C_{\pi} + C_M)}$$


PSpice Results for Common Emitter

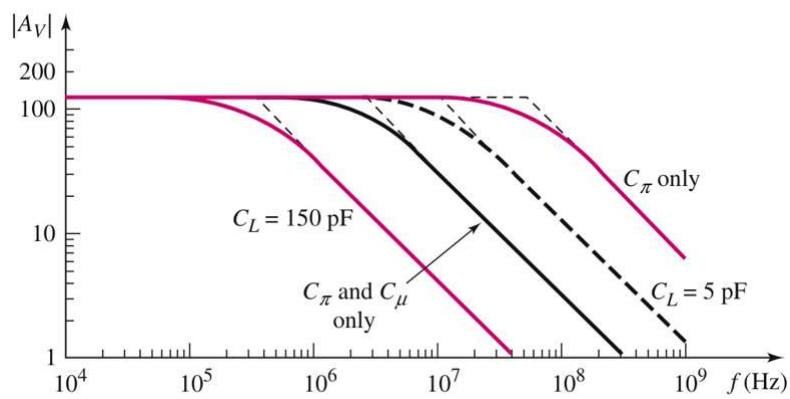

Common-Base Amplifier

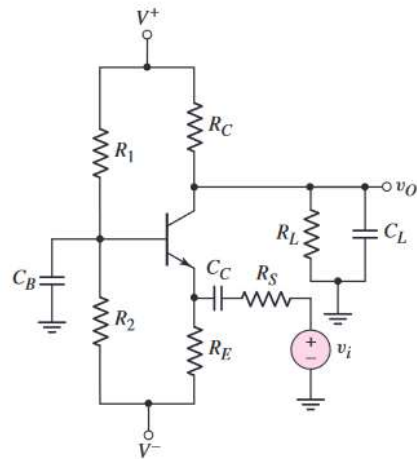

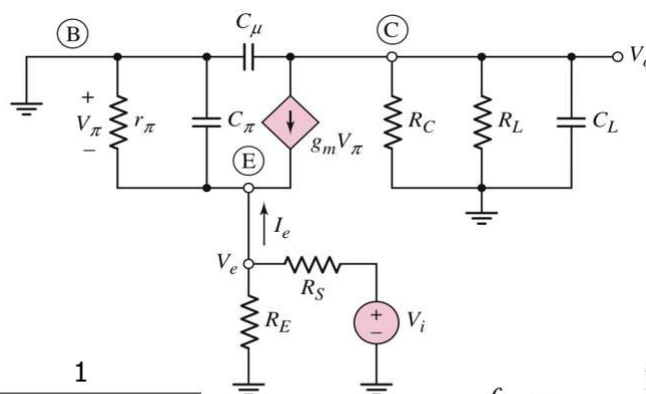High-Frequency Equivalent Circuit: Common Base




$$f_{H\pi} = \frac{1}{2\pi \left[\frac{r_\pi}{1 + \beta} \parallel R_E \parallel R_S \right] C_\pi}$$


(a)

$$f_{H\mu} = \frac{1}{2\pi (R_C \parallel R_L) C_\mu}$$


PSpice Results for Common Base

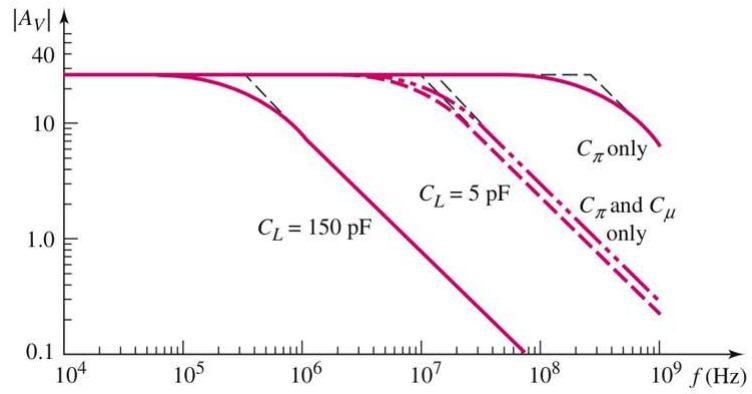

Cascode Circuit

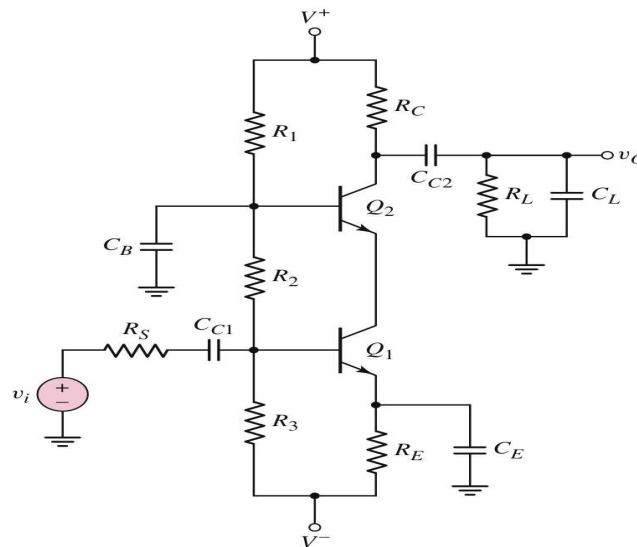

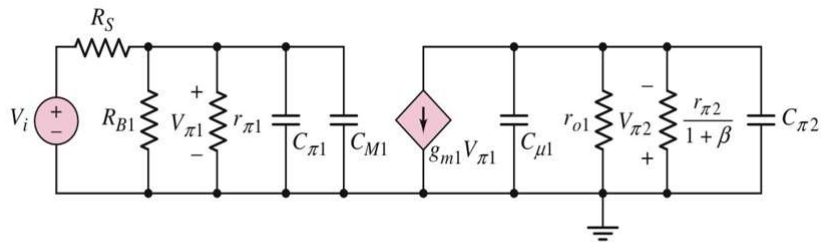High-Frequency Equivalent Circuit: Cascode




(c)


$$f_{H\pi} = \frac{1}{2\pi[R_S \parallel R_{B1} \parallel r_{\pi 1}](C_{\pi 1} + C_{M1})}$$

$$f_{H\mu} = \frac{1}{2\pi(R_C \parallel R_L)C_{\mu 2}}$$


PSpice Results for Cascode

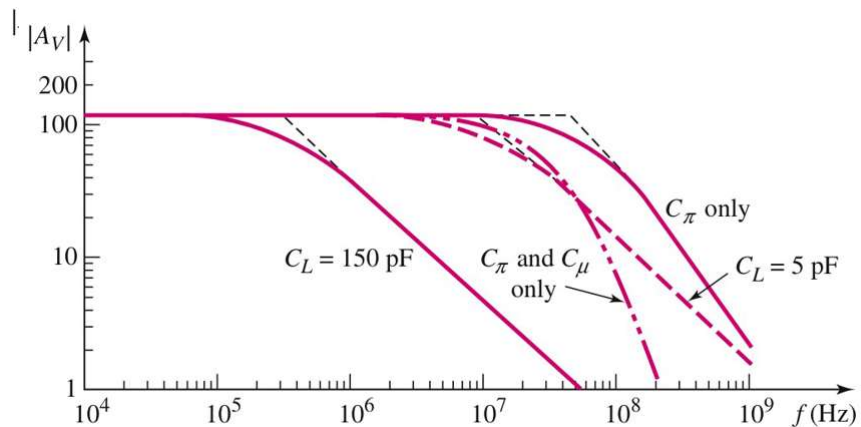

Emitter-Follower Circuit

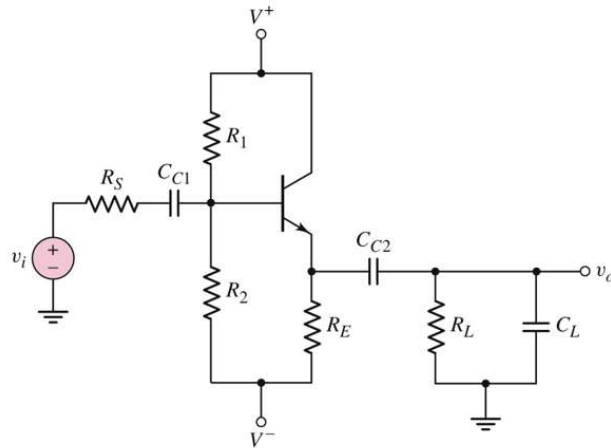

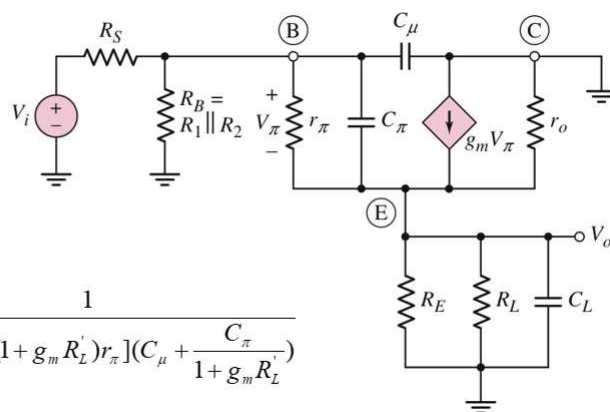High-Frequency Equivalent Circuit: Emitter Follower



$$f_H \cong \frac{1}{2\pi [R_S \parallel R_B \parallel (1 + g_m R_L') r_\pi] (C_\mu + \frac{C_\pi}{1 + g_m R_L'})}$$

PSpice Results for Emitter Follower

