



Laboratorij za načrtovanje integriranih vezij

**FE**

UNIVERZA V LJUBLJANI

Fakulteta za elektrotehniko


## Linearna elektronska vezja

### Osnove tranzistorjev FET


#### In this chapter, we will:

- ▶ Study and understand the operation and characteristics of the various types of MOSFETs.
- ▶ Understand and become familiar with the dc analysis and design techniques of MOSFET circuits.
- ▶ Examine three applications of MOSFET circuits.
- ▶ Investigate current source biasing of MOSFET circuits, such as those used in integrated circuits.
- ▶ Analyze the dc biasing of multistage or multitransistor circuits.


### Basic Structure of MOS Capacitor

 


### Cross Section of nMOSFET

 

 
## Conventional vs FinFET and Gate-All-Around Structure




## Basic Transistor Operation

 


## Basic Transistor Operation

 

 
## Current Versus Voltage Characteristics: Enhancement-Mode nMOSFET



 
### Family of $i_D$ Versus $v_{DS}$ Curves: Enhancement-Mode nMOSFET




### p-Channel Enhancement-Mode MOSFET

 

 
### Symbols for n-Channel Enhancement-Mode MOSFET




 
### Symbols for p-Channel Enhancement-Mode MOSFET





### n-Channel Depletion-Mode MOSFET

 

  
### Family of $i_D$ Versus $v_{DS}$ Curves: Depletion-Mode nMOSFET



Symbols

  

## CMOS Inverter Layout

 

## Summary of I-V Relationships

Region	NMOS	PMOS
Nonsaturation	$v_{DS} < v_{DS}(\text{sat})$ $i_D = K_n [2(v_{GS} - V_{TN})v_{DS} - v_{DS}^2]$	$v_{SD} < v_{SD}(\text{sat})$ $i_D = K_p [2(v_{SG} + V_{TP})v_{SD} - v_{SD}^2]$
Saturation	$v_{DS} > v_{DS}(\text{sat})$ $i_D = K_n [v_{GS} - V_{TN}]^2$	$v_{SD} > v_{SD}(\text{sat})$ $i_D = K_p [v_{SG} + V_{TP}]^2$
Transition Pt.	$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$	$v_{SD}(\text{sat}) = v_{SG} + V_{TN}$
Enhancement Mode	$V_{TN} > 0V$	$V_{TP} < 0V$
Depletion Mode	$V_{TN} < 0V$	$V_{TP} > 0V$

### Conduction Parameters

► NMOSFET

$$K_n = \frac{W\mu_n C_{ox}}{2L} = \frac{k'_n W}{2L}$$


► PMOSFET

$$K_p = \frac{W\mu_p C_{ox}}{2L} = \frac{k'_p W}{2L}$$


where:

$$C_{ox} = \epsilon_o / t_{ox}$$

 
### Channel Length Modulation: Early Voltage




## Body Effect

 


## Subthreshold Condition

 


### NMOS Common-Source Circuit

 

### PMOS Common-Source Circuit

 


 
### Load Line and Modes of Operation: NMOS Common-Source Circuit




### Problem-Solving Technique: NMOSFET DC Analysis

1. Assume the transistor is in saturation.
  - a.  $V_{GS} > V_{TN}$ ,  $I_D > 0$ , &  $V_{DS} \geq V_{DS}(\text{sat})$
2. Analyze circuit using saturation I-V relations.
3. Evaluate resulting bias condition of transistor.
  - a. If  $V_{GS} < V_{TN}$ , transistor is likely in cutoff
  - b. If  $V_{DS} < V_{DS}(\text{sat})$ , transistor is likely in nonsaturation region
4. If initial assumption is proven incorrect, make new assumption and repeat Steps 2 and 3.


### Enhancement Load Device

  

 
### Circuit with Enhancement Load Device and NMOS Driver



 
Voltage Transfer Characteristics:  
NMOS Inverter with Enhancement Load Device




NMOS Inverter with Depletion Load Device

 


### CMOS Inverter

 


### 2-Input NMOS NOR Logic Gate

 


### MOS Small-Signal Amplifier

 

### Current Mirrors

 

## 2-Stage Cascade Amplifier

 

## NMOS Cascode Circuit

