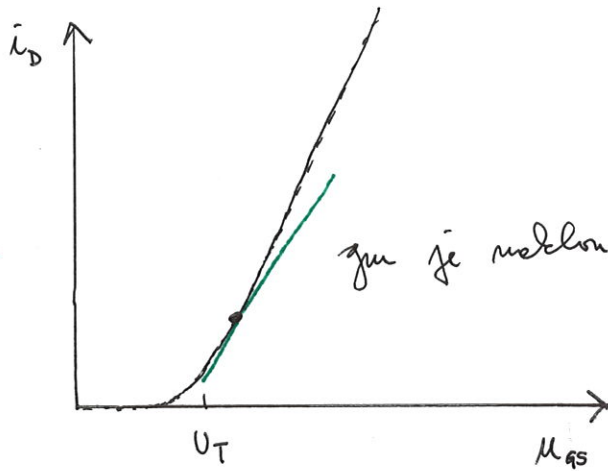


$$i_D = I_D + i_d$$

$$i_d = I_d \cdot \sin \omega t$$



g_m je malom tangente

$$g_m = \frac{\partial i_D}{\partial U_{GS}}$$

Zanimivo nos spreminjena točka i_D gleda ne spreminjena U_{GS} n. D.T.

$$i_D = K_N \cdot (U_{GS} - U_{TN})^2$$

TRANSKONDUKTANCA:

$$\left. \frac{\partial i_D}{\partial U_{GS}} \right|_{D.T.} = 2 K_N \cdot (U_{GS} - U_{TN}) \Big|_{D.T.} = \frac{2 K_N \cdot (U_{GS} - U_{TN})}{1}$$


$$I_D = K_N \cdot (U_{GS} - U_{TN})^2 \Rightarrow U_{GS} - U_{TN} = \sqrt{\frac{I_D}{K_N}}$$

$$= 2 K_N \cdot \sqrt{\frac{I_D}{K_N}} = \underline{2 \sqrt{K_N \cdot I_D}}$$

$$g_m = \left. \frac{\partial i_D}{\partial U_{GS}} \right|_{D.T.}$$

$$i_D = g_m \cdot U_{GS}$$
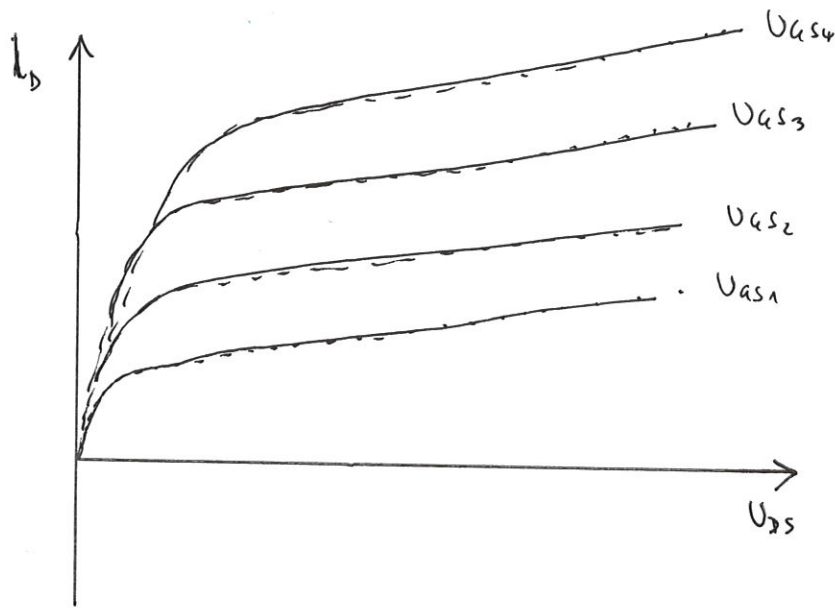
$$g_m = 2 K_N \cdot (U_{GS} - U_{TN}) = 2 \sqrt{K_N \cdot I_D}$$



$$i_D = K_N \cdot (U_{GS} - U_{TN})^2 (1 + \lambda U_{DS})$$

IZHODNA UPORNOST = R_{izh}

$$\left. \frac{\partial U_{DS}}{\partial i_D} \right|_{D.T.}$$

$$\left. \frac{\partial i_D}{\partial U_{DS}} \right|_{D.T.} = R_{izh}^{-1}$$

$$\left. \frac{\partial i_D}{\partial U_{DS}} \right|_{D.T.} = \underbrace{K_N \cdot (U_{GS} - U_{TN})^2}_{\doteq I_D} \cdot \lambda$$


$$\frac{1}{R_{izh}} = \lambda \cdot I_D \Rightarrow R_{izh} = \underline{\underline{\frac{1}{\lambda \cdot I_D}}}$$

$$u_o = -g_m \cdot u_{gs} \cdot (r_o \parallel R_D)$$

$$u_{gs} = u_i$$

$$u_o = -g_m \cdot u_i \cdot (r_o \parallel R_D)$$
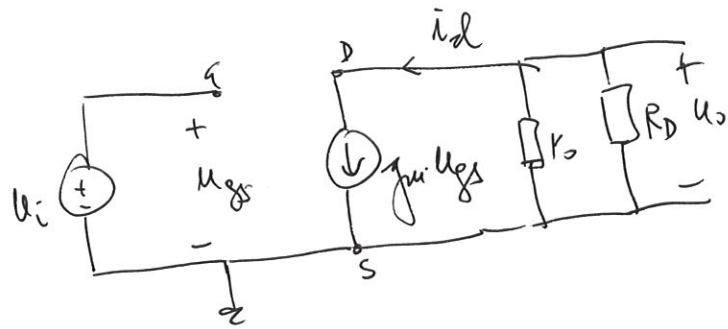
$$A_u = \frac{u_o}{u_i} = \underline{-g_m (r_o \parallel R_D)}$$



A_u je negativno!


u_o u u_i ste u protifazi

$$u_o = -g_m \cdot u_{gs} \cdot r_o \parallel R_D$$


$$u_{gs} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}} \cdot u_i$$

$$u_o = -g_m \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}} \cdot u_i \cdot r_o \parallel R_D$$

$$A_u = \frac{u_o}{u_i} = \underline{-g_m \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}} \cdot r_o \parallel R_D}$$

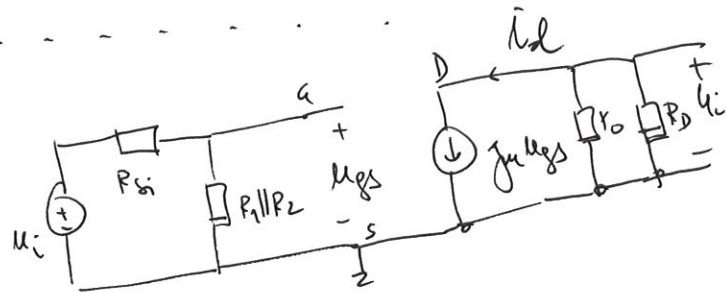

Ex. 4.3

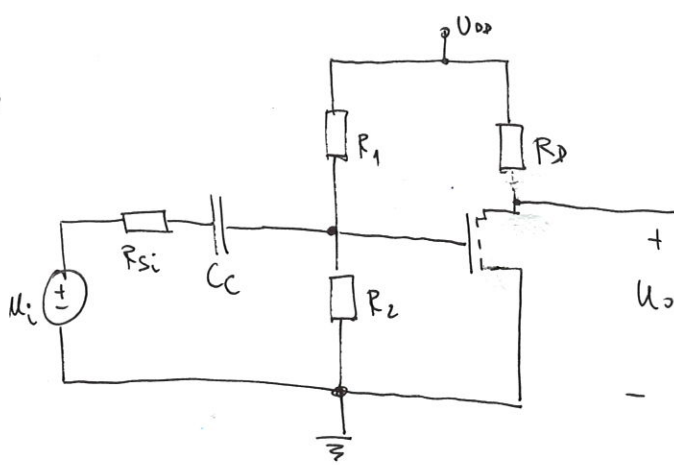

(4)

$$U_{DD} = 3.3V$$

$$R_D = 10k\Omega$$

$$R_1 = 140k\Omega$$

$$R_2 = 60k\Omega$$

$$R_{Si} = 4k\Omega$$

$$C_C = 10\mu F$$

$$U_{TD} = 0.4V$$

$$K_p = 0.5 \frac{mA}{V^2}$$

$$\lambda = 0.02 V^{-1}$$

$$U_{GS} = \frac{R_2}{R_1 + R_2} \cdot U_{DD} = \frac{60k\Omega}{140k\Omega + 60k\Omega} \cdot 3.3V = \underline{0.99V}$$

$$I_D = K_p \cdot (U_{GS} - U_{TD})^2 = 0.5 \frac{mA}{V^2} \cdot (0.99V - 0.4V)^2 = \underline{0.174mA}$$

$$U_{DS} = U_{DD} - I_D \cdot R_D = 3.3V - 0.174mA \cdot 10k\Omega = \underline{1.56V}$$

NASTRČENJE?

$$U_{DS} > U_{GS} - U_{TD}$$

$$1.56V > 0.99V - 0.4V \quad \checkmark$$

$$g_m = 2\sqrt{K_p \cdot I_D}$$

$$= 2\sqrt{0.5 \frac{mA}{V^2} \cdot 0.174mA} = \underline{0.59mS}$$

$$r_o = \frac{1}{\lambda \cdot I_D} = \frac{1}{0.02 \frac{1}{V} \cdot 0.174mA} = \underline{287k\Omega}$$

$$A_u = -g_m \cdot \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}} \cdot r_o \parallel R_D$$

$$= -0.59mS \cdot \frac{42k\Omega}{42k\Omega + 4k\Omega} \cdot 287k\Omega \parallel 10k\Omega = \underline{-5.21}$$

$$R_i = R_1 \parallel R_2 = \underline{42k\Omega}$$


$$R_o = r_o \parallel R_D = 287k\Omega \parallel 10k\Omega = \underline{9.66k\Omega}$$

$$u_{gs} = \frac{R_i}{R_i + R_{Si}} \cdot u_i$$

$$u_{gs} = \frac{42k\Omega}{42k\Omega + 4k\Omega} \cdot u_i = \underline{0.91}$$

LOADING EFFECT

5

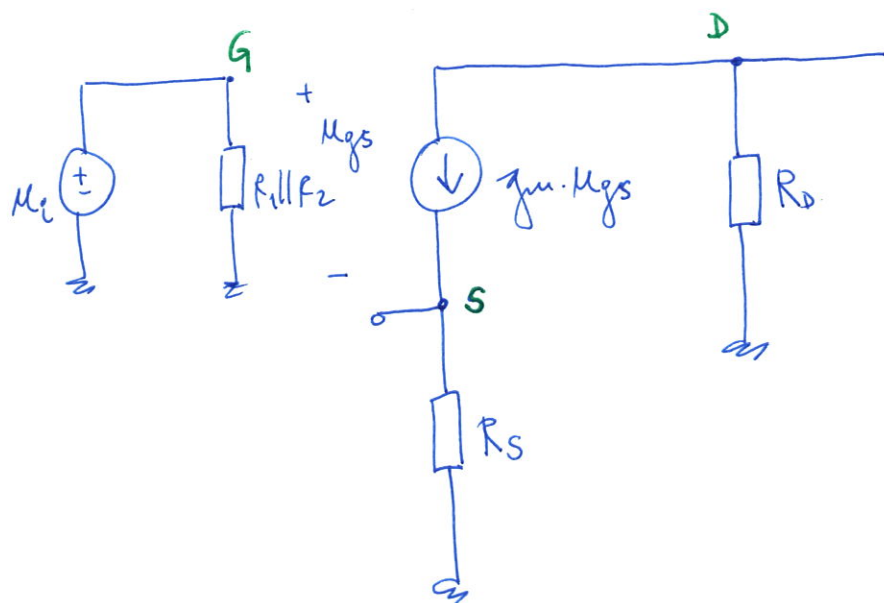

$$u_i = u_{gs} + g_m \cdot u_{gs} \cdot R_s$$

$$u_{izh} = -g_m \cdot u_{gs} \cdot R_D$$

$$u_i = (1 + g_m \cdot R_s) \cdot u_{gs}$$

$$u_{izh} = -g_m R_D \cdot \frac{u_i}{1 + g_m R_s}$$

$$u_{gs} = \frac{u_i}{1 + g_m \cdot R_s}$$


$$A_u = \frac{u_{izh}}{u_{ih}} = - \frac{g_m R_D}{1 + g_m R_s}$$

ZMANJSŠAMO VPLIV SPREMEMB GEOMETRIJE TRANZ. NA A_u
(PARAMETROV)

K_N	g_m	A_u
0.72	0.912	-2.44
0.80	0.974	-2.48
0.88	1.03	-2.52

$$\pm 10\% \longrightarrow \pm 1.8\%$$

Vendar manjše A_u !

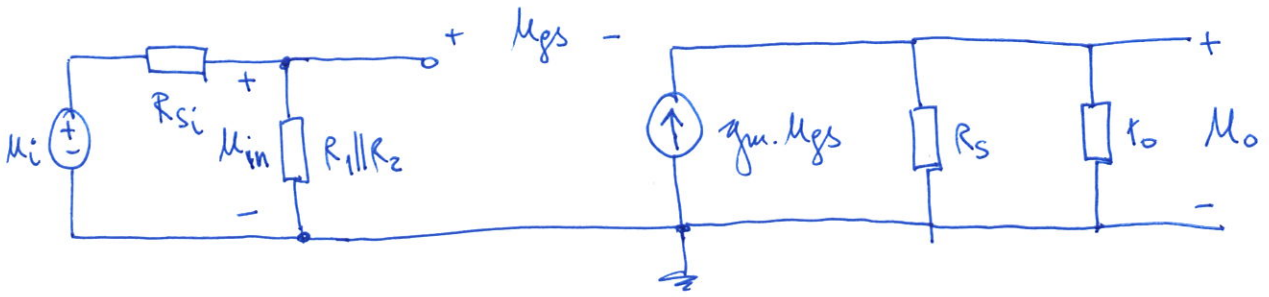

$$u_o = g_m \cdot u_{in} \cdot (R_s \parallel r_o)$$

$$u_{in} = u_{gs} + u_o = u_{gs} + g_m \cdot u_{in} \cdot (R_s \parallel r_o)$$

$$u_{in} = (1 + g_m (R_s \parallel r_o)) \cdot u_{gs}$$

$$u_{gs} = \frac{u_{in}}{1 + g_m (R_s \parallel r_o)} = \frac{\frac{1}{g_m}}{\frac{1}{g_m} + R_s \parallel r_o} \cdot u_{in}$$

$$u_o = g_m \cdot (R_s \parallel r_o) \cdot \frac{\frac{1}{g_m}}{\frac{1}{g_m} + R_s \parallel r_o} \cdot u_{in}$$


$$u_{in} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{si}} \cdot u_i$$

$$= \frac{R_i}{R_i + R_{si}} \cdot u_i$$

$$u_o = \frac{R_s \parallel r_o}{\frac{1}{g_m} + R_s \parallel r_o} \cdot \frac{R_i}{R_i + R_{si}} \cdot u_i$$

$$A_u = \frac{u_o}{u_i} = \underbrace{\frac{R_s \parallel r_o}{\frac{1}{g_m} + R_s \parallel r_o}}_{< 1} \cdot \underbrace{\frac{R_i}{R_i + R_{si}}}_{< 1} \Rightarrow A_u < 1$$

7

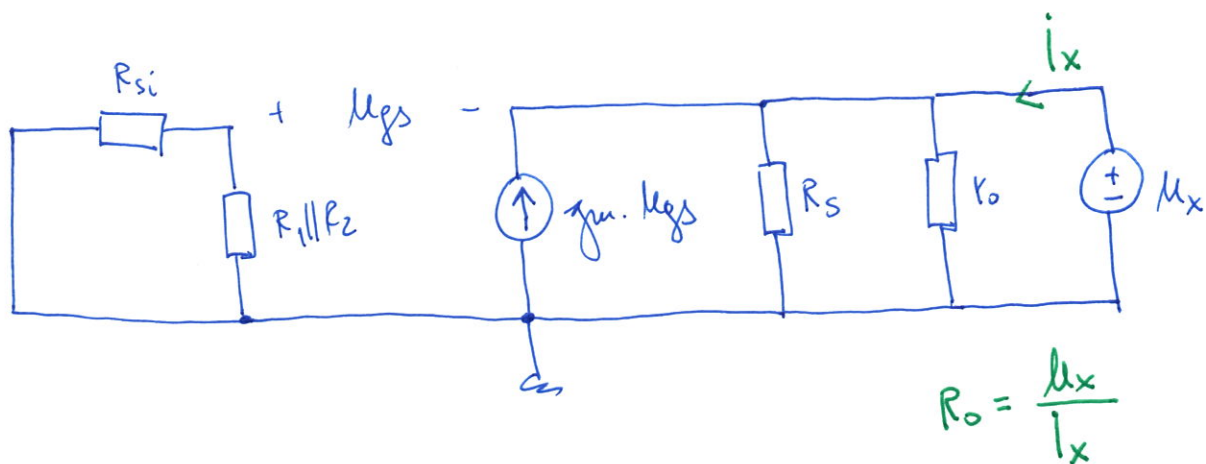


$$i_x + g_m \cdot u_{gs} = \frac{u_x}{R_s} + \frac{u_x}{r_o} \quad u_{gs} = -u_x$$

$$i_x = u_x \cdot \left(g_m + \frac{1}{R_s} + \frac{1}{r_o} \right)$$

$$\frac{i_x}{u_x} = \frac{1}{R_o} = g_m + \frac{1}{R_s} + \frac{1}{r_o} \Rightarrow R_o = \frac{1}{g_m} \parallel R_s \parallel r_o$$

$\sim \Omega$

R_o je mizka ↓

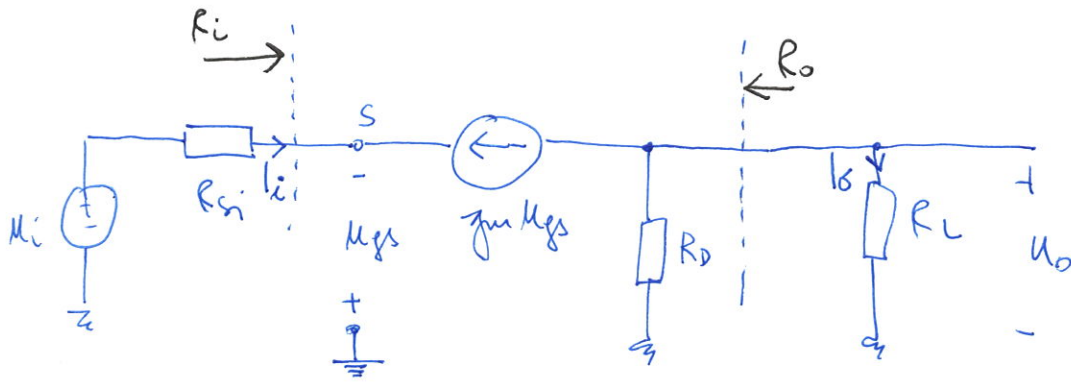

$$R_i = \frac{-u_{gs}}{i_i} = \frac{-u_{gs}}{-g_m u_{gs}} = \frac{1}{g_m} \text{ NIZKA!}$$


R_o

$$u_i = 0$$

$$u_{gs} = -g_m u_{gs} R_{si} \Rightarrow u_{gs} = 0$$

$$g_m u_{gs} = 0 \Rightarrow R_o = R_D$$

TO KOLIKO OJAKANJE

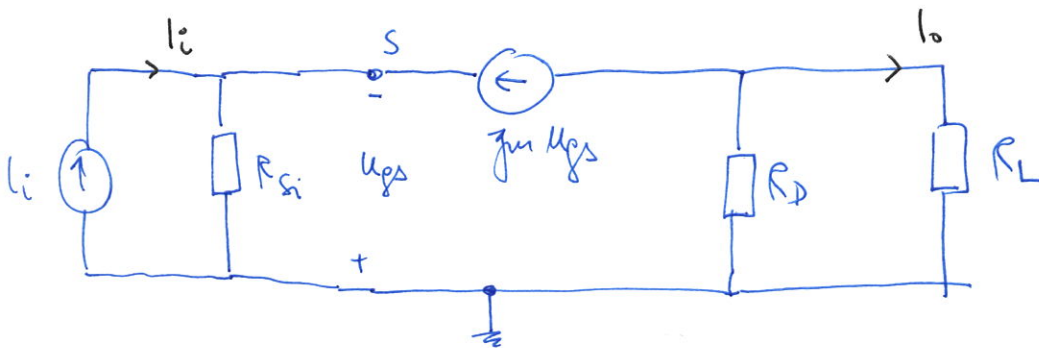

$$i_o = \frac{R_D}{R_D + R_L} \cdot (-g_m u_{gs})$$



$$i_i + g_m u_{gs} + \frac{u_{gs}}{R_{si}} = 0$$

$$i_i = -u_{gs} \cdot \left(g_m + \frac{1}{R_{si}} \right) = -u_{gs} \left(\frac{1 + g_m R_{si}}{R_{si}} \right)$$

$$i_o = \frac{R_D}{R_D + R_L} \cdot \frac{g_m R_{si}}{1 + g_m R_{si}} \cdot i_i$$

$$u_{gs} = -i_i \frac{R_{si}}{1 + g_m R_{si}}$$
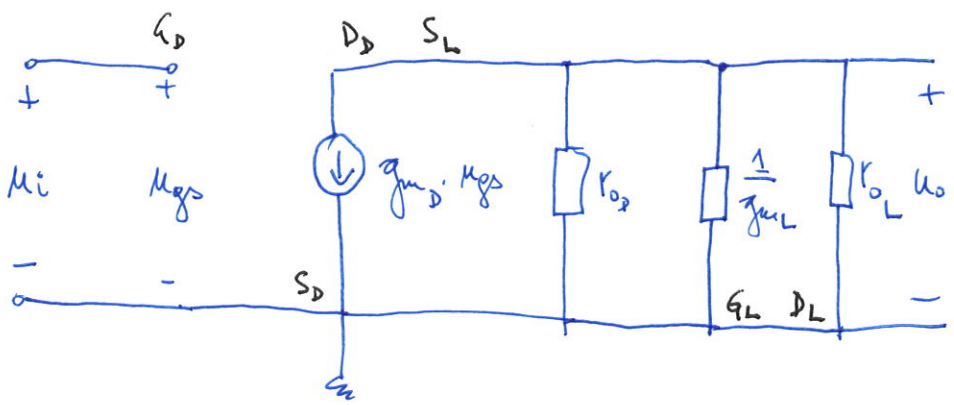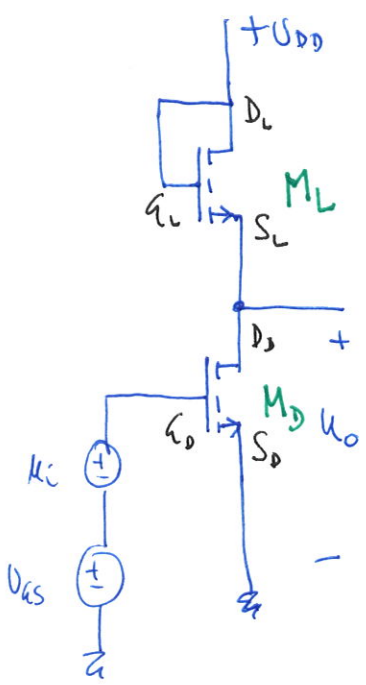
$$A_i = \frac{i_o}{i_i} = \frac{R_D}{R_D + R_L} \cdot \frac{g_m R_{si}}{1 + g_m R_{si}}$$





$$u_o = -g_{mD} \cdot u_{gs} \cdot (r_{oD} \parallel \frac{1}{g_{mL}} \cdot r_{oL})$$


$$u_o = -g_{mD} \cdot \frac{1}{g_{mL}} \cdot i_i$$

$$A_u = \frac{u_o}{i_i} = -\frac{g_{mD}}{g_{mL}} = -\sqrt{\frac{K_{DD}}{K_{LL}}} = -\sqrt{\frac{(\frac{W}{L})_D}{(\frac{W}{L})_L}}$$

$$A_u = -\sqrt{\frac{W_D}{W_L}}$$

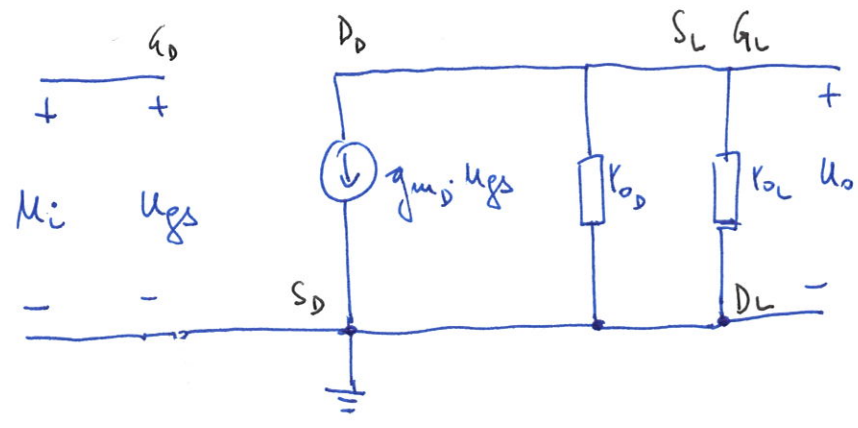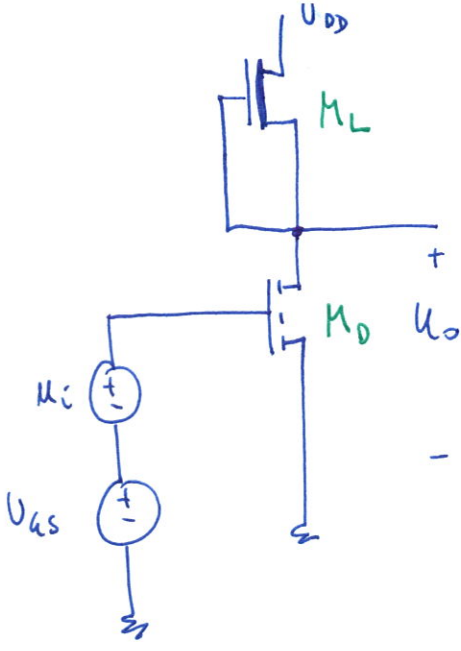
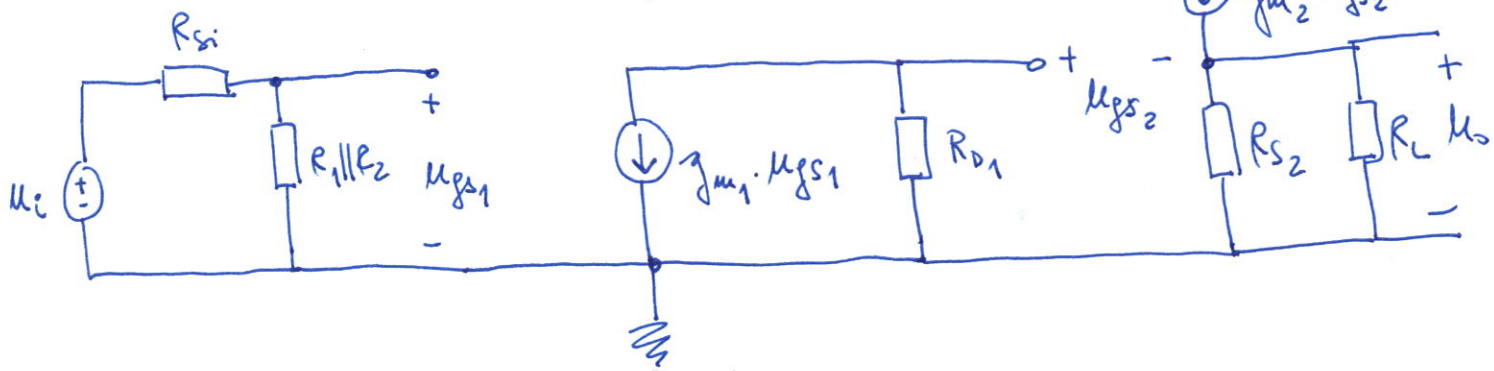
$$A_u = \frac{u_o}{u_i} = -g_{m0} \cdot (r_{o0} \parallel R_L)$$



$$u_o = g_{m2} u_{gs2} (R_{S2} \parallel R_L)$$

$$-g_{m1} \cdot u_{gs1} \cdot R_{D1} = u_{gs2} + u_o \Rightarrow u_{gs2} = -g_{m1} u_{gs1} R_{D1} - u_o$$

$$u_o = g_{m2} (R_{S2} \parallel R_L) \cdot (-g_{m1} u_{gs1} R_{D1} - u_o)$$

$$u_o (1 + g_{m2} (R_{S2} \parallel R_L)) = -g_{m1} g_{m2} (R_{S2} \parallel R_L) R_{D1} \cdot \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}} \cdot u_i$$

$$A_u = \frac{u_o}{u_i} = - \frac{g_{m1} \cdot g_{m2} \cdot (R_{S2} \parallel R_L) \cdot R_{D1} \cdot R_1 \parallel R_2}{1 + g_{m2} (R_{S2} \parallel R_L) \cdot (R_1 \parallel R_2 + R_{Si})}$$