



Laboratorij za načrtovanje integriranih vezij



FE

UNIVERZA V LJUBLJANI  
Fakulteta za elektrotehniko


## Linearna elektronska vezja

Tokovna zrcala in aktivna bremena


### In this chapter, we will:

- ▶ Analyze and understand the characteristics of various bipolar circuits used to provide a constant output current.
- ▶ Analyze and understand the characteristics of various MOSFET circuits used to provide a constant output current.
- ▶ Analyze the dc characteristics of amplifier circuits using transistors as load devices (active loads).
- ▶ Analyze the small-signal characteristics of amplifier circuits with active loads.


## 2-Transistor Current Source

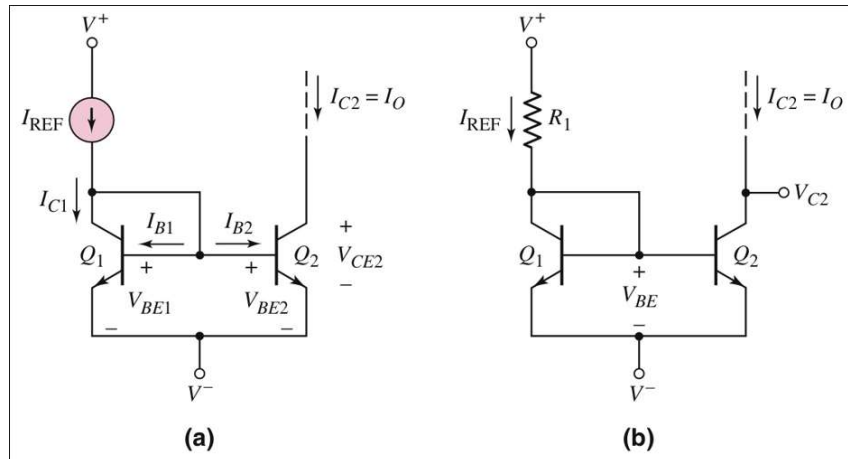

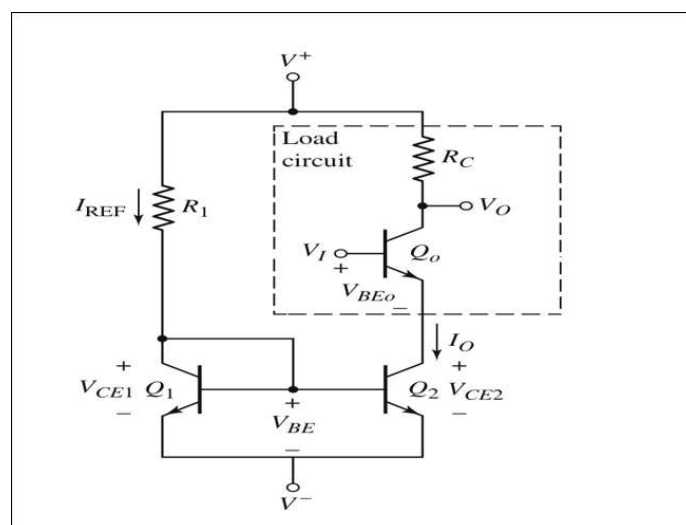
## DC Equivalent Circuit: 2-Transistor Current Source




### 3-Transistor Current Source

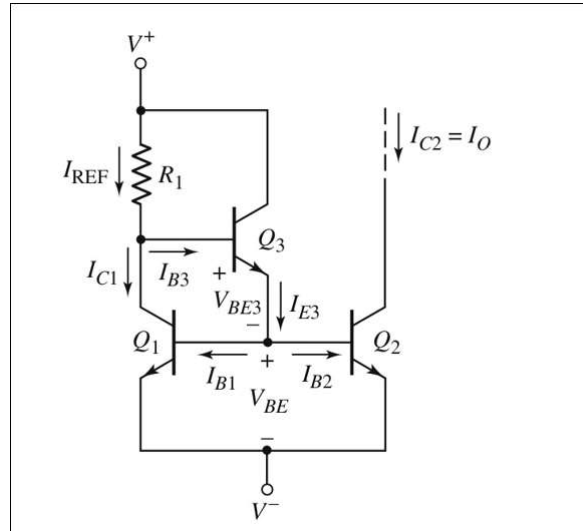

### Bipolar Cascode Current Mirror

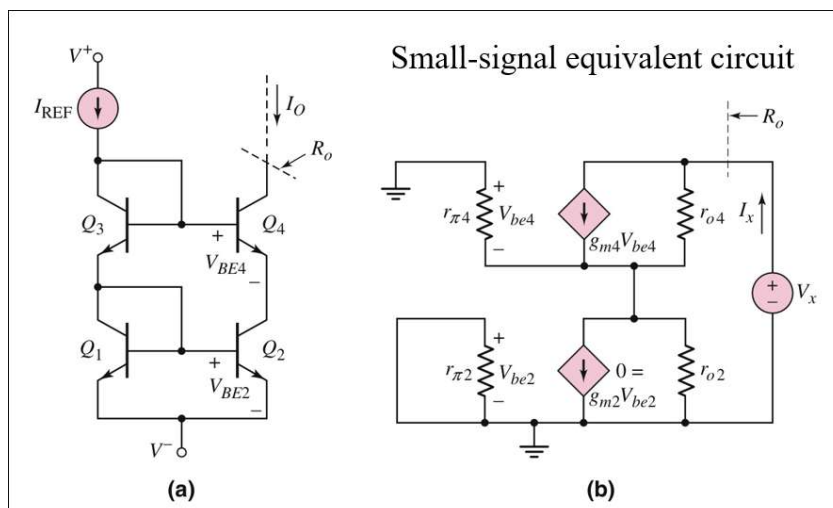

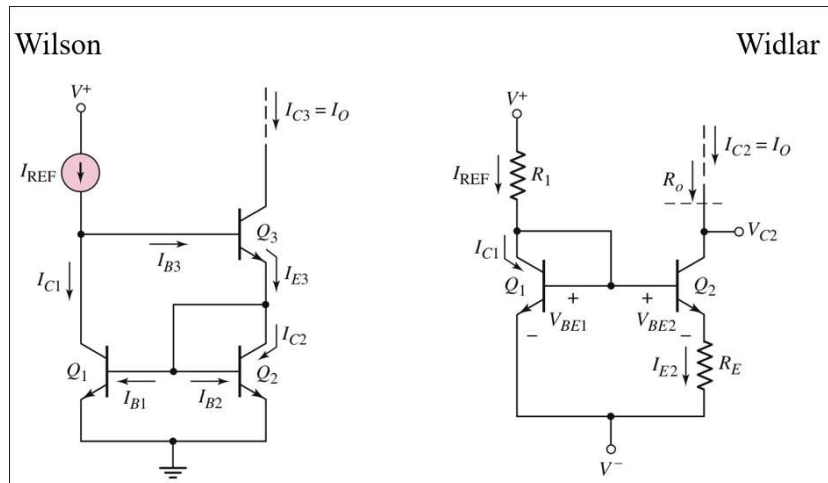
### Problem-Solving Technique: Ideal Op-Amp Circuits




### Problem-Solving Technique: BJT Current Source Circuits

- ▶ Sum currents at various nodes to find relation between reference and bias currents.
- ▶ Place test voltage at output node and analyze small-signal equivalent circuit to find output resistance.
- ▶ Reference current is a constant
  - ▶ Some base voltages may be constant or at ac ground.

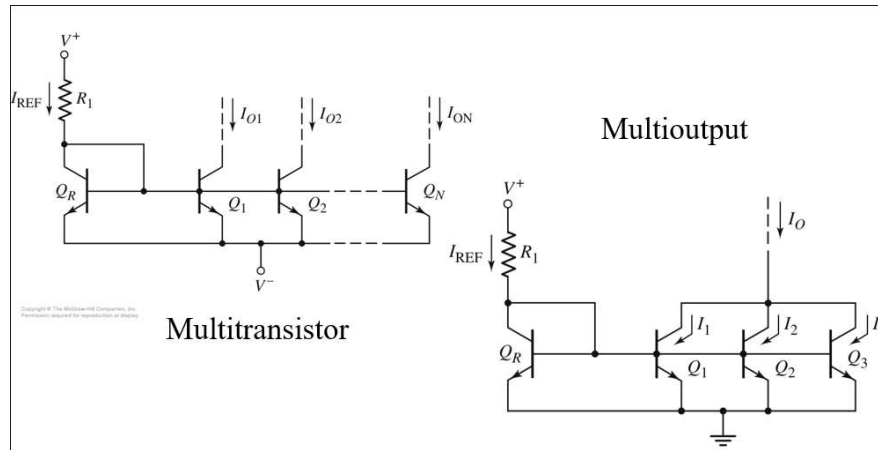
### Multitransistor and Multioutput Current Mirror




### Generalized Current Mirror

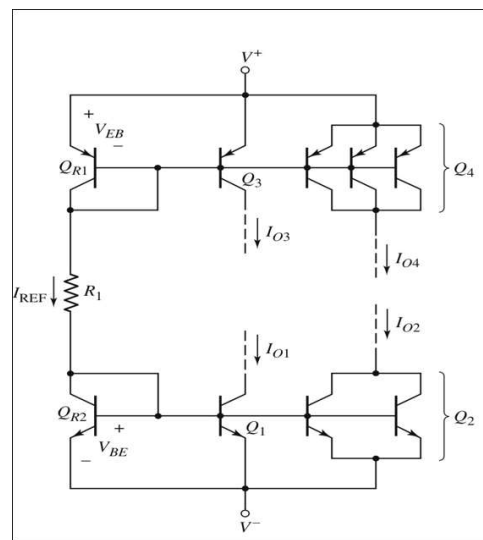


## MOSFET Current Source

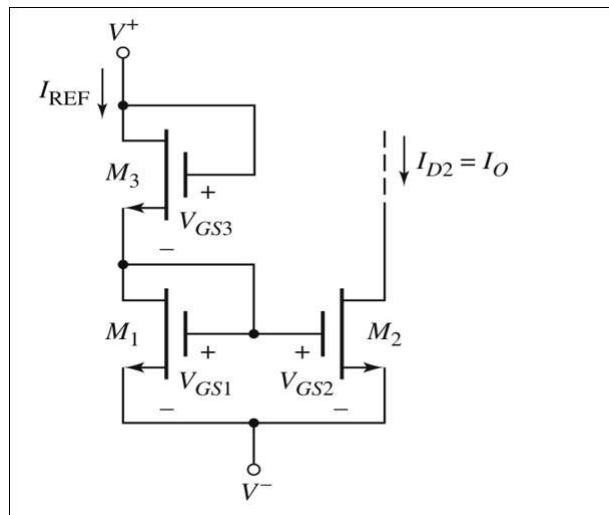


## MOSFET Cascode Current Source

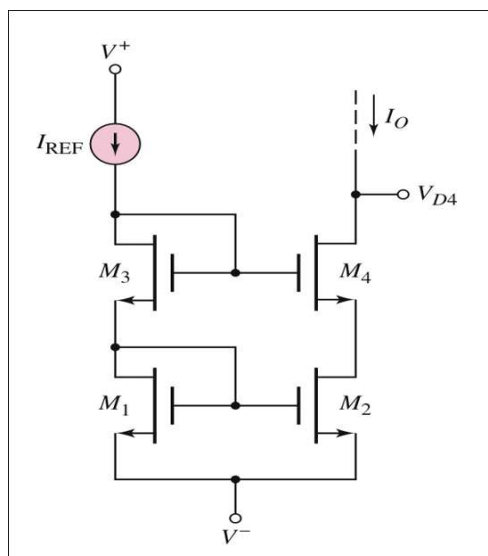

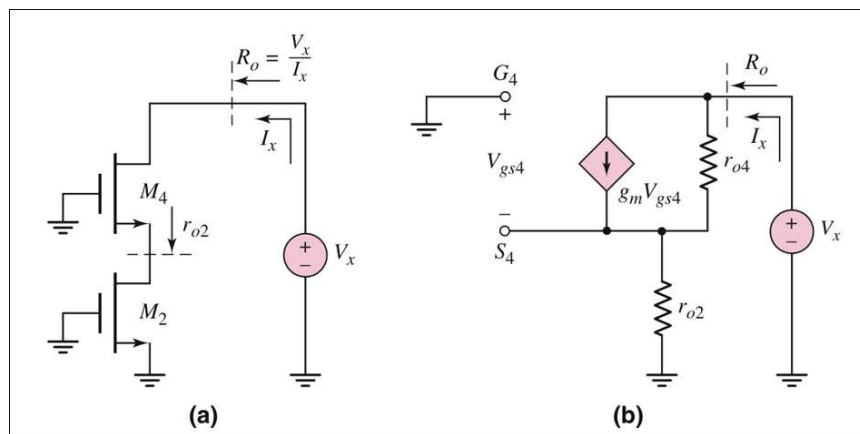
### Equivalent Circuits for MOSFET Cascode Current Mirror




### MOSFET Wilson Current Source

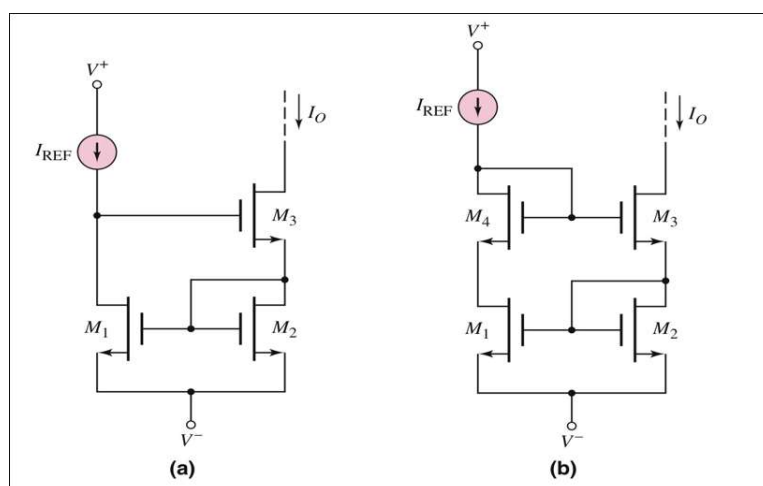

### BJT Amplifier with Active Load

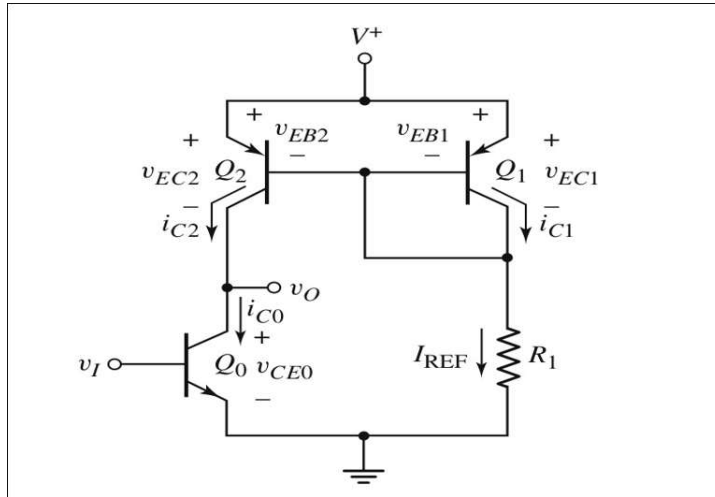

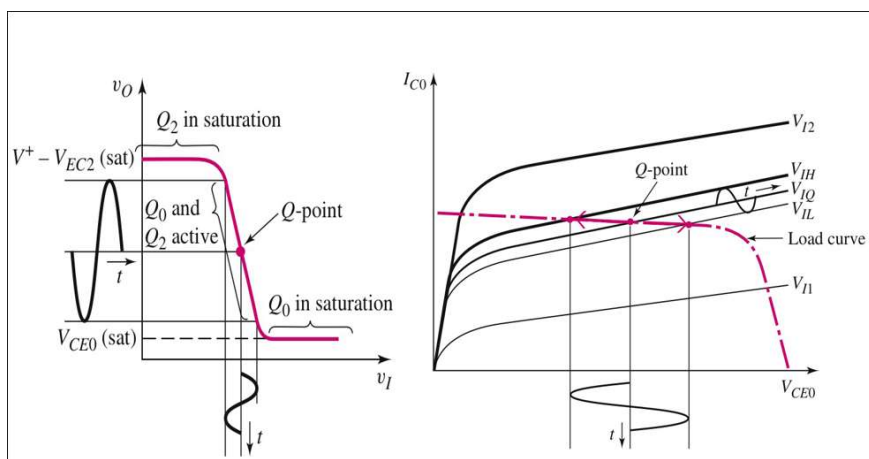
### Characteristics of Bipolar Circuit with Active Load







### MOSFET Amplifier with Active Load

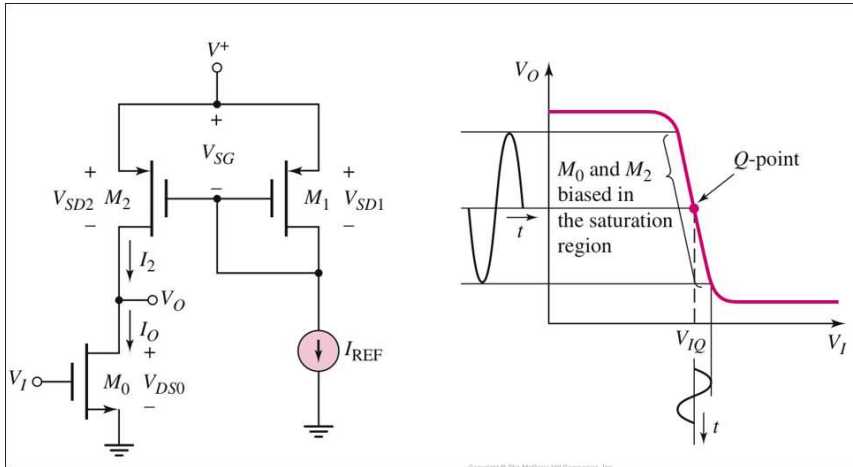
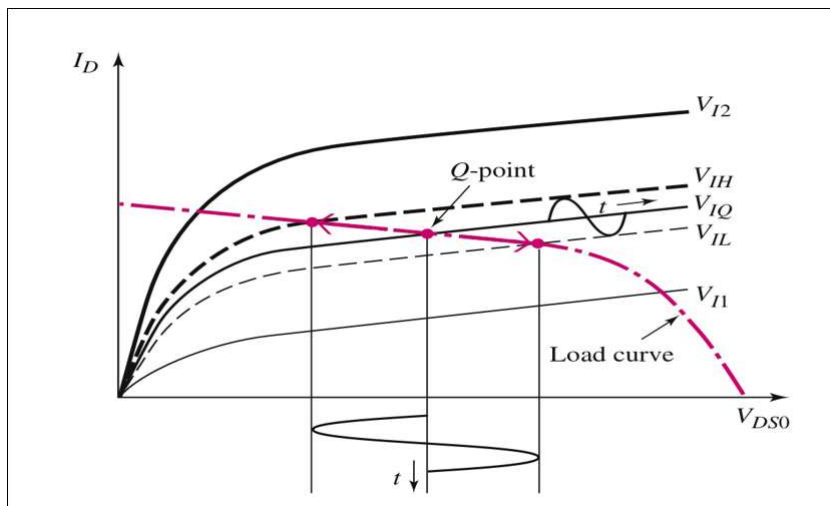
### Driver Characteristics: MOSFET Amplifier with Active Load



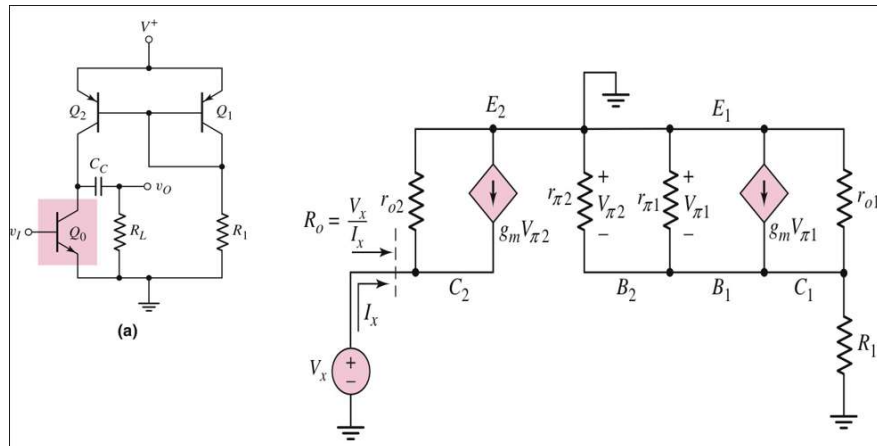
### Small-Signal Equivalent Circuit: BJT Active Load



### Problem-Solving Technique: BJT Active Loads

- ▶ Ensure active load devices are biased in forward active mode.
- ▶ Small-signal analysis considers output resistance looking back into output of active load device as well as the equivalent circuit of amplifying transistor.
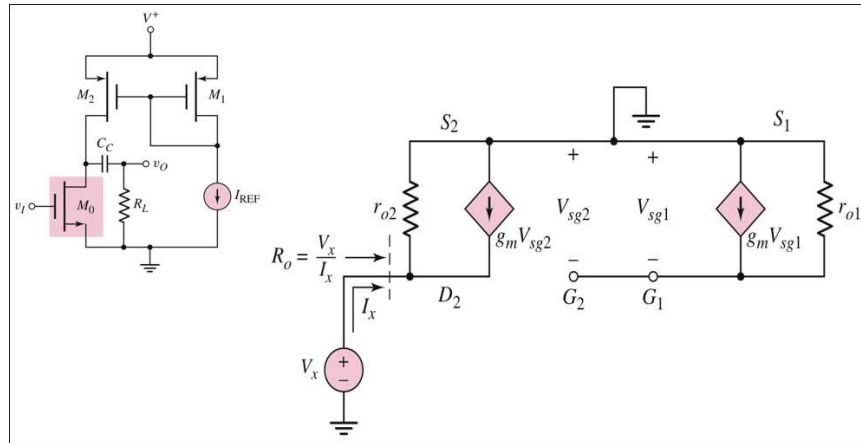
### Small-Signal Equivalent Circuit: MOSFET Active Load



### MOSFET Cascode Amplifier with Cascode Active Load

